

Example- A Boolean function is defined as-


$$F_1 = A'B'C' + A'B'C + A'BC' + A'BC$$

- F_1 has 4 terms and 12 literals
- F_1 has a Truth Table

| A | B | C | A' | B' | C' | A'B'C' | A'B'C | A'BC' | A'BC | F ₁ |
|---|---|---|----|----|----|--------|-------|-------|------|----------------|
| 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

- F_1 has a logic-circuit diagram with 8 logic gates and three inputs-

$$F_1 = A'B'C' + A'B'C + A'BC' + A'BC$$

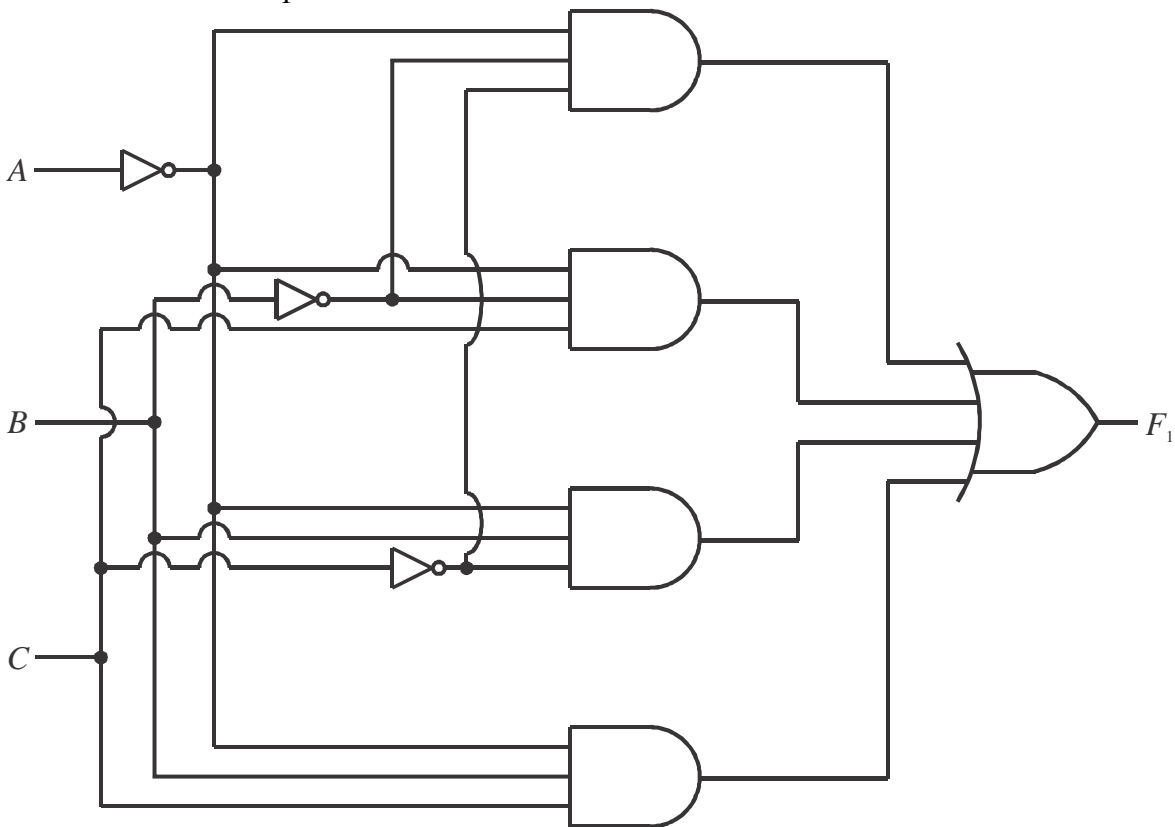

- Can F_1 be simplified using Basic Theorems & Postulates for Boolean algebra?

$$\begin{aligned}
 F_1 &= A'B'C' + A'B'C + A'BC' + A'BC \\
 &= A'[B'C' + B'C + BC' + BC] \text{ used Postulate 4(a) distributive} \\
 &= A'[B'(C' + C) + B(C' + C)] \text{ used Postulate 4(a) distributive} \\
 &= A'[B'(1) + B(1)] \text{ used Postulate 5(a)} \\
 &= A'[B' + B] \text{ used Postulate 2(b)} \\
 &= A'[1] \text{ used Postulate 5(a)} \\
 \underline{F_1} &= A' \text{ used Postulate 2(b)}
 \end{aligned}$$

Note that inputs B and C are unnecessary.

- Check that the simplified F_1 has same Truth Table → **Yes!**

| A | B | C | $F_1=A'$ |
|-----|-----|-----|----------|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

- Note that the simplified F_1 has much simpler logic-circuit diagram with 1 input & logic gate

