
 


Positive-edge-triggered *D* flip-flop (Figure 5.10 of text)


Copyright ©2013 Pearson Education, publishing as Prentice Hall

Set <i>S</i>	Reset <i>R</i>	<i>Q</i>	<i>Q'</i>	Notes
1	0	0	1	reset
1	1	0	1	no change
0	1	1	0	set
1	1	1	0	no change
0	0	1	1	'forbidden', don't know next state

 Positive-edge-triggered D flip-flop w/ asynchronous reset (Figure 5.14 of text)



(a) Circuit diagram

 

(b) Graphic symbol

<i>Reset</i>	<i>Clk</i>	<i>D</i>	<i>Q</i>	<i>Q'</i>
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

(b) Function table