

Example- A Boolean function is defined as-

$$\underline{F_2 = A'C' + A'B'C + A'BC + BC'}$$

- F_2 has 4 terms and 10 literals
- First create K-Map directly from function.
 - a) For term $A'C'$, we fill-in each square that has $A=0$ (i.e., A') AND $C=0$ (i.e., C') (should be two squares),

$A \setminus BC$	00	01	11	10
0	1	-	-	1
1	-	-	-	-

- b) for term $A'B'C$, we fill-in the square that has $A=0$ (i.e., A') AND $B=0$ (i.e., B') AND $C=1$ (i.e., C),

$A \setminus BC$	00	01	11	10
0	1	1		1
1				

- c) for term $A'BC$, we fill-in the square that has $A=0$ (i.e., A') AND $B=1$ (i.e., B) AND $C=1$ (i.e., C), and

$A \setminus BC$	00	01	11	10
0	1	1	1	1
1	-	-	-	-

- d) for term BC' , we also fill-in each square that has $B=1$ (i.e., B) AND $C=0$ (i.e., C') (should be two squares),

$A \setminus BC$	00	01	11	10
0	1	1	1	1
1	-	-	-	1

- Next, use this K-Map to directly express F_2 in the canonical sum-of-minterms form. Put the applicable minterm into each square where there is a “1”-

$A \setminus BC$	00	01	11	10
0	$m_0 = A'B'C'$	$m_1 = A'B'C$	$m_3 = A'BC$	$m_2 = A'BC'$
1	-	-	-	$m_6 = ABC'$

Therefore,
$$F_2 = m_0 + m_1 + m_2 + m_3 + m_6 = \sum (0,1,2,3,6)$$

$$= \underline{A'B'C' + A'B'C + A'BC + A'BC' + ABC'}$$

- Then, use this K-Map to directly express F_2 in simplified sum-of-products form.

$A \setminus BC$	00	01	11	10
0	1	1	1	1
1	-	-	-	1

- The first row has four adjacent squares which correspond to the single literal $A = 0$ (i.e., A').
- The rightmost column has two adjacent squares which corresponds to the two literals $BC = 10$ (i.e., BC').
- Therefore, the simplified sum-of-products form is-

$$\underline{F_2 = A' + BC'}$$

- Check these results using Truth Tables to show they agree.

$$F_2 = A'C' + A'B'C + A'BC + BC'$$

A	B	C	A'	B'	C'	A'C'	A'B'C	A'BC	BC'	F ₂
0	0	0	1	1	1	1	0	0	0	1
0	0	1	1	1	0	0	1	0	0	1
0	1	0	1	0	1	1	0	0	1	1
0	1	1	1	0	0	0	0	1	0	1
1	0	0	0	1	1	0	0	0	0	0
1	0	1	0	1	0	0	0	0	0	0
1	1	0	0	0	1	0	0	0	1	1
1	1	1	0	0	0	0	0	0	0	0

$$F_2 = A'B'C' + A'B'C + A'BC + A'BC' + ABC'$$


A	B	C	A'	B'	C'	A'B'C'	A'B'C	A'BC	A'BC'	ABC'	F ₂
0	0	0	1	1	1	1	0	0	0	0	1
0	0	1	1	1	0	0	1	0	0	0	1
0	1	0	1	0	1	0	0	0	1	0	1
0	1	1	1	0	0	0	0	1	0	0	1
1	0	0	0	1	1	0	0	0	0	0	0
1	0	1	0	1	0	0	0	0	0	0	0
1	1	0	0	0	1	0	0	0	0	1	1
1	1	1	0	0	0	0	0	0	0	0	0

$$F_2 = A' + BC'$$

A	B	C	C'	A'	BC'	F ₂
0	0	0	1	1	0	1
0	0	1	0	1	0	1
0	1	0	1	1	1	1
0	1	1	0	1	0	1
1	0	0	1	0	0	0
1	0	1	0	0	0	0
1	1	0	1	0	1	1
1	1	1	0	0	0	0

- The original F_2 has a logic-circuit diagram with 8 logic gates (three NOT, two 2-input AND, two 3-input AND, & a 4-input OR) and three inputs-

$$F_2 = A'C' + A'B'C + A'BC + BC'$$

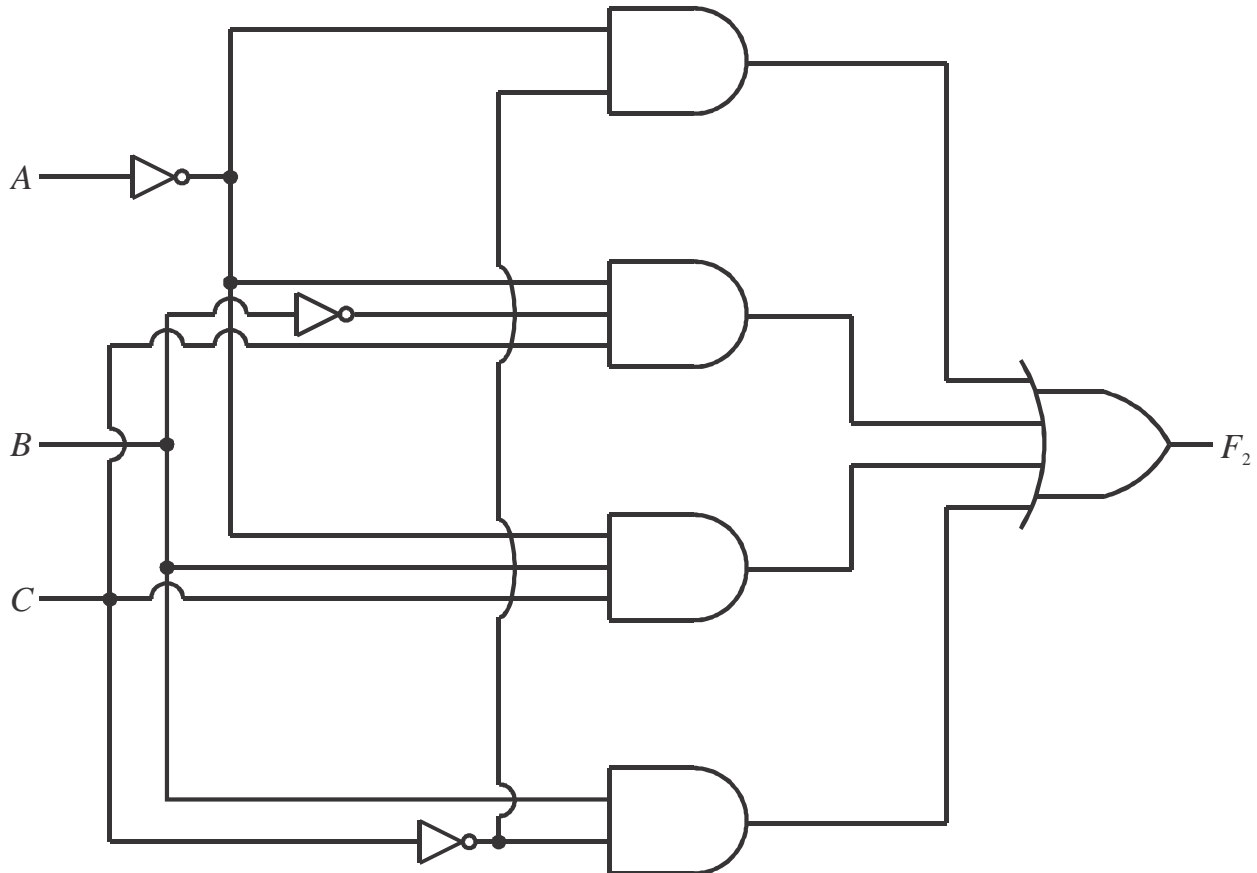

- Note that the simplified F_2 has much simpler logic-circuit diagram with four simpler logic gates (2 NOT, a 2-input AND, & a 2-input OR) and 3 inputs.

$$F_2 = A' + BC'$$

