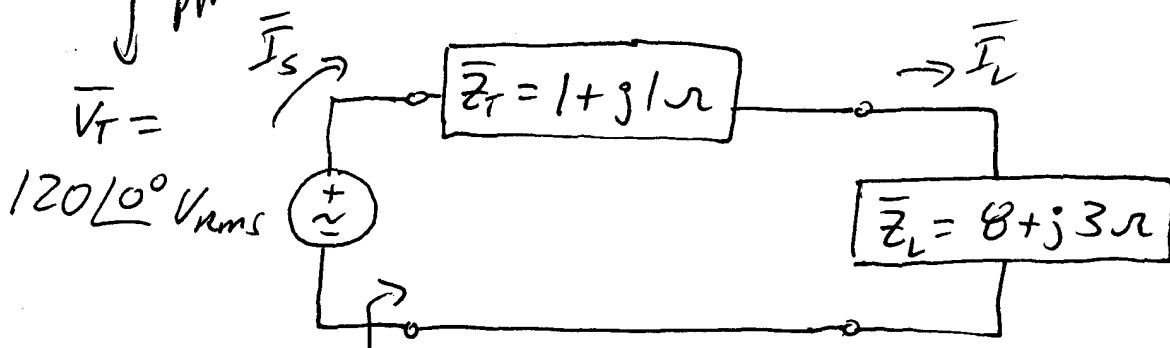


ex. \downarrow RMS Phasor!

$$\bar{Z}_{eq} = (1 + j1) + (8 + j3) = 9 + j4 \Omega$$

$$= 9.84886 \angle 23.96249^\circ \Omega$$

$$\bar{I}_s = \bar{I}_L = \frac{\bar{V}_T}{\bar{Z}_{eq}} = \frac{120\angle 0^\circ}{9.85\angle 24^\circ} = 12.184154 \angle -23.96249^\circ A_{rms}$$

\uparrow I_{rms}

Apparent Power
to load from source

$$S = V_{rms} I_{rms} = 120 (12.184)$$

$$S = \underline{\underline{1462.1 \text{ VA}}}$$

Power Factor
'seen' by source
of total load

$$pf = \cos \theta_z = \cos (\theta_v - \theta_f)$$

$$= \cos 23.96^\circ = \cos (0 - (-23.96^\circ))$$

$$pf = \underline{\underline{0.9138 \text{ lagging}}}$$

 \uparrow
R-L load!

$$P_{ave, source} = \text{Re} \{ \bar{V}_{rms} \bar{I}_{rms}^* \} = \text{Re} \{ (120\angle 0^\circ V_{rms}) (12.184\angle +23.96^\circ) \}$$

$$= \text{Re} \{ 1336.1 + j593.8 \} = \underline{\underline{1336.1 \text{ W}}} \text{ supplied}$$

$$P_{ave, load} = I_{L, rms}^2 R_L = (12.184)^2 8 = \underline{\underline{1187.6 \text{ W}}} \text{ absorbed}$$

$$P_{ave, Z_T} = I_{s, rms}^2 R_T = (12.184)^2 1 = \underline{\underline{148.45 \text{ W}}} \text{ absorbed}$$