

**Example-** For an AC motor, we measure the line voltage to be  $120 V_{\text{RMS}}$  and the line current to be  $12 A_{\text{RMS}}$  using a multimeter while the power is measured to be  $1150 \text{ W}$  using a wattmeter. Determine the apparent power, power factor, complex power, reactive power, and load impedance. [Hint: Motors are resistive-inductive loads.]

$$\text{Apparent Power } S = V_{\text{rms}} I_{\text{rms}} = 120(12)$$

$$\underline{\underline{S = 1440 \text{ VA}}}$$

$$\text{Power Factor } pf = \frac{P}{S} = \frac{1150}{1440} = \underline{\underline{0.7986 \text{ lagging}}}$$

↑  
Resistive -  
inductive

$$\theta_v - \theta_i = \theta_z = \theta_s = \cos^{-1}(pf) = \cos^{-1}(0.7986)$$

$$\underline{\underline{\theta_z = \theta_s = +37.002^\circ}}$$

$$\text{Complex Power } \underline{\underline{\bar{S} = S \angle \theta_s = 1440 \angle 37.002^\circ \text{ VA}}}$$

$$\underline{\underline{\bar{S} = 1150 + j866.66 \text{ VA}}}$$

$$\text{Reactive Power } \underline{\underline{Q = \text{Im}(\bar{S}) = 866.66 \text{ VAR}}}$$

$$Z_L = \frac{V}{I} = \frac{120}{12} = 10 \Omega \quad \leftarrow \text{Magnitude of impedance}$$

$$\underline{\underline{\bar{Z}_L = Z_L \angle \theta_z = 10 \angle 37.002^\circ \Omega = 7.986 + j6.018 \Omega}}$$