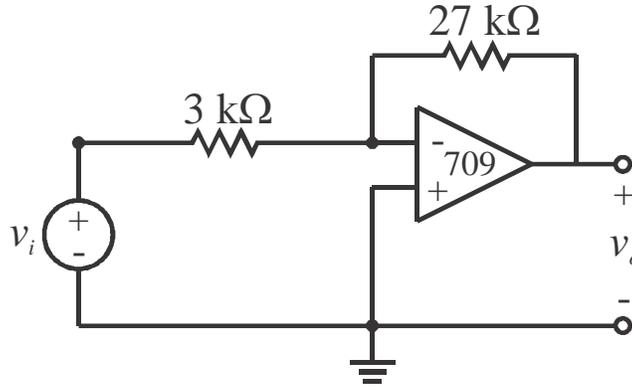



LM709 Op-Amp

- Inferior predecessor to very popular LM741 op-amp developed ~1968 by Dave Fullagar at Fairchild Semiconductor
- Consists of ~14 BJTs and 15 resistors
- $A = 45,000$, $R_i = 400 \text{ k}\Omega$, and $R_o = 150 \Omega$

Find the closed loop gain $A_v = v_o/v_i$ for the circuit below.



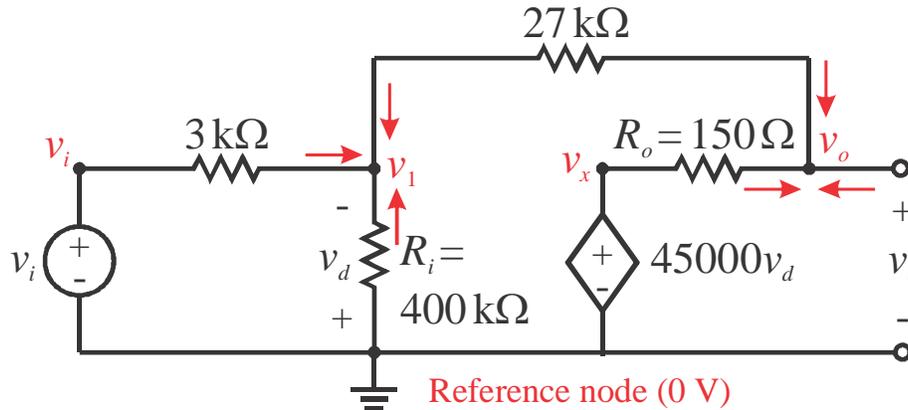Replace op-amp with equivalent circuit model.



Apply nodal analysis-

Input node: $v_i = v_i$

Node 1:
$$\frac{v_i - v_1}{3000} + \frac{0 - v_1}{400000} + \frac{v_o - v_1}{27000} = 0$$

Node x: $v_x = 45000v_d$

Output node:
$$\frac{v_1 - v_o}{27000} + \frac{v_x - v_o}{150} + 0 = 0$$

From the circuit, note that $v_1 = -v_d$.

\Rightarrow Modify output node equation $\frac{-v_d - v_o}{27000} + \frac{45000v_d - v_o}{150} = 0$ and solve for difference voltage to get:

$$v_d = \left(\frac{\frac{1}{27000} + \frac{1}{150}}{\frac{45000}{150} - \frac{1}{27000}} \right) v_o = \left(\frac{1 + 180}{8100000 - 1} \right) v_o = \left(\frac{181}{8099999} \right) v_o$$

\Rightarrow Modify node 1 equation $\frac{v_i + v_d}{3000} + \frac{v_d}{400000} + \frac{v_o + v_d}{27000} = 0$

\Rightarrow Substitute for difference voltage in the modified node 1 equation to get an equation solely in terms of v_i and v_o :

$$\frac{v_i + \left(\frac{181}{8099999} \right) v_o}{3000} + \frac{\left(\frac{181}{8099999} \right) v_o}{400000} + \frac{v_o + \left(\frac{181}{8099999} \right) v_o}{27000} = 0$$

Solve for the closed loop gain-

$$1 + \frac{\left(\frac{181}{8099999} \right) \frac{v_o}{v_i}}{3000} + \frac{\left(\frac{181}{8099999} \right) \frac{v_o}{v_i}}{400000} + \frac{\frac{v_o}{v_i} + \left(\frac{181}{8099999} \right) \frac{v_o}{v_i}}{27000} = 0$$

$$\frac{v_o}{v_i} \left(\frac{181}{8099999} \right) \left[\frac{1}{3000} + \frac{1}{400000} + \frac{\frac{8099999}{181} + 1}{27000} \right] = \frac{-1}{3000}$$

$$A_v = \frac{v_o}{v_i} = \frac{\frac{-1}{3000} \left(\frac{8099999}{181} \right)}{\frac{1}{3000} + \frac{1}{400000} + \frac{\frac{8099999}{181} + 1}{27000}}$$

$$\underline{A_v = -8.997975771}$$