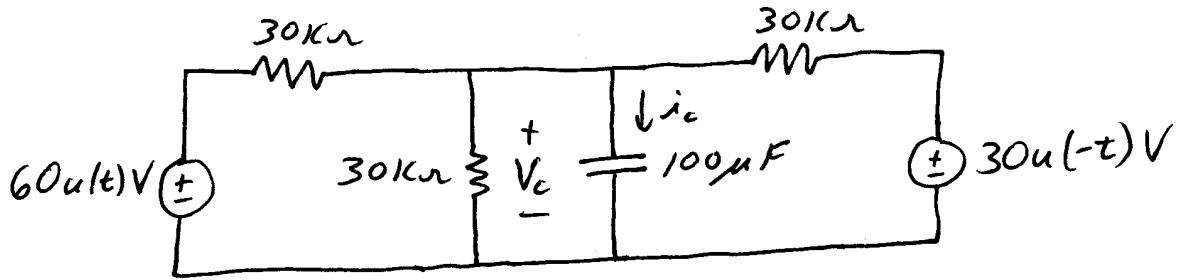


ex. Find  $i_c(t)$  and  $V_c(t)$  for all  $t \geq 0$  for the circuit.




For  $t \geq 0$ , the circuit undergoes a RC step response, as the  $60u(t)V$  turns on and the  $30u(-t)V$  source turns off. Applicable solution form is:

$$V_c(t) = V_c(\infty) + [V_c(0) - V_c(\infty)] e^{-t/\tau} \quad t \geq 0$$

where  $\tau = RC$ .

Find  $V_c(0)$

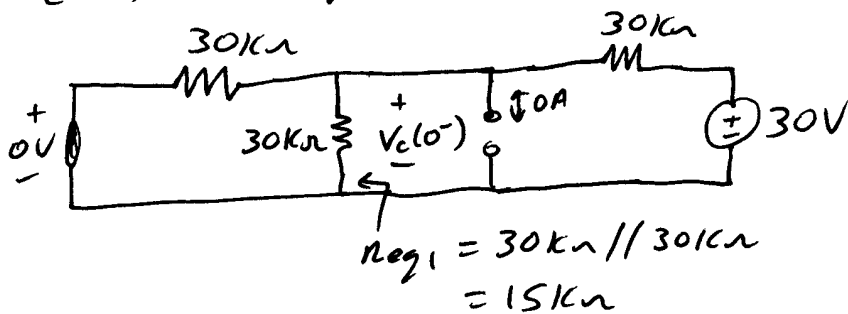→ Analyze circuit at time  $t = 0^-$ . Why? Circuit is at steady-state.  $60u(t)V = 0$  (short circuit),  $30u(-t)V = 30V$  (has been on since  $t \rightarrow -\infty$ ), and  $i_c(0^-) = 0$  (open circuit @ steady-state).




Equiv. Circuit @  $t = 0^-$

By voltage division  $V_{Req1} = V_c(0^-) = 30V \frac{15k\Omega}{30k\Omega + 15k\Omega} = \underline{10V}$

Capacitor Property  $\underline{V_c(0) = V_c(0^-) = 10V}$

ex. cont.Find  $V_c(\infty)$ 

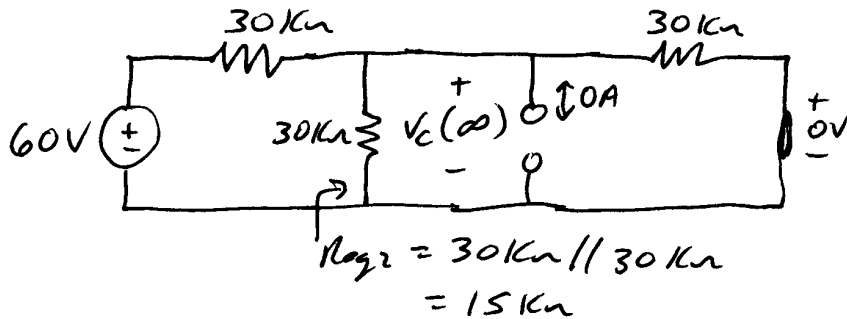→ As  $t \rightarrow \infty$ ,  $60u(t) V = 60V$  (has been on for all  $t > 0$ ),  
 $30u(-t) V = 0$  (short circuit), and  $i_c(\infty) = 0$   
 (capacitor is open circuit @ steady-state).




Equiv. circuit  
as  $t \rightarrow \infty$

By voltage division  $V_{Req2} = V_c(\infty) = 60V \frac{15k\Omega}{30k\Omega + 15k\Omega} = \underline{20V}$

Find  $R, C, \tau$  for  $t > 0$ 

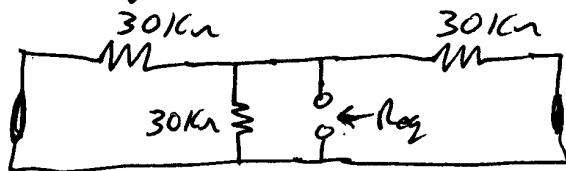→ set independent sources to zero & find  $R_{eq}$  looking into capacitor terminals



$R_{eq} = 30k\Omega \parallel 30k\Omega \parallel 30k\Omega$   
 $R_{eq} = 10k\Omega = R$

→  $C = 100 \mu F$  (No other capacitors)

→  $\tau = RC = 10 \times 10^3 (100 \times 10^{-6}) = 1 \text{ sec}$

Solution

$$V_c(t) = 20 + [10 - 20]e^{-t/\tau} \text{ V } t \geq 0$$

$$\underline{V_c(t) = 20 - 10e^{-t} \text{ V } t \geq 0}$$

ex. cont.

$$\begin{aligned}
 i_c(t) &= C \frac{dv_c}{dt} \\
 &= 100 \times 10^{-6} \frac{d(20 - 10e^{-t})}{dt} \\
 &= 100 \times 10^{-6} [0 - 10(-1)e^{-t}] \\
 &= 0.001 e^{-t} \text{ A}
 \end{aligned}$$

$$\underline{\underline{i_c(t) = 1 e^{-t} \text{ mA } t > 0}}$$

We do NOT know  $i_c(t=0)$ ; slope of  $v_c(t=0)$  unknown.

Bonus:  $v_c(t < 0) = v_c(0^-) = 10 \text{ V}$

$$i_c(t < 0) = C \frac{dv_c(t < 0)}{dt} = 0 \text{ (Steady-state)}$$

$$v_c(t) = \begin{cases} 10 \text{ V} & t \leq 0 \\ 20 - 10e^{-t} \text{ V} & t \geq 0 \end{cases}$$

$$i_c(t) = \begin{cases} 0 & t < 0 \\ ? & t = 0 \\ 1e^{-t} \text{ mA} & t > 0 \end{cases}$$

**ex. cont.** Plot  $i_C(t)$  and  $v_C(t)$ 

$$n := 0..349 \quad t_n := (n - 49) \cdot 0.01$$

$$IC1 := 0$$

$$VC1 := 10$$

$$IC2(t) := 1 \cdot e^{-t}$$

$$VC2(t) := 20 - 10 \cdot e^{-t}$$

$$i_{C_n} := \text{if}(t_n < 0, IC1, IC2(t_n))$$

$$v_{C_n} := \text{if}(t_n < 0, VC1, VC2(t_n))$$

