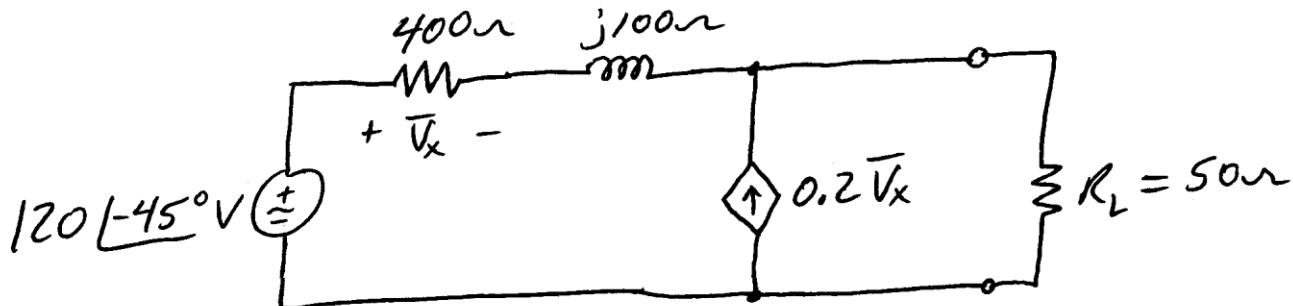


Ex. For the circuit shown, find the Thevenin and Norton Equivalent Circuits




Find \bar{Z}_T and \bar{Z}_N

→ Set independent voltage source to zero (short)

→ Replace load with $1L^{\circ}A$ test source

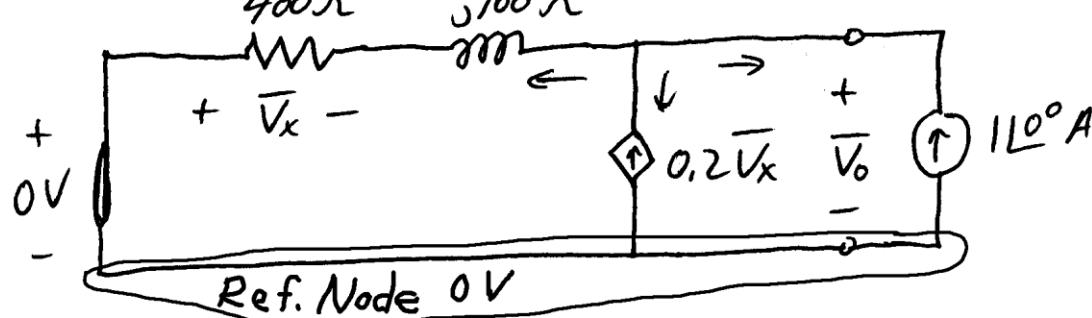→ Find \bar{V}_o , $\bar{Z}_T = \bar{Z}_N = \frac{\bar{V}_o}{1L^{\circ}A}$



$$\text{Apply KCL to top right node: } \frac{\bar{V}_o - 0}{400 + j100} - 0.2\bar{V}_x - 1L^{\circ} = 0$$


$$\text{By voltage division: } \bar{V}_x = \left(\frac{400}{400 + j100} \right) (0 - \bar{V}_o)$$

Substituting this into the KCL eqn yields:

$$\frac{\bar{V}_o}{400 + j100} + 0.2 \left(\frac{400}{400 + j100} \right) \bar{V}_o = 1L^{\circ}$$

$$\hookrightarrow \bar{V}_o = 4.9383 + j1.2346 \text{ V} \Rightarrow$$

$$\bar{Z}_T = \bar{Z}_N = \frac{\bar{V}_o}{1L^{\circ}} = \underline{4.9383 + j1.2346 \Omega}$$

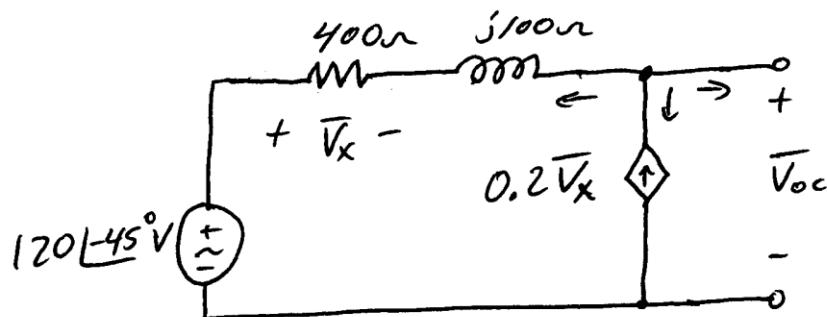Ex. contiFind \bar{V}_T \rightarrow Remove R_L & find $\bar{V}_{oc} = \bar{V}_T$ 

$$\text{Apply KCL to top right node : } \frac{\bar{V}_{oc} - 120\angle -45^\circ}{400 + j100} - 0.2\bar{V}_x + 0 = 0$$

$$\text{By voltage division : } \bar{V}_x = (120\angle -45^\circ - \bar{V}_{oc}) \frac{400}{400 + j100}$$

Substituting this into the KCL eq'n:

$$\frac{\bar{V}_{oc} - 120\angle -45^\circ}{400 + j100} - 0.2(120\angle -45^\circ - \bar{V}_{oc}) \frac{400}{400 + j100} = 0$$

$$\bar{V}_{oc} - 120\angle -45^\circ - 9600\angle -45^\circ + 80\bar{V}_{oc} = 0$$

$$\bar{V}_{oc} = \frac{9600\angle -45^\circ + 120\angle -45^\circ}{81} = \underline{120\angle -45^\circ V} = \underline{\bar{V}_T}$$


By source transformation:

$$\bar{I}_N = \frac{\bar{V}_T}{Z_T} = \frac{120\angle -45^\circ}{4.9383 + j1.2346}$$

$$\underline{\bar{I}_N = 23.574\angle -59.04^\circ A}$$

Ex. cont.

Thevenin Equivalent Circuit

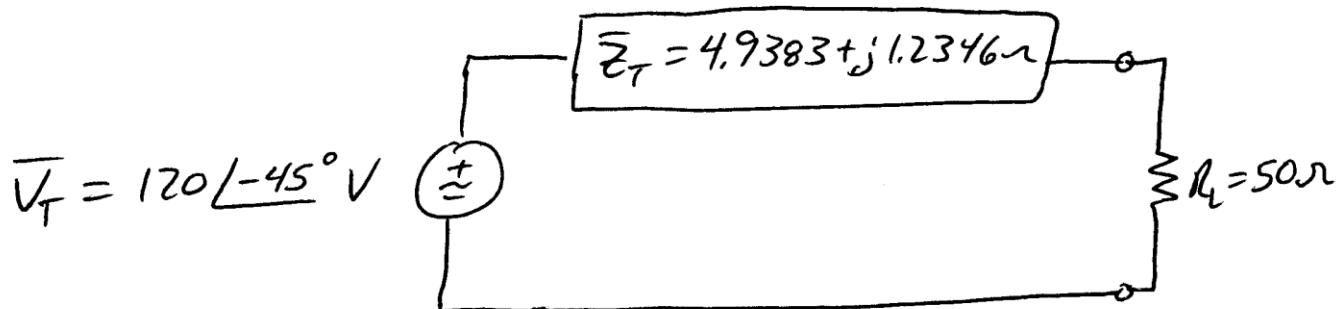

Norton Equivalent Circuit

