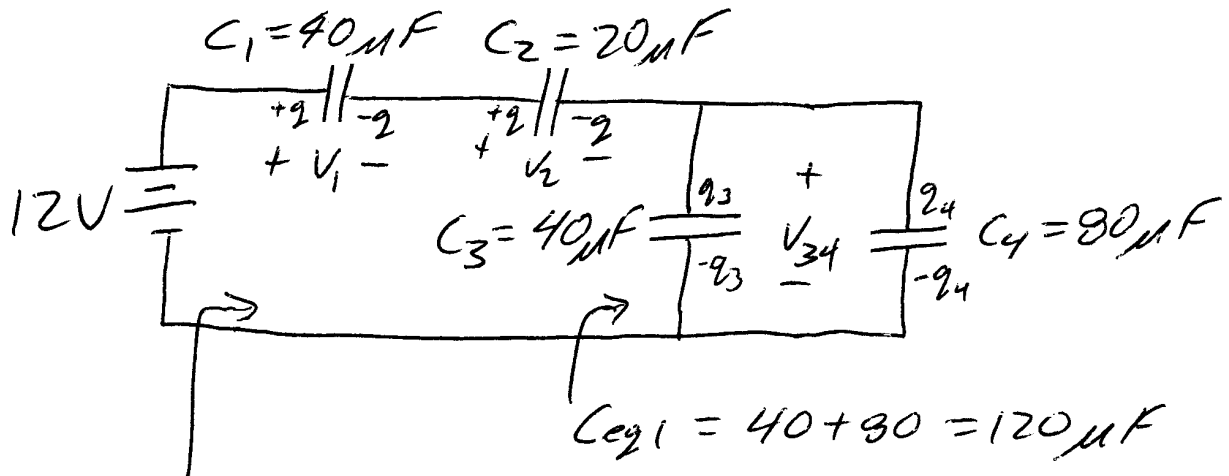


Example- Find the equivalent capacitance, voltage across, and charge stored by each capacitor.



$$C_{eq} = \left[\frac{1}{40} + \frac{1}{20} + \frac{1}{120} \right]^{-1} = 12 \mu\text{F}$$

$$12\text{V} \equiv \boxed{\begin{matrix} +2 \\ -2 \end{matrix}} C_{eq} = 12 \mu\text{F} \quad q = C_{eq}(12\text{V}) = 144 \mu\text{C}$$

$$V_1 = V_s \frac{C_{eq}}{C_1} = 12 \frac{12 \mu\text{F}}{40 \mu\text{F}} = \underline{3.6\text{V}}$$

$$q_1 = C_1 V_1 = 40 \mu\text{F} (3.6\text{V}) = \underline{144 \mu\text{C}}$$

$$V_2 = 12 \frac{12}{20} = \underline{7.2\text{V}}$$

$$q_2 = C_2 V_2 = 20 \mu\text{F} (7.2\text{V}) = \underline{144 \mu\text{C}}$$

$$V_{34} = 12 \frac{12}{120} = \underline{1.2\text{V}}$$

$$q_3 = C_3 V_{34} = (40 \mu\text{F})(1.2\text{V}) = \underline{48 \mu\text{C}}$$

$$q_4 = C_4 V_{34} = (80 \mu\text{F})(1.2\text{V}) = \underline{96 \mu\text{C}}$$

Note: $q_3 + q_4 = 48 + 96 = \underline{144 \mu\text{C}} = q!$