
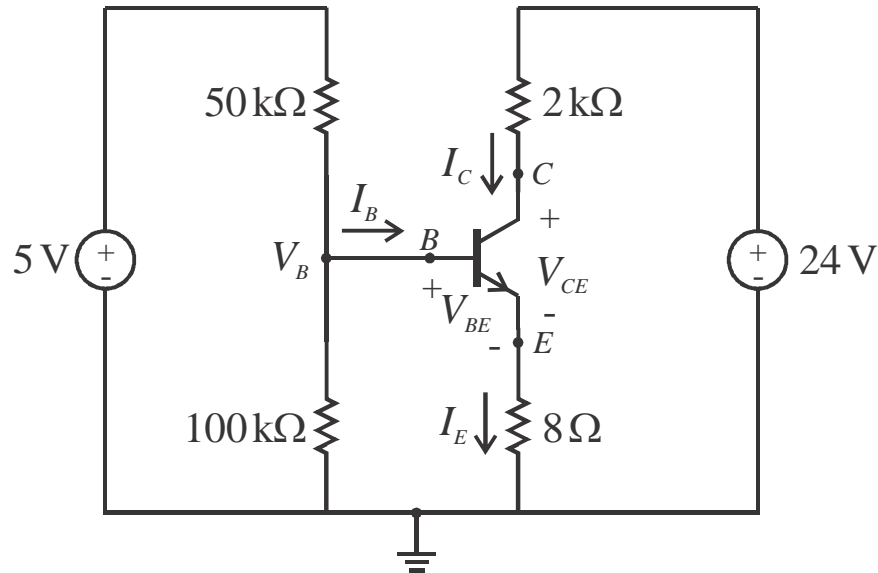


Example-

Given that $\beta = 100$ and $V_{BE} = 0.7 \text{ V}$, find V_{CE} , V_B , V_E , V_C , I_B , I_C , and I_E .

Mesh Analysis

Redraw circuit and assign mesh currents.

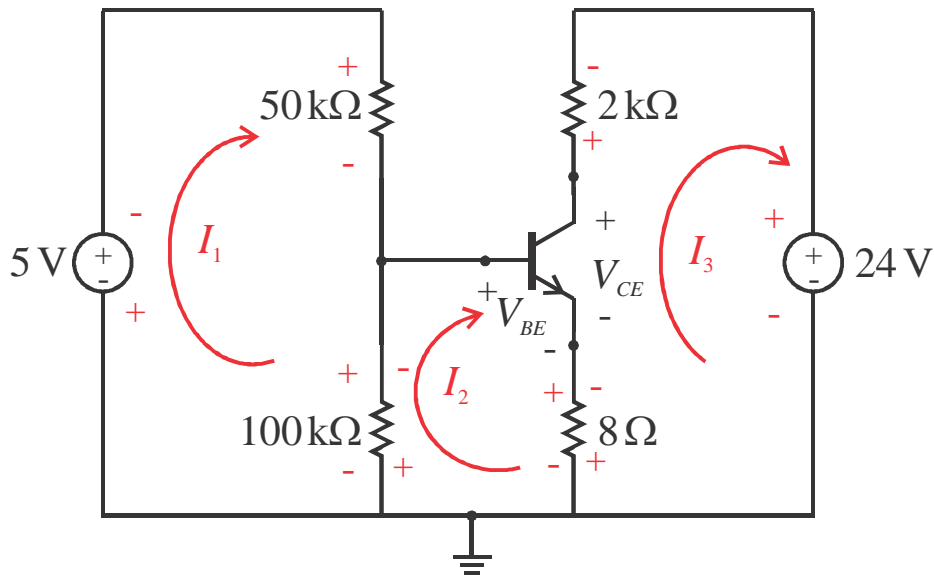

$$\text{Mesh 1: } -5 + 50 \times 10^3 I_1 + 100 \times 10^3 (I_1 - I_2) = 0$$

$$\text{Mesh 2: } 100 \times 10^3 (I_2 - I_1) + V_{BE}^{0.7} + \beta (I_2 - I_3) = 0$$

$$\text{Mesh 3: } 8 (I_3 - I_2) - V_{CE} + 2000 I_3 + 24 = 0$$

Simplify equations

$$[50 \times 10^3 + 100 \times 10^3] I_1 + (-100 \times 10^3) I_2 + (0) I_3 = 5$$

$$(-100 \times 10^3) I_1 + [100 \times 10^3 + 8] I_2 + (-8) I_3 = -0.7$$

$$(0) I_1 + (-8) I_2 + [2000 + 8] I_3 + (-1) V_{CE} = -24$$

\Rightarrow 3 equations + 4 unknowns ($I_1, I_2, I_3, + V_{CE}$)

How do we simplify?

* Note (from circuit drawing): $I_2 = I_B \leftarrow \text{Sub \#1}$
 $I_3 = -I_C$

* Now, for BJT transistors, we know that

$$I_C = \beta I_B = 100 I_B \xrightarrow{\text{use \#1}} I_3 = -100 I_B \leftarrow \text{Sub \#2}$$

Using substitution #2 in the above equations leads to -

$$(150 \times 10^3) I_1 + (-100 \times 10^3) I_B + (0) V_{CE} = 5$$

$$(-100 \times 10^3) I_1 + [100 \times 10^3 + 8 + 8(100)] I_B + (0) V_{CE} = -0.7$$

$$(0) I_1 + [-8 - 2008(100)] I_B + (-1) V_{CE} = -24$$

\Rightarrow 3 equations + 3 unknowns

\Downarrow solve using TI-68

$$\underline{\underline{I_1 = 84.754 \mu A}}$$

$$\underline{\underline{I_B = 77.13 \mu A}}$$

$$\underline{\underline{V_{CE} = 8.5116 V}}$$

Using these currents and voltage -

$$I_C = 100 I_B = \underline{\underline{7.713 mA}}$$

By KCL, $I_E = I_C + I_B = 7.713 \times 10^{-3} + 77.13 \times 10^{-6}$

$$\underline{\underline{I_E = 7.79 mA}}$$

By Ohm's Law, $V_E = I_E (8) = 7.79 \times 10^{-3} (8)$

$$\underline{\underline{V_E = 0.06232 V = 62.32 mV}}$$

By Ohm's Law, $V_B = V_{100k\Omega} = (I_1 - \overset{I_B}{I_2}) 100 \times 10^3$
 $= (84.754 \times 10^{-6} - 77.13 \times 10^{-6}) 100 \times 10^3$


$$\underline{\underline{V_B = 0.7624 V}}$$

By KVL, $V_C = V_E + V_{CE} = 0.06232 + 8.5116$

$$\underline{\underline{V_C = 8.5739 V}}$$

Nodal Analysis

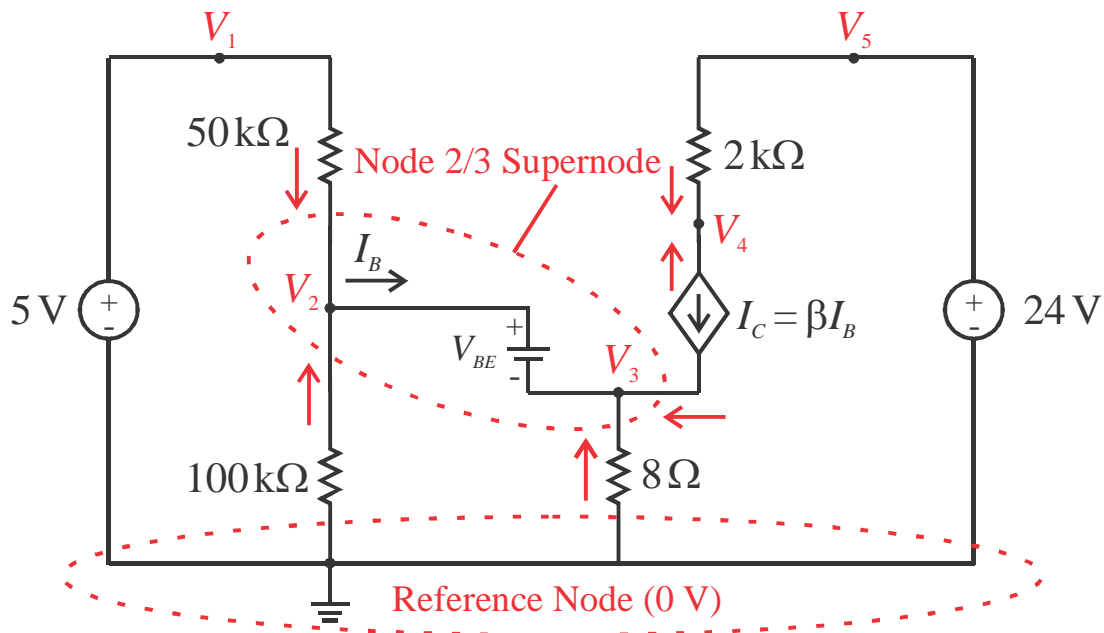Redraw circuit, using first-order circuit model of BJT transistor, and assign node voltages.



$$\text{Node 1: } V_1 = 5V$$

$$\text{Node 2/3 Aux. Eq'n: } V_2 - V_3 = V_{BE} = 0.7$$

$$\text{Node 2/3 Supernode: } \overset{5}{\uparrow} \frac{V_1 - V_2}{50 \times 10^3} + \frac{0 - V_2}{100 \times 10^3} + \frac{0 - V_3}{8} + \overset{\beta=100}{\downarrow} \beta I_B = 0$$

$$\text{Node 4: } -\overset{100}{\uparrow} \beta I_B + \overset{24}{\rightarrow} \frac{V_5 - V_4}{2000} = 0$$

$$\text{Node 5: } V_5 = 24V$$

\Rightarrow 4 unknowns ($V_2, V_3, I_B, + V_4$) + 3 equations

Can we determine I_B in terms of the node voltages?

Using KCL @ node 2,

$$I_B = \frac{0 - V_2}{100 \times 10^3} + \frac{V_1 - V_2}{50 \times 10^3}$$

At this point, we could substitute the above equation for I_B into the node equations to get 3 equations - 3 unknowns OR use the above equation and have 4 equations - 4 unknowns (less likely to make an error) \rightarrow gather up terms + coefficients

$$\rightarrow (1)V_2 + (-1)V_3 + (0)V_4 + (0)I_B = 0.7$$

$$\left[\frac{-1}{50 \times 10^3} + \frac{-1}{100 \times 10^3} \right] V_2 + \left(\frac{-1}{8} \right) V_3 + (0)V_4 + (100)I_B = \frac{-5}{50 \times 10^3}$$

$$(0)V_2 + (0)V_3 + \left(\frac{-1}{2000} \right) V_4 + (-100)I_B = \frac{-24}{2000}$$

$$\left[\frac{-1}{50 \times 10^3} + \frac{-1}{100 \times 10^3} \right] V_2 + (0)V_3 + (0)V_4 + (-1)I_B = \frac{-5}{50 \times 10^3}$$

\Downarrow solve using TI-68

$$\underline{\underline{V_2 = V_B = 0.76232V}}$$

$$\underline{\underline{V_3 = V_E = 0.06232V = 62.32mV}}$$

$$\underline{\underline{V_4 = V_C = 8.5739V}}$$

$$\underline{\underline{I_B = 77.13\mu A}}$$

$$V_{CE} = V_C - V_E = \underline{\underline{8.5116V}}$$

$$I_E = \frac{V_3 - 0}{8} = \underline{\underline{7.79mA}}$$

} Same answers!