


EE 220/220L Circuits I Examination 1

Name _____

Example

Instructions: Show all work for full credit. Write answers in indicated places.

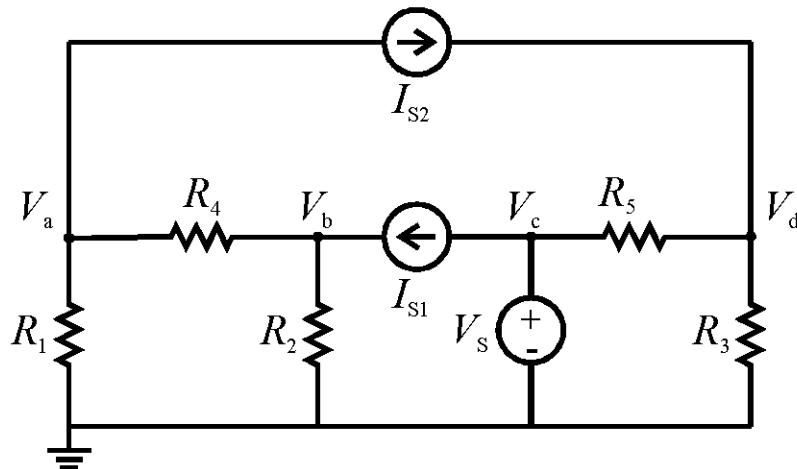- 1) For the circuit shown, $R_1 = R_2 = 800 \Omega$, $R_3 = R_4 = 500 \Omega$, $R_5 = 400 \Omega$, $V_S = 26 \text{ V}$, $I_{S1} = 16 \text{ mA}$, and $I_{S2} = 24 \text{ mA}$. Using **nodal analysis**, write the node equations for nodes a-d below in the boxes below (Do NOT simplify). Then, solve for the node voltages.



Node a:


Node b:

Node c:

Node d:

$$V_a = \underline{-7.01 \text{ V}} \quad V_b = \underline{0.61 \text{ V}} \quad V_c = \underline{26 \text{ V}} \quad V_d = \underline{19.78 \text{ V}}$$

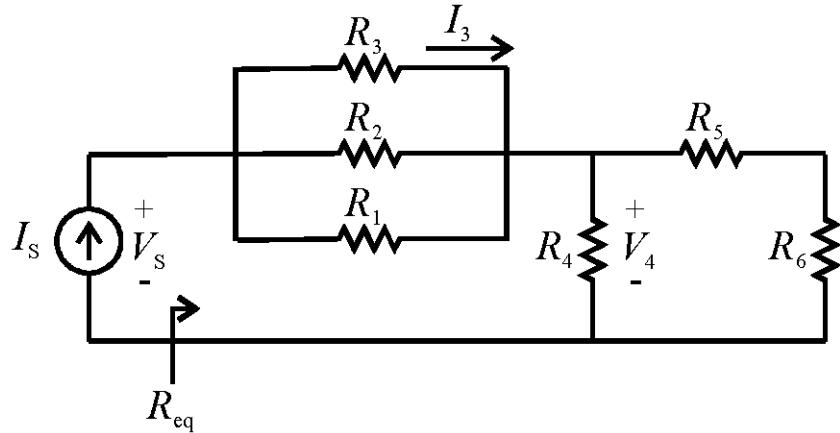
- 2) For the circuit shown, determine the total number of branches b , nodes n , and independent loops l . Then, use circuit reduction techniques (e.g., series resistance rule, current &/or voltage division ...) to find R_{eq} , V_S , I_3 , and V_4 . Given: $I_S = 40 \text{ mA}$, $R_1 = R_4 = 1.5 \text{ k}\Omega$, $R_2 = R_6 = 800 \Omega$, $R_3 = R_5 = 1.2 \text{ k}\Omega$. Show work for partial credit!



$$b = \underline{\hspace{2cm} 7 \hspace{2cm}} \quad n = \underline{\hspace{2cm} 4 \hspace{2cm}} \quad l = \underline{\hspace{2cm} 4 \hspace{2cm}}$$

$$R_{\text{eq}} = \underline{\hspace{2cm} 1220.8 \Omega \hspace{2cm}} \quad V_S = \underline{\hspace{2cm} 48.83 \text{ V} \hspace{2cm}} \quad I_3 = \underline{\hspace{2cm} 12.12 \text{ mA} \hspace{2cm}} \quad V_4 = \underline{\hspace{2cm} 34.286 \text{ V} \hspace{2cm}}$$

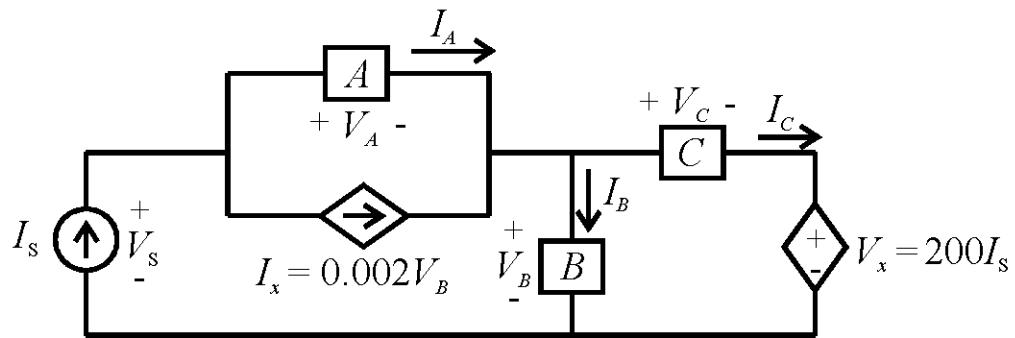
- 3) For the circuit shown, $I_S = 25 \text{ mA}$, $V_A = 7 \text{ V}$, $V_B = 18 \text{ V}$, and $I_B = 12 \text{ mA}$. Determine the voltages V_C , V_S & V_x , and currents I_A , I_C & I_x . Calculate the power absorbed by elements A and C.



$$V_C = \underline{13 \text{ V}} \quad V_S = \underline{25 \text{ V}} \quad V_x = \underline{5 \text{ V}} \quad P_A = \underline{-77 \text{ mW}}$$

$$I_A = \underline{-11 \text{ mA}} \quad I_C = \underline{13 \text{ mA}} \quad I_x = \underline{36 \text{ mA}} \quad P_C = \underline{169 \text{ mW}}$$

- 4) Using **mesh analysis** techniques, write the mesh equations (in the boxes below) required to determine the mesh currents I_1, I_2, I_3 , and I_4 when $R_1 = R_3 = 80 \Omega$, $R_2 = R_4 = 50 \Omega$, $R_5 = R_6 = 40 \Omega$, $V_S = 26 \text{ V}$, $I_{S1} = 160 \text{ mA}$, and $I_{S2} = 240 \text{ mA}$. Use given values in equations and do NOT simplify. Indicate perimeter(s) of supermeshes with dashed line(s).

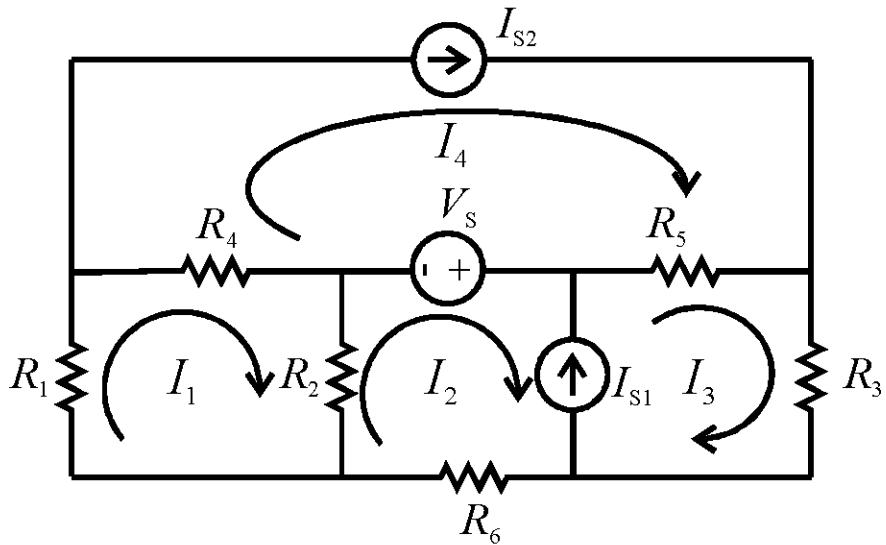

Mesh 1

2/3 Supermesh

2/3 Aux. eq'n

Mesh 4