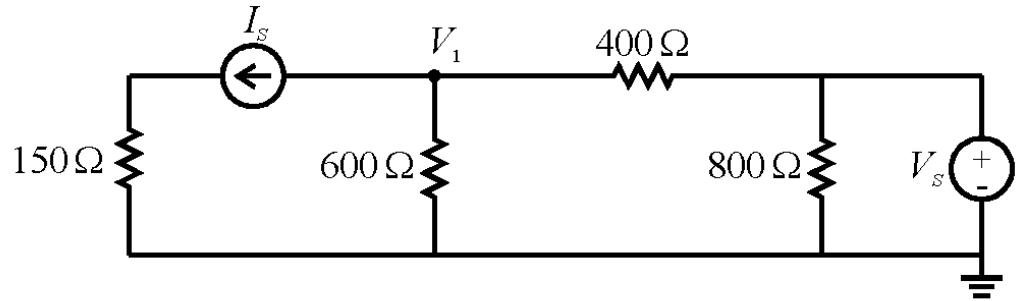


EE 220/220L Circuits I (Spring 2011) Examination 2

Name _____ Example


Instructions: Show all work for full credit. Write answers in indicated places. Attach equation sheet.

- 1) For the circuit shown, determine the node voltage V_1 due to each source and overall using the **Principle of Superposition** when $I_S = 44 \text{ mA}$ and $V_S = 14 \text{ V}$.





$$V_{1,I_S} = \underline{-10.56 \text{ V}} \quad V_{1,V_S} = \underline{8.4 \text{ V}} \quad V_1 = \underline{-2.16 \text{ V}}$$

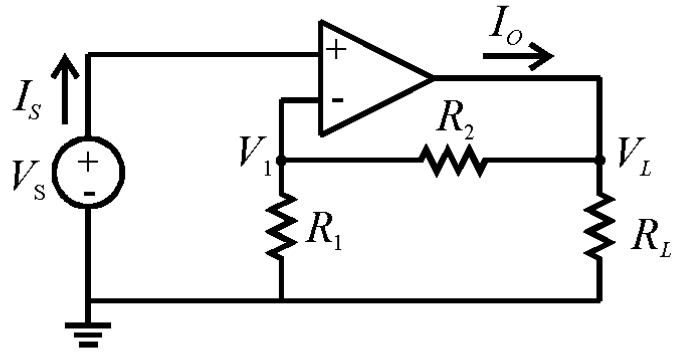- 2) For the circuit, the operational amplifier has an open-loop gain of 4×10^4 , input resistance of $1 \text{ M}\Omega$, and output resistance of 100Ω . When $V_S = 2 \text{ V}$, $R_1 = 10 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, and $R_L = 5 \text{ k}\Omega$, find I_S , V_1 , V_L , and I_O (keep at least 6 significant figures). Show clearly labeled work for partial credit!




$$I_S = \underline{0.153488 \text{ nA}} \quad V_1 = \underline{1.99985 \text{ V}} \quad V_L = \underline{5.99954 \text{ V}} \quad I_O = \underline{1.399835 \text{ mA}}$$

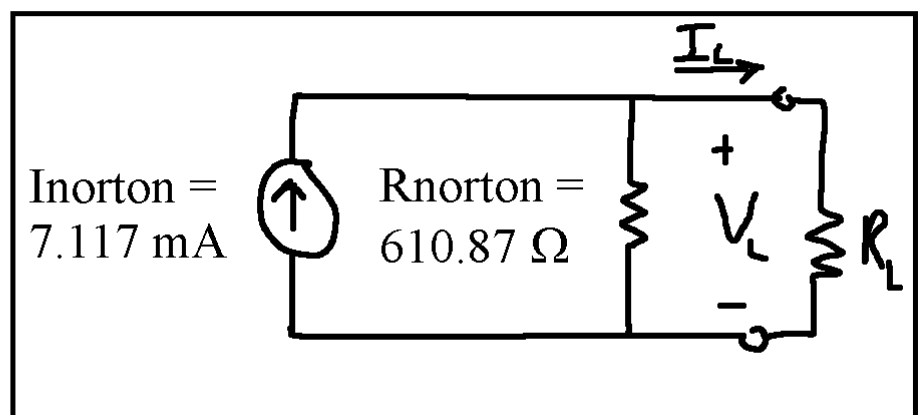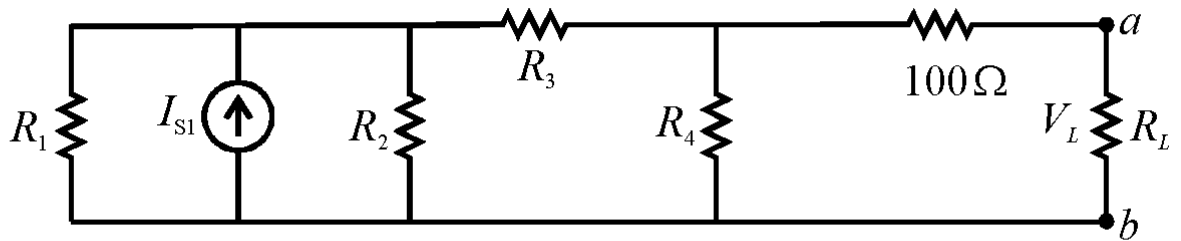- 3) For the circuit shown, find and sketch a fully-labeled Norton equivalent circuit at terminals $a-b$ when $I_{S1} = 20 \text{ mA}$, $R_1 = R_4 = 1 \text{ k}\Omega$, $R_2 = 800 \Omega$, and $R_3 = 600 \Omega$. Then, determine the resistance R_L for maximum power transfer, and find the load voltage V_L and load power P_L .



$$R_L = \underline{610.87 \Omega} \quad V_L = \underline{2.1739 \text{ V}} \quad P_L = \underline{7.736 \text{ mW}}$$

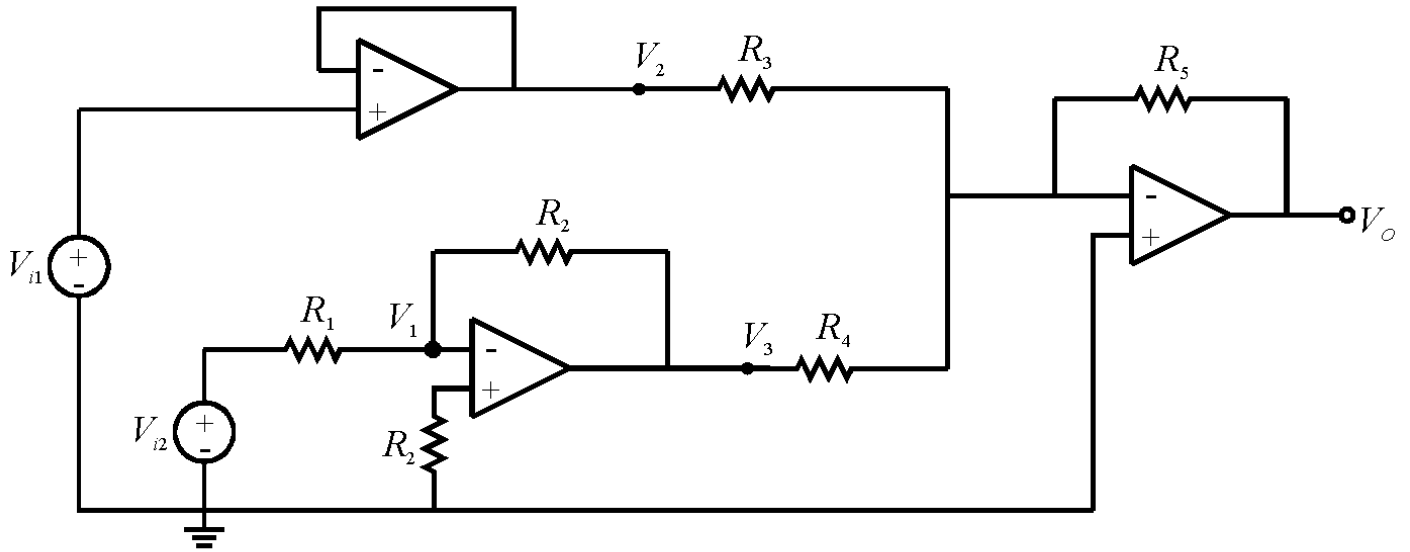- 4) Determine the voltages V_1 , V_2 , V_3 , and V_O in the ideal operational amplifier circuit shown below when $V_{i1} = 2$ V, $V_{i2} = -4$ V, $R_1 = 10$ k Ω , $R_2 = 20$ k Ω , $R_3 = 4$ k Ω , $R_4 = 8$ k Ω , and $R_5 = 16$ k Ω .



$$V_1 = \underline{0 \text{ V}}$$

$$V_2 = \underline{2 \text{ V}}$$

$$V_3 = \underline{8 \text{ V}}$$

$$V_O = \underline{-24 \text{ V}}$$