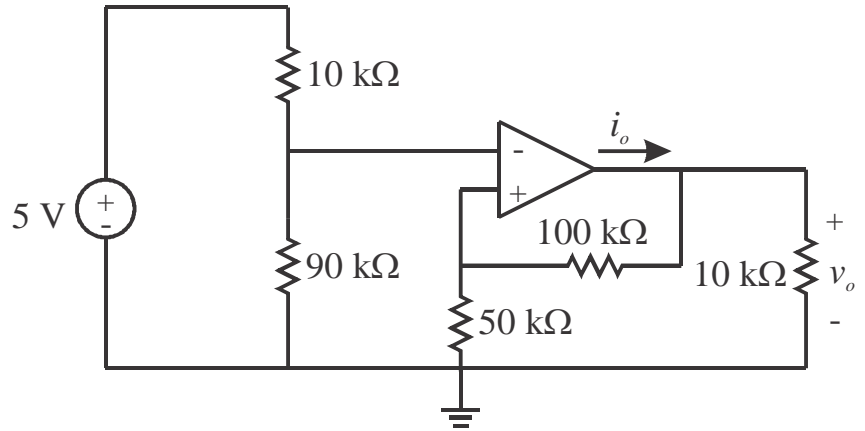


# EE 220/220L Circuits I Final Examination example problems

Name \_\_\_\_\_


**Instructions:** Show all work for full credit. Write answers in indicated places. Put all phasors in polar form with angle in degrees. Put all admittances and impedances in rectangular form.

1) For the ideal op-amp circuit shown, find  $v_o$  and  $i_o$ .




$v_o =$  13.5 V       $i_o =$  1.44 mA

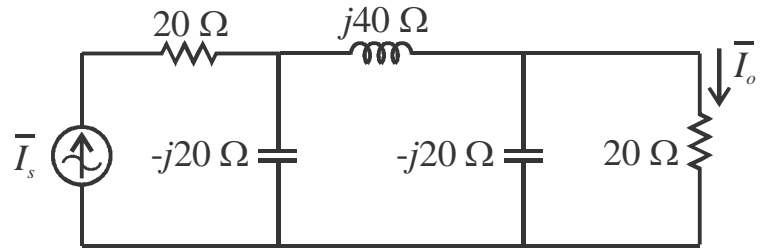2) Given  $\bar{I}_s = 0.5\angle 0^\circ$  A, find the impedance seen by the source and the phasor current  $\bar{I}_o$ .



$$\bar{Z}_{eq} = \underline{\underline{40 - j40 \Omega}} \quad \bar{I}_o = \underline{\underline{500\angle 180^\circ \text{ mA}}}$$

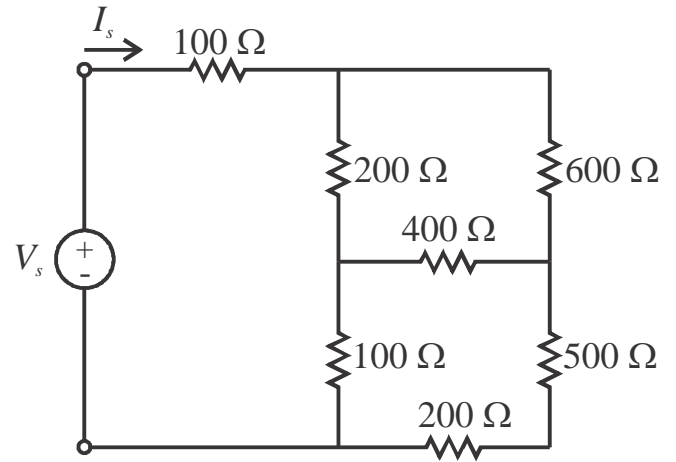
3) Calculate the equivalent resistance  $R_{eq}$  seen by the source and source current  $I_s$ , when  $V_s = 24$  V.



$$R_{eq} = \underline{\underline{340.625 \Omega}}$$

$$I_s = \underline{\underline{70.46 \text{ mA}}}$$

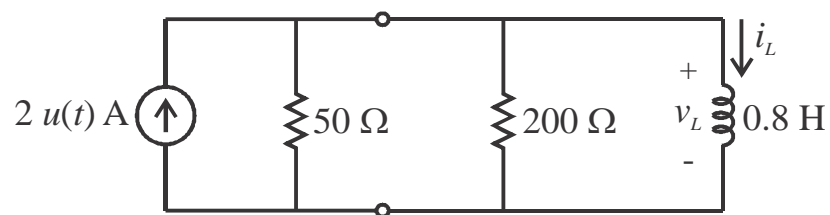
4) Find  $i_L(t)$  and  $v_L(t)$  for  $t > 0$ .



$$i_L(t) = \underline{2 - 2e^{-50t} \text{ A } t > 0}$$


$$v_L(t) = \underline{80e^{-50t} \text{ V } t > 0}$$

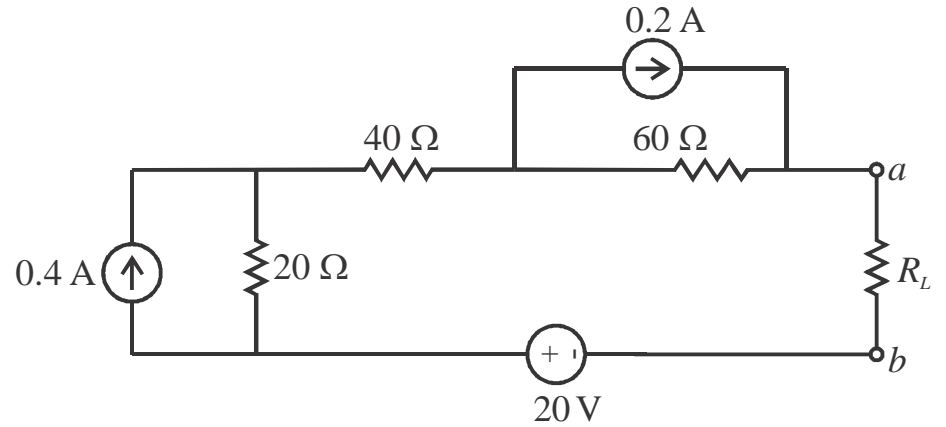- 5) Find the Thevenin equivalent circuit for the circuit shown. Then, determine the load resistance  $R_{L,\max}$  for maximum power delivered and the maximum load power  $P_{L,\max}$ .




$$V_T = \underline{40 \text{ V}} \quad R_T = \underline{120 \Omega} \quad R_{L,\max} = \underline{120 \Omega} \quad P_{L,\max} = \underline{3.33 \text{ W}}$$

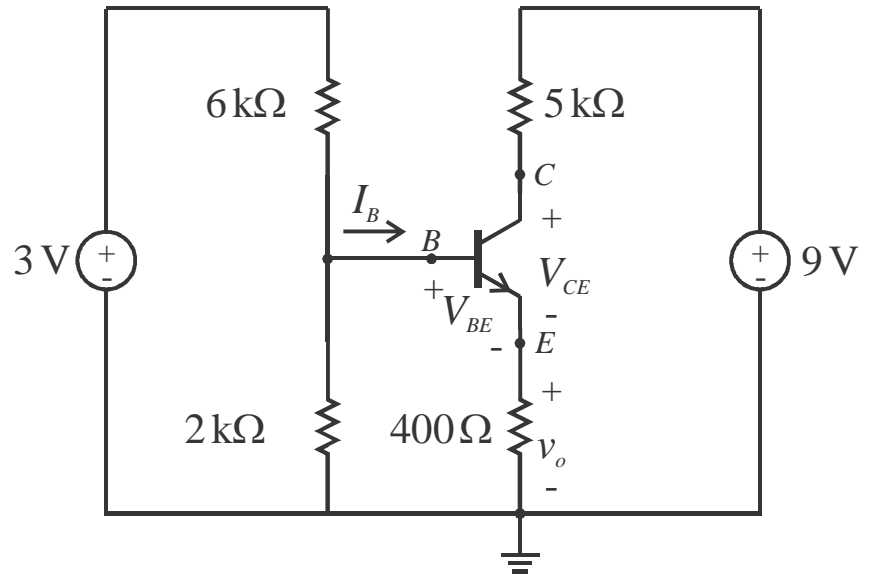- 6) For the npn DC transistor circuit shown, find  $I_B$ ,  $V_{CE}$ , and  $v_o$  **using mesh analysis** when  $\beta = 200$  and  $V_{BE} = 0.7$  V.




$$I_B = \underline{\underline{610.5 \text{ nA}}} \quad V_{CE} = \underline{\underline{8.34 \text{ V}}} \quad v_o = \underline{\underline{49.08 \text{ mV}}}$$

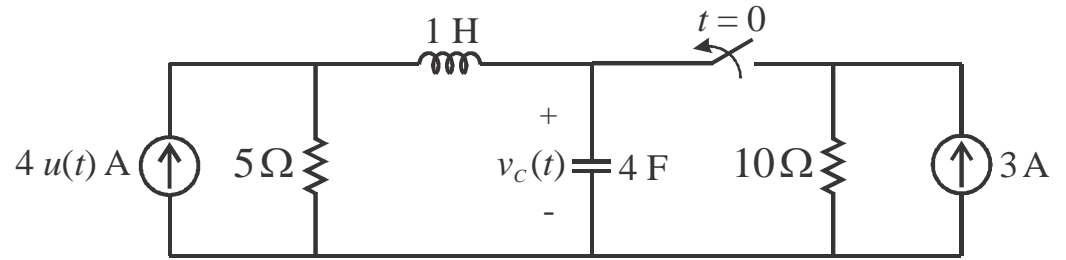7) For the circuit shown, the switch **opens** at  $t = 0$  after being closed for a long time. Find  $v_C(t)$  for  $t > 0$ .



$$v_C(t) = \underline{\underline{20 - 10.205 e^{-0.0505t} + 0.205 e^{-4.9495t} \text{ V} \quad t > 0}}$$

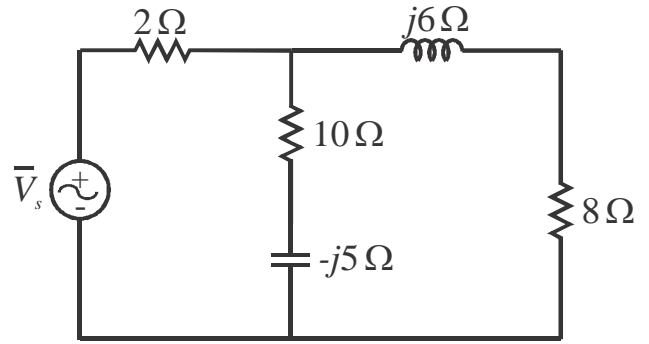- 8) Given  $\bar{V}_s = 16\angle 45^\circ \text{ V}_{\text{rms}}$ , find the power factor  $pf$ , average  $P_{\text{ave}}$ , reactive  $Q$ , apparent  $S$ , & complex  $\bar{S}$  powers delivered by the source.




$$pf = \underline{0.9956 \text{ lagging}} \quad P_{\text{ave}} = \underline{31.119 \text{ W}} \quad Q = \underline{2.936 \text{ VAR}}$$

$$S = \underline{31.257 \text{ VA}} \quad \bar{S} = \underline{31.119 + j 2.936 \text{ VA}}$$



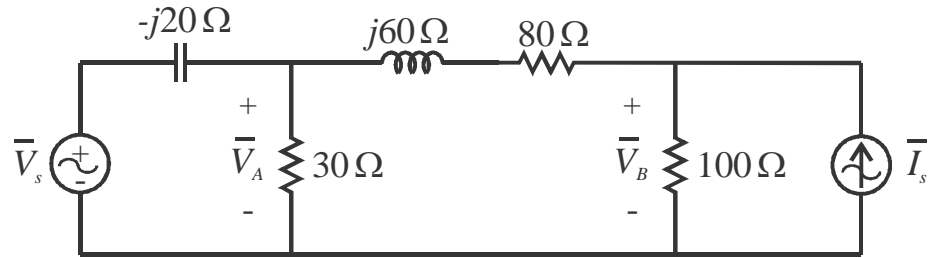- 9) For the circuit shown, use **nodal analysis** to find the labeled phasor voltages when  $\bar{V}_s = 4\angle 30^\circ \text{ V}$  and  $\bar{I}_s = 0.5\angle 0^\circ \text{ A}$ .



$$\underline{\bar{V}_A = 2.835\angle -20.65^\circ \text{ V}}$$

$$\underline{\bar{V}_B = 27.18\angle 15.78^\circ \text{ V}}$$