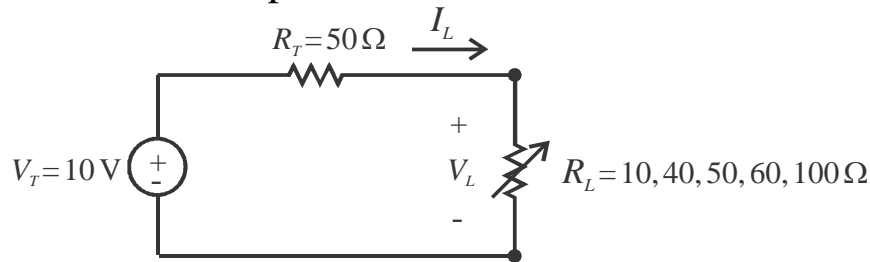


**Example-** Look at maximum power transfer for the circuit below.



$$\underline{R_L = 10 \Omega}$$

$$I_L = \frac{V_T}{R_T + R_L} = \frac{10\text{V}}{50 \Omega + 10 \Omega} = 166.\bar{6} \text{ mA},$$

$$V_L = V_T \frac{R_L}{R_T + R_L} = I_L R_L = 10\text{V} \left( \frac{10 \Omega}{50 \Omega + 10 \Omega} \right) = 1.\bar{6} \text{ V}$$

$$P_L = V_L I_L = (1.\bar{6} \text{ V})(166.\bar{6} \text{ mA}) = \underline{277.\bar{7} \text{ mW}}$$

$$P_{RT} = I_L^2 R_T = (0.166\bar{6} \text{ A})^2 50 = \underline{1388.\bar{8} \text{ mW}}$$

$$\underline{R_L = 40 \Omega}$$

$$I_L = \frac{V_T}{R_T + R_L} = \frac{10\text{V}}{50 \Omega + 40 \Omega} = 111.\bar{1} \text{ mA},$$

$$V_L = I_L R_L = (0.\bar{1} \text{ A})(40 \Omega) = 4.\bar{4} \text{ V}$$

$$P_L = V_L I_L = (4.\bar{4} \text{ V})(111.\bar{1} \text{ mA}) = \underline{493.83 \text{ mW}}$$

$$P_{RT} = I_L^2 R_T = (0.\bar{1} \text{ A})^2 50 = \underline{617.284 \text{ mW}}$$

$$\underline{R_{L,\max} = R_T = 50 \Omega}$$

$$I_L = \frac{V_T}{R_T + R_L} = \frac{10\text{V}}{50 \Omega + 50 \Omega} = 100 \text{ mA},$$

$$V_L = I_L R_L = (0.1 \text{ A})(50 \Omega) = 5 \text{ V}$$

$$P_{L,\max} = V_L I_L = (5\text{V})(100 \text{ mA}) = \underline{500 \text{ mW}}$$

$$P_{RT} = I_L^2 R_T = (0.1 \text{ A})^2 50 = \underline{500 \text{ mW}}$$

$$\underline{R_L = 60 \Omega}$$

$$I_L = \frac{V_T}{R_T + R_L} = \frac{10\text{V}}{50 \Omega + 60 \Omega} = 90.\bar{90} \text{ mA},$$

$$V_L = I_L R_L = (0.090 \text{ A})(50 \Omega) = 5.\bar{45} \text{ V}$$

$$P_L = V_L I_L = (5.\bar{45} \text{ V})(90.\bar{90} \text{ mA}) = \underline{495.87 \text{ mW}}$$

$$P_{RT} = I_L^2 R_T = (0.090 \text{ A})^2 50 = \underline{413.22 \text{ mW}}$$

$$\underline{R_L = 100 \Omega}$$


$$I_L = \frac{V_T}{R_T + R_L} = \frac{10\text{V}}{50 \Omega + 100 \Omega} = 66.\bar{6} \text{ mA},$$

$$V_L = I_L R_L = (0.06\bar{6} \text{ A})(100 \Omega) = 6.\bar{6} \text{ V}$$

$$P_L = V_L I_L = (6.\bar{6} \text{ V})(66.\bar{6} \text{ mA}) = \underline{444.\bar{4} \text{ mW}}$$

$$P_{RT} = I_L^2 R_T = (0.06\bar{6} \text{ A})^2 50 = \underline{222.\bar{2} \text{ mW}}$$

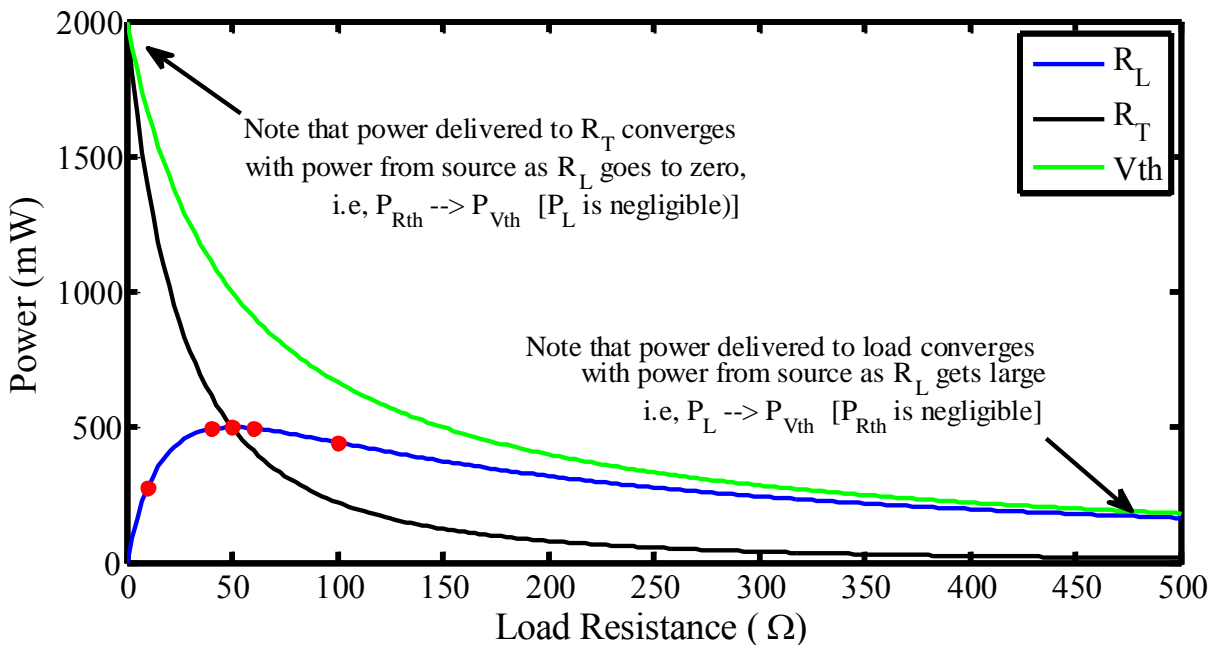**Note:** As  $R_L$  increased,  $I_L$  decreased, and  $V_L$  increased.



```
% max_power_transfer.m
% EE 220L
% Dr. Thomas P. Montoya
% Generate plot of load power vs. load resistance
%
clear;clc;close all;
Rth = 50; % Thevenin equivalent resistance
Vth = 10; % Thevenin equivalent voltage
RLex = [10,40,50,60,100]; % example resistance
PLex = [277.78,493.83,500,495.87,444.44]; % example power
RL = 0:2.5:500;
IL = Vth./(Rth + RL);
PL1 = 1000*IL.*IL.*RL;
PRth = 1000*IL.*IL.*Rth;
PVth = Vth.*IL*1000;
Perc_pwr_del = 100*PL./PVth;
plot(RL,PL1,'b-',RL,PRth,'k-',RL,PVth,'g-',RLex,PLex,'r. ');
legend('R_L','R_T','Vth');
ylabel('Power (mW)','fontsize',16,'fontname','times')
xlabel('Load Resistance (\Omega)','fontsize',16,'fontname','times')
set(findobj('type','axes'),'fontname','times','fontsize',14)
set(findobj('type','line'),'linewidth',2)
set(findobj('type','line'),'markersize',20)
set(findobj('type','axes'),'linewidth',2.5)
```