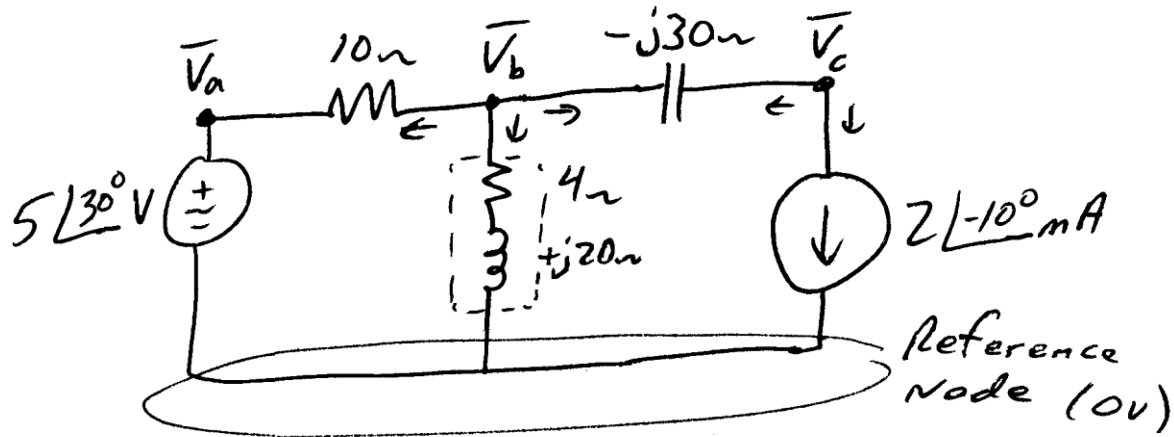


Ex. Determine the labeled phasor node voltages.



$$\text{Node a: } \bar{V}_a = 5 \angle 30^\circ \text{ V}$$

$$\text{Node b: } \frac{\bar{V}_b - \bar{V}_a}{10} + \frac{\bar{V}_b - 0}{4 + j20} + \frac{\bar{V}_b - \bar{V}_c}{-j30} = 0$$

$$\text{Node c: } \frac{\bar{V}_c - \bar{V}_b}{-j30} + 2 \angle -10^\circ \text{ mA} = 0$$

$$\left( \frac{1}{10} + \frac{1}{4 + j20} + \frac{1}{-j30} \right) \bar{V}_b + \left( \frac{-1}{-j30} \right) \bar{V}_c = \frac{5 \angle 30^\circ}{10}$$

$$\left( \frac{-1}{-j30} \right) \bar{V}_b + \left( \frac{-1}{-j30} \right) \bar{V}_c = -2 \times 10^{-3} \angle -10^\circ$$

$$\hookrightarrow \bar{V}_b = 2.4578 + j3.36186 \text{ V} = 4.1645 \angle 53.83^\circ \text{ V}$$

$$\bar{V}_c = 2.4682 + j3.42095 = 4.2184 \angle 54.190^\circ \text{ V}$$

$$\text{Check } \frac{\bar{V}_b - \bar{V}_c}{-j30} = 2.00 \angle -9.95^\circ \text{ mA}$$

$$\approx 2 \angle -10^\circ \text{ mA}$$

Illustrates the need to carry more significant digits w/ complex #'s