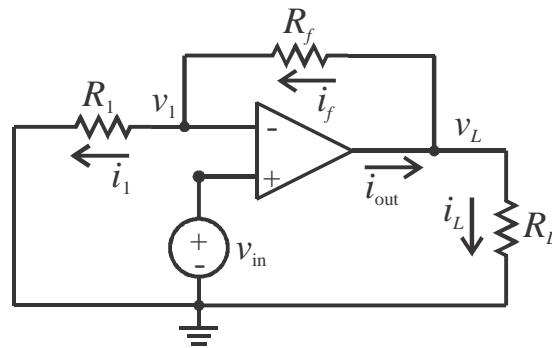


Design a non-inverting amplifier to supply a 1 kΩ load with 10 V when 1 V is input while ensuring $i_{out} < 18$ mA. Then, determine all labeled currents and voltages when 1 V is input.



Non-inverting Amplifier

- Using (5.11), $v_L = v_o = \left(1 + \frac{R_f}{R_1}\right)v_i$ and the requirement that the output be 10 V when the input is 1 V, we get

$$A_v = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_1} = \frac{10\text{ V}}{1\text{ V}} = 10 \Rightarrow \frac{R_f}{R_1} = 9.$$


- When the output is 10 V and given that the load is 1 kΩ, the load current is

$$i_L = \frac{v_L}{R_L} = \frac{10}{1000} = 10 \text{ mA}.$$

- Using KCL at the output node and applying the requirement that $i_{out} < 18$ mA, we find that

$$i_{out} = i_f + i_L \Rightarrow i_f \leq 18 - 10 = 8 \text{ mA}.$$

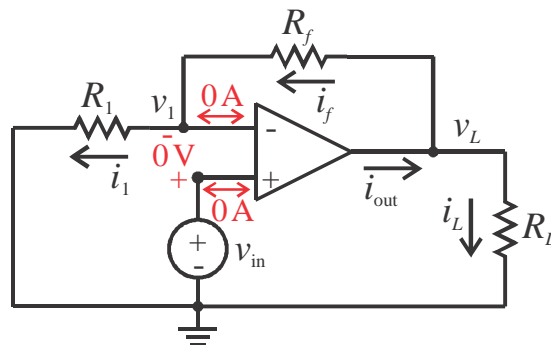
- Applying the ideal op-amp assumptions (see circuit below), $v_{in} = v_1 = 1\text{ V}$.



- Then, by Ohm's Law

$$i_f = \frac{v_L - v_1}{R_f} = \frac{10 - 1}{R_f} \leq 8 \text{ mA} \Rightarrow R_f \geq 1125 \Omega$$

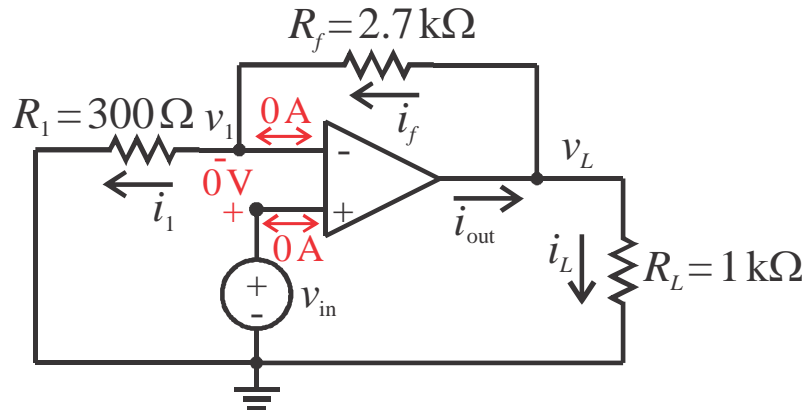- With the above information in mind and looking at the available leaded resistors in EP 336, **select** $R_f = 2.7 \text{ k}\Omega$ and $R_1 = 300 \Omega$. This yields the circuit



Now, we can calculate all the currents and voltages for our non-inverting amplifier design when the input is 1 V.

Check gain-

$$A_v = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_1} = 1 + \frac{2700}{300} = \underline{10}.$$

Given $v_i = v_{in} = 1 \text{ V}$ -

$$v_o = A_v v_i = 10(1 \text{ V}) \Rightarrow v_o = \underline{v_L = 10 \text{ V}}$$

By ideal op-amp assumption-

$$v_{in} = \underline{v_1 = 1 \text{ V}}$$

Using Ohm's Law-

$$i_L = \frac{v_L}{R_L} = \frac{10 \text{ V}}{1000 \Omega} \Rightarrow \underline{i_L = 10 \text{ mA}}$$

$$i_f = \frac{v_L - v_1}{R_f} = \frac{10 - 1}{2700} \Rightarrow \underline{i_f = 3.3 \text{ mA}}$$

$$i_1 = \frac{v_1 - 0}{R_1} = \frac{1 - 0}{300} \Rightarrow \underline{i_1 = 3.3 \text{ mA}}$$

Using KCL at the output node-

$$i_{out} = i_f + i_L = 3.3 \text{ mA} + 10 \text{ mA} \Rightarrow \underline{i_{out} = 13.3 \text{ mA}}.$$

Design meets all specifications!