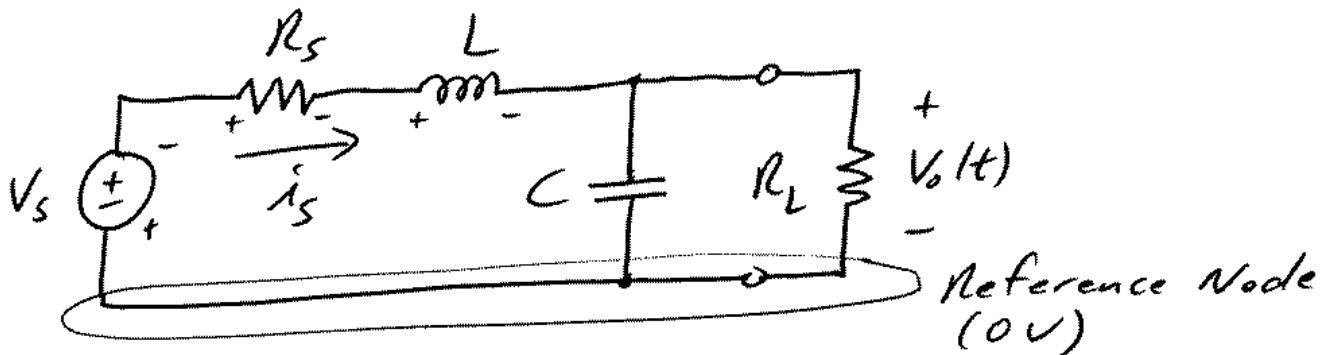


Obtain the differential equation for the output voltage  $v_o(t)$  of the power supply circuit shown. Then, determine  $v_o(t)$  when  $v_s = 12 u(t)$  V,  $R_s = 8 \Omega$ ,  $L = 10 \text{ mH}$ ,  $C = 47 \mu\text{F}$ , and  $R_L = 8 \Omega$  for all time  $t \geq 0$ .



① Apply KVL to outer loop

$$-V_s + i_s R_s + L \frac{di_s}{dt} + V_o(t) = 0$$

② Apply KCL to top right node

$$i_s = C \frac{dV_o}{dt} + \frac{V_o}{R_L}$$

③ Substitute  $i_s$  into first equation

$$\left( C \frac{dV_o}{dt} + \frac{V_o}{R_L} \right) R_s + L \frac{d}{dt} \left( C \frac{dV_o}{dt} + \frac{V_o}{R_L} \right) + V_o = V_s$$

$$R_s C \frac{dV_o}{dt} + \frac{R_s}{R_L} V_o + L C \frac{d^2 V_o}{dt^2} + \frac{L}{R_L} \frac{dV_o}{dt} + V_o = V_s$$

do a little algebra


$$\underline{\underline{\frac{d^2 V_o}{dt^2} + \frac{1}{LC} \left( R_s C + \frac{L}{R_L} \right) \frac{dV_o}{dt} + \frac{1}{LC} \left( \frac{R_s}{R_L} + 1 \right) V_o = \frac{V_s}{LC}}}$$

Find initial & final conditions

$$\text{At } t=0^-, V_s = 0 \Rightarrow i_s(0^-) = i_L(0^-) = 0 = i_c(0^-)$$

$$\Rightarrow V_o(0^-) = V_c(0^-) = 0 = V_o(0^-)$$

At  $t=0^+$  Circuit is in transition

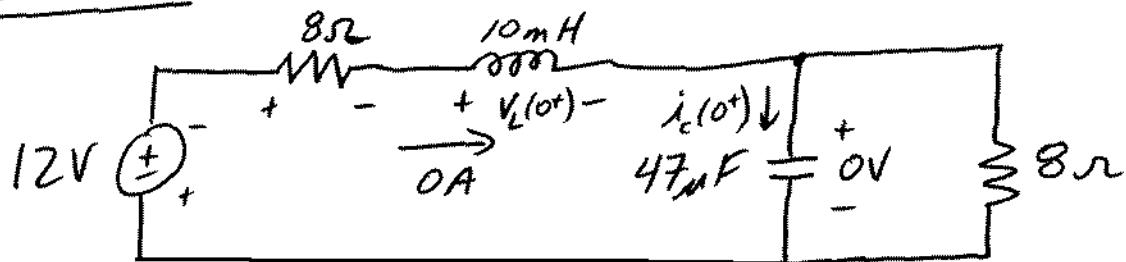

$$\text{Apply KVL} \quad -12 + 0(8\Omega) + V_L(0^+) + 0 = 0$$


$$V_L(0^+) = 10 \times 10^{-3} \frac{di_L}{dt} \Big|_{t=0^+} = 12$$

$$\frac{di_L}{dt} \Big|_{t=0^+} = 1200 \text{ A/S}$$

$$\text{Apply KCL top right node} \quad 0 + i_c(0^+) + \frac{0V}{8\Omega} = 0$$

$$(47 \times 10^{-6}) \frac{dV_o}{dt} \Big|_{t=0^+} = i_c(0^+) = 0 \Rightarrow \frac{dV_o}{dt} \Big|_{t=0^+} = 0$$

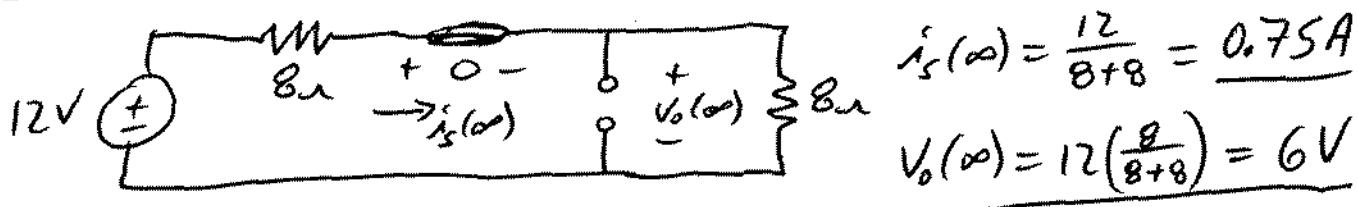At  $t \rightarrow \infty$  Circuit is at steady-state ( $V_L = 0$ ,  $i_c = 0$ )



$$i_s(\infty) = \frac{12}{8+8} = 0.75A$$

$$V_o(\infty) = 12 \left( \frac{8}{8+8} \right) = 6V$$

Determine characteristic equation for natural response ( $V_s = 0$ )

$$s^2 + \frac{1}{LC} \left( R_S C + \frac{L}{R_L} \right) s + \frac{1}{LC} \left( \frac{R_S}{R_L} + 1 \right) = 0$$

$$s^2 + \frac{1}{10 \times 10^{-3} (47 \times 10^{-6})} \left( 8(47 \times 10^{-6}) + \frac{10 \times 10^{-3}}{8} \right) s + \frac{1}{10 \times 10^{-3} (47 \times 10^{-6})} \left( \frac{8}{8} + 1 \right) = 0$$

$$s^2 + 3459.574468 s + 4255319.149 = 0 \quad \rightarrow \text{TI-68}$$

$$s_1 = -1729.787 + j1123.9018 \text{ s}^{-1}$$

$$s_2 = -1729.787 - j1123.9018 \text{ s}^{-1}$$

Natural Response      ↓ underdamped

$$V_{o,n}(t) = e^{-1729.8t} [A_1 \cos(1123.9t) + A_2 \sin(1123.9t)]$$

Forced Response

$$V_{o,f}(t) = V_o(\infty) = 6 \text{ V}$$

Total Response

$$V_o(t) = V_{o,n}(t) + V_{o,f}(t) \quad \leftarrow \text{General Solution}$$

$$\underline{V_o(t) = e^{-1729.8t} [A_1 \cos(1123.9t) + A_2 \sin(1123.9t)] + 6 \text{ V}}$$

Find particular solution (i.e., apply initial conditions)

$$V_o(0) = 0 = e^0 [A_1 \cos(0) + A_2 \sin(0)] + 6 \text{ V}$$

$$\Rightarrow \underline{A_1 = -6 \text{ V}}$$

$$V_o(t) = e^{-1729.8t} [-6 \cos(1123.9t) + A_2 \sin(1123.9t)] + 6 \text{ V}$$

$$\frac{dV_o}{dt} = -1729.8 e^{-1729.8t} [-6 \cos(1123.9t) + A_2 \sin(1123.9t)] \\ + e^{-1729.8t} [+6(1123.9) \sin(1123.9t) + A_2(1123.9) \cos(1123.9t)]$$

$$\left. \frac{dV_o}{dt} \right|_{t=0} = 0 = -1729.8(1) [-6 \overset{\uparrow}{\cos}(0) + A_2 \overset{\uparrow}{\sin}(0)] \\ + (1) [6(1123.9) \overset{\uparrow}{\sin}(0) + A_2(1123.9) \overset{\uparrow}{\cos}(0)]$$

$$\hookrightarrow A_2 = \frac{-6(1729.8)}{1123.9} = \underline{-9.234545}$$

$$\underline{\underline{V_o(t) = e^{-1729.8t} [-6 \cos(1123.9t) - 9.234545 \sin(1123.9t)] + 6 \text{ V}}} \\ \underline{\underline{t \geq 0}}$$

Power Supply Circuit Step Response (underdamped)

$$n := 0 \dots 2000 \quad t_n := n \cdot 3 \cdot 10^{-6} \text{ s}$$

$$\alpha := 1729.787 \text{ np/s} \quad \omega_d := 1123.9018 \text{ rad/s}$$

$$v_o(t) := e^{-\alpha \cdot t} \cdot (-6 \cdot \cos(\omega_d \cdot t) - 9.234545 \cdot \sin(\omega_d \cdot t)) + 6 \text{ V}$$

