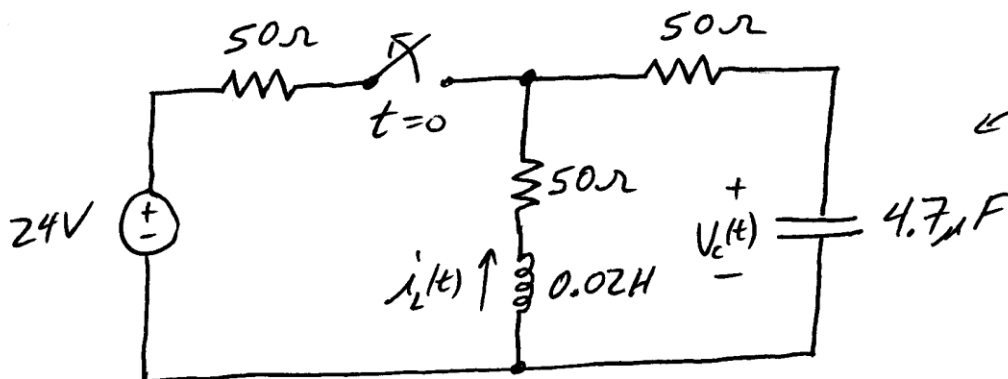



ex. Find  $i_L(t)$  and  $V_C(t)$  for  $t > 0$  for the circuit shown.



Source-Free  
Series RLC  
for  $t > 0$

Step 1 Determine initial conditions

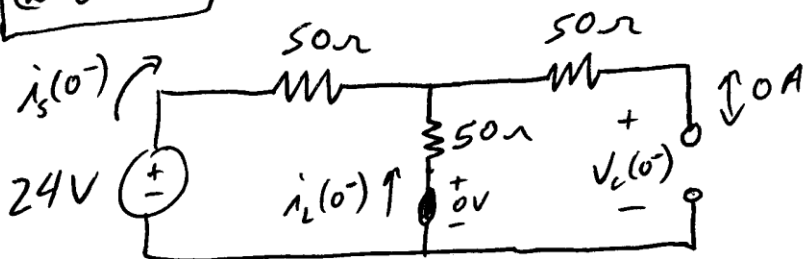@  $t = 0^-$  (Ckt @ steady-state,  $i_C = 0 + V_C = 0$ )



By Ohm's Law,  $i_S(0^-) = \frac{24V}{50+50\Omega} = 0.24A$


$i_L(0^-) = -i_S(0^-) = \underline{\underline{-0.24A = i_L'(0)}}$

By KVL on righthand loop

$0 + i_L(0^-)50 + 0(50) + V_C(0^-) = 0$

$V_C(0^-) = +0.24(50) = \underline{\underline{12V = V_C(0)}}$

@  $t = 0^+$  (Ckt in transition)

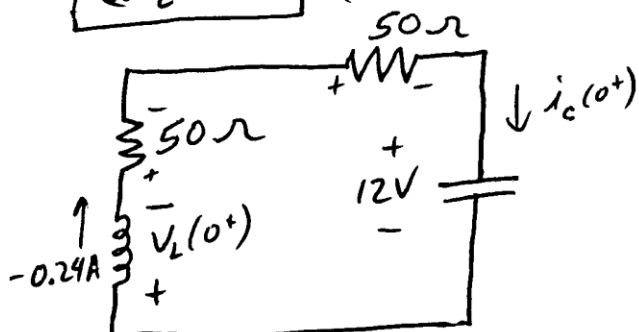

$i_C(0^+) = -0.24A = C \frac{dV_C}{dt} \Big|_{t=0^+}$

$\frac{dV_C}{dt} \Big|_{t=0^+} = \frac{-0.24A}{4.7 \times 10^{-6}F}$

$\frac{dV_C}{dt} \Big|_{t=0^+} = \underline{\underline{-51,064 \frac{V}{s}}}$

Apply KVL around  
the loop

$$V_L(0^+) + (-0.24)(50+50) + 12 = 0$$


$$V_L(0^+) = 0.02 \left. \frac{di_L}{dt} \right|_{t=0^+} = 12$$

$$\left. \frac{di_L}{dt} \right|_{t=0^+} = 600 \text{ A/s}$$

Step 2 Find final conditions (steady-state)

@  $t \rightarrow \infty$

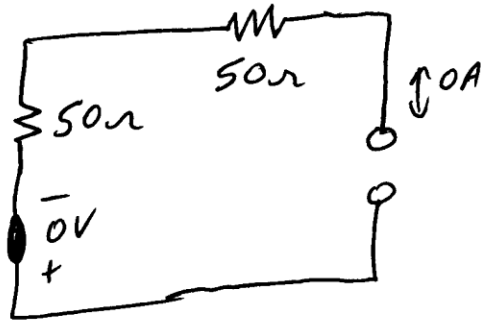No current  
& No Voltages  $\Rightarrow$



$$\underline{i_L(\infty) = 0}$$

$$\underline{V_C(\infty) = 0}$$

Step 3 Differential & Characteristic Eqs

$$(8.4) \frac{d^2 i_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{1}{LC} i_L = 0$$

+

$$(8.8) s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

$$s^2 + \left( \frac{50+50}{0.02} \right) s + \frac{1}{0.02(4.7 \times 10^{-6})} = 0$$

$$s^2 + 5000 s + 10,638,298 = 0$$

$$s_1 = -2500 + j 2094.8 \text{ s}^{-1}$$

$$s_2 = -2500 - j 2094.8 \text{ s}^{-1}$$

Find roots  
using  
TI-68

Underdamped!

From  $s_1$  &  $s_2$  and/or eq'ns:

$$\alpha = |\operatorname{Re}(s_{1,2})| = \frac{R}{2L} = 2500 \text{ rad/s} \quad (8.11)$$

$$\text{damped} \rightarrow \omega_d = |\operatorname{Im}(s_{1,2})| = \sqrt{\omega_0^2 - \alpha^2} = 2094.8 \text{ rad/s} \quad (8.22 a, b)$$

$$\text{undamped} \rightarrow \omega_0 = \frac{1}{\sqrt{LC}} = 3261.6 \text{ rad/s} \quad (8.11)$$

Step 4 General Solution

$$(8.26) \quad i_L(t) = e^{-\alpha t} [B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)]$$

Step 5 Find particular sol'n using initial conditions

$$i_L(0) = -0.24 = e^0 [B_1 \cos(0) + B_2 \sin(0)]$$

$$\hookrightarrow \underline{B_1 = -0.24}$$

$$i_L(t) = e^{-\alpha t} [-0.24 \cos(\omega_d t) + B_2 \sin(\omega_d t)]$$

$$\frac{di_L}{dt} = -\alpha e^{-\alpha t} [-0.24 \cos(\omega_d t) + B_2 \sin(\omega_d t)] + e^{-\alpha t} [0.24 \omega_d \sin(\omega_d t) + B_2 \omega_d \cos(\omega_d t)]$$

$$\left. \frac{di_L}{dt} \right|_{t=0} = 600 = -2500 e^0 [-0.24 \cos(0) + B_2 \sin(0)] + e^0 [0.24(2094.8) \sin(0) + B_2(2094.8) \cos(0)]$$

$$600 = 600 + B_2(2094.8)$$

$$\hookrightarrow \underline{B_2 = 0}$$

Step 5 cont.

$$\underline{i_L(t) = -0.24 e^{-2500t} \cos(2094.8t) \text{ (A)} \quad t \geq 0$$

Step 6 Find  $V_C(t)$ Note that  $i_L(t) = i_C(t)$ . Therefore

$$V_C(t) = \frac{1}{C} \int_{t=0}^t i_L(t) dt + V_C(0)$$

$$= \frac{1}{4.7 \times 10^{-6}} \int_{t=0}^t -0.24 e^{-2500t} \cos(2094.8t) dt + 12 \text{ V}$$

$$\text{Use } \int e^{ax} \cos(bx) dx = \frac{e^{ax} [a \cos(bx) + b \sin(bx)]}{a^2 + b^2}$$

$$V_C(t) = (-51,063.83) \frac{e^{-2500t} [-2500 \cos(2094.8t) + 2094.8 \sin(2094.8t)]}{(-2500)^2 + (2094.8)^2} \Big|_{t=0}^t + 12 \text{ V}$$

$$= -0.0048 \left[ e^{-2500t} (-2500 \cos(2094.8t) + 2094.8 \sin(2094.8t)) - e^0 (-2500 \cos(0) + 2094.8 \sin(0)) \right] + 12$$

$$\underline{V_C(t) = e^{-2500t} [12 \cos(2094.8t) - 10 \sin(2094.8t)] \text{ (V)} \quad t \geq 0$$

Source Free Series RLC circuit (underdamped)

$$n := 0..100 \quad t_n := \frac{0.003}{100} n \quad s$$

$$iL_n := -0.24 \cdot e^{-2500 \cdot t_n} \cdot \cos(2094.8 \cdot t_n) \quad A, t > 0$$

$$vC_n := e^{-2500 \cdot t_n} \cdot (12 \cos(2094.8 \cdot t_n) - 10 \cdot \sin(2094.8 \cdot t_n)) \quad V, t > 0$$

