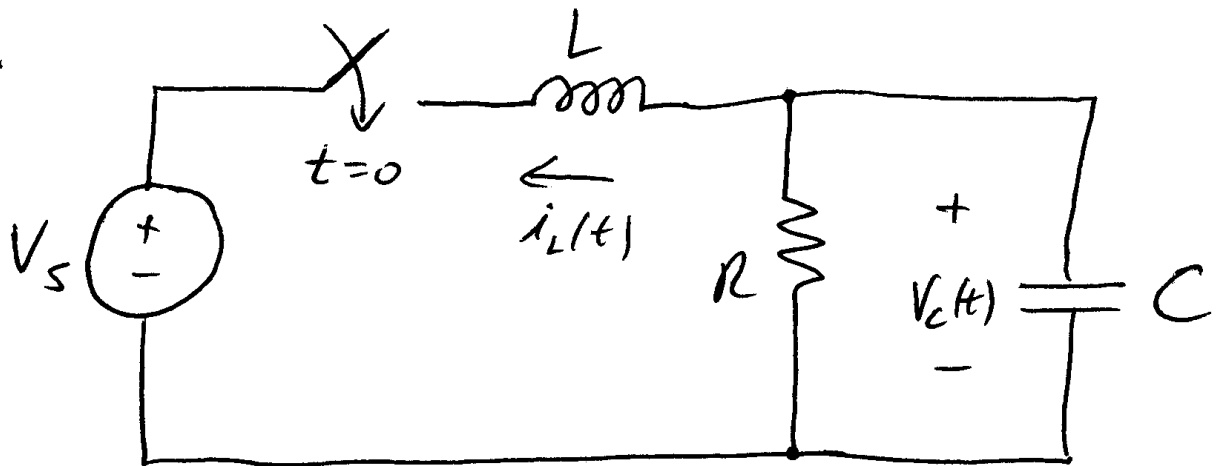



ex.



Find  $i_L(t)$  &  $V_C(t)$  when  $V_s = 5V$ ,  $L = 20mH$ ,  
 $R = 1k\Omega$ , and  $C = 10\mu F$ .

1) Find initial conditions


@  $t=0^-$  (Switch open & steady-state)

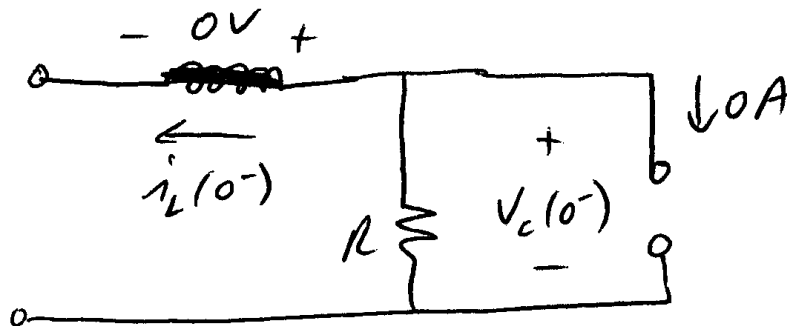

$$\underline{\underline{i_L(0^-) = 0 = i_L(0^+)}}$$

$$\underline{\underline{V_C(0^-) = 0 = V_C(0^+)}}$$

1) cont. @  $t=0^+$

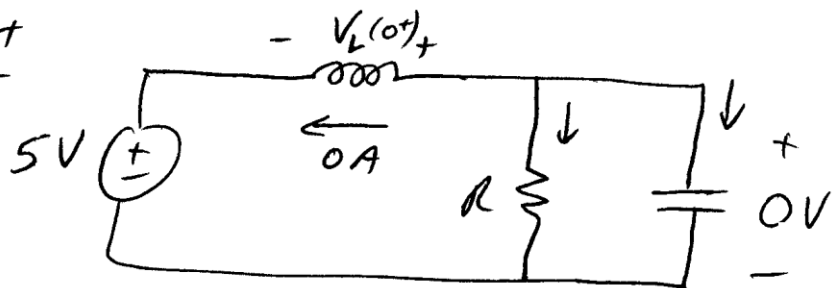

Apply KCL  $0A + \frac{0V}{R} + C \left. \frac{dV_C(t)}{dt} \right|_{t=0^+} = 0$

$$\hookrightarrow \underline{\underline{\left. \frac{dV_C}{dt} \right|_{t=0^+} = 0}}$$


Apply KVL  $-5V - V_L(0^+) + 0 = 0$

$$V_L(0^+) = L \left. \frac{di_L}{dt} \right|_{t=0^+} = -5$$

$$\hookrightarrow \left. \frac{di_L}{dt} \right|_{t=0^+} = \frac{-5}{20 \times 10^{-3}} = \underline{\underline{-250 \frac{A}{s}}}$$

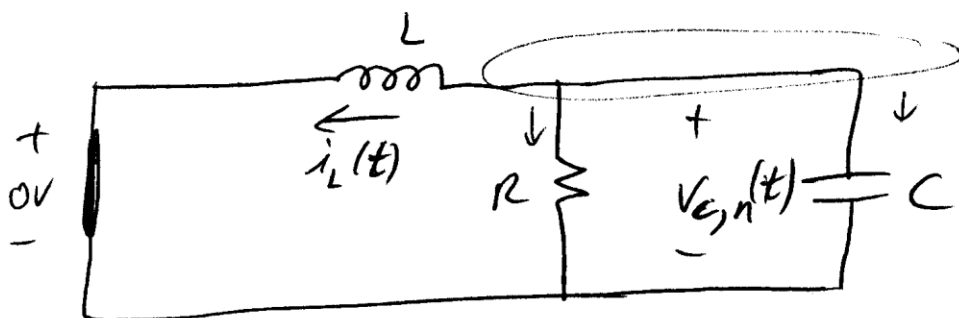2) Find Natural Response  $t \geq 0$

$\rightarrow$  set indep. sources to zero



Apply KCL  $i_L(t) + \frac{V_{C,n}(t)}{R} + C \frac{dV_{C,n}(t)}{dt} = 0$

$$\frac{1}{L} \int_{-\infty}^t V_{C,n}(t) dt + \frac{V_{C,n}(t)}{R} + C \frac{dV_{C,n}(t)}{dt} = 0$$

ex. cont.

2) cont talking  $\frac{d}{dt}$ 

$$\frac{V_{c,n}}{L} + \frac{1}{R} \frac{dV_{c,n}}{dt} + \frac{1}{C} \frac{d^2 V_{c,n}}{dt^2} = 0$$

$$\frac{d^2 V_{c,n}}{dt^2} + \frac{1}{RC} \frac{dV_{c,n}}{dt} + \frac{1}{LC} V_{c,n} = 0$$

Assuming  $V_{c,n} = A e^{st}$ 

Characteristic Eqn  $s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$

Plug in R, L, + C values

$$s^2 + 100s + 5 \times 10^6 = 0$$


TI-68  
root  
solver

$$\left. \begin{aligned} s_1 &= -50 + j 2235.5 \text{ s}^{-1} \\ s_2 &= -50 - j 2235.5 \text{ s}^{-1} \end{aligned} \right\} \underline{\text{Underdamped}}$$

$\uparrow$                        $\uparrow$   
 $\alpha$                        $\omega_d$

$$\underline{\underline{V_{c,n}(t) = e^{-50t} [A_1 \cos(2235.5 t) + A_2 \sin(2235.5 t)]}}$$

ex. cont.

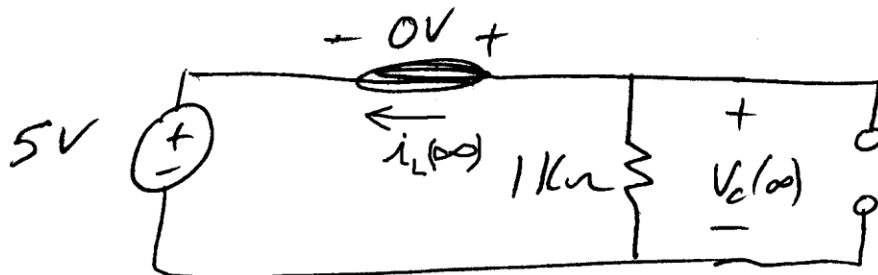3) Find Forced Responselet  $t \rightarrow \infty$  (Steady-state)

$$\Rightarrow \underline{V_c(\infty) = 5V = V_{c,f}} \quad \underline{i_L(\infty) = \frac{0-5}{1000} = -5\text{mA}}$$

4) Find Total Response

$$V_c(t) = V_{c,n}(t) + V_{c,f}$$

$$V_c(t) = e^{-50t} [A_1 \cos(2235.5t) + A_2 \sin(2235.5t)] + 5$$

$$\text{Apply } V_c(0) = 0 = (1) [A_1(1) + A_2(0)] + 5$$

$$\hookrightarrow \underline{A_1 = -5V}$$

$$\begin{aligned} \frac{dV_c(t)}{dt} &= e^{-50t} (-50) [-5 \cos(2235.5t) + A_2 \sin(2235.5t)] \\ &\quad + e^{-50t} [(-5)(-2235.5 \sin(2235.5t)) \\ &\quad \quad + A_2 (2235.5 \cos(2235.5t))] \end{aligned}$$


$$\left. \frac{dV_c}{dt} \right|_{t=0} = 0 = (1)(-50)[-5 + 0] + (1)[0 + A_2(2235.5)]$$

ex. cont.

4) cont.  $A_2 = \frac{-(-50)(-5)}{2235.5} = -0.11183$

$$V_c(t) = e^{-50t} \left[ -5 \cos(2235.5t) - 0.11183 \sin(2235.5t) \right] + 5 \text{ V}$$

$$t \geq 0$$

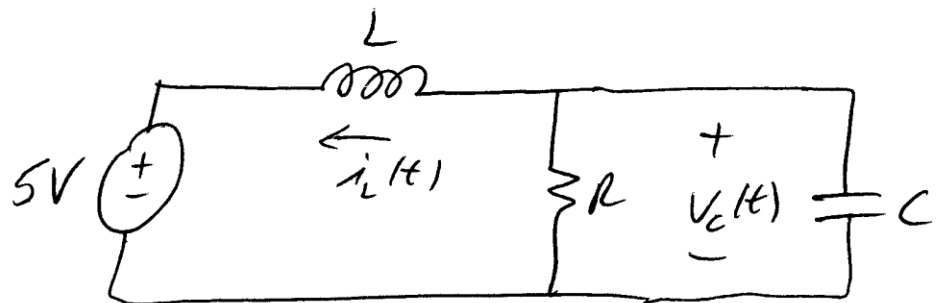Find  $i_L(t)$ 

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t (V_c(t) - 5) dt$$

OR  
using KCL

$$i_L(t) = \frac{0 - V_c(t)}{R} + C \frac{d(0 - V_c(t))}{dt}$$

OR

$$i_L(t) = e^{-50t} \left[ B_1 \cos(2235.5t) + B_2 \sin(2235.5t) \right] + i_L(\infty)$$

$$i_L(t) = e^{-50t} \left[ 5 \cos(2235.5t) - 111.72 \sin(2235.5t) \right] - 5 \text{ mA}$$

$$t \geq 0$$

## Step Response Parallel RLC circuit (underdamped)

$$n := 0..2000 \quad t_n := \frac{n}{33000} \text{ s}$$

$$v_C(x) := e^{-50 \cdot x} \cdot (-5 \cdot \cos(2235.5 \cdot x) - 0.11183 \cdot \sin(2235.5 \cdot x)) + 5 \quad \text{V}$$

$$i_L(x) := e^{-50 \cdot x} \cdot (5 \cdot \cos(2235.5 \cdot x) - 117.19 \cdot \sin(2235.5 \cdot x)) - 5 \quad \text{mA}$$

