


EE 220 Circuits I (Fall 2017) Quiz #1

Name Key A

Instructions: **Closed** notes & homework. Place answers in indicated spaces & show all work for credit.

Useful equations: $v = iR$, $p = vi = i^2R = v^2/R$, $i = dq/dt$, $v_{ab} = dw/dq$, $\sum_{\text{circuit}} p = 0$, $w = \int p dt$, $q = \int i dt$

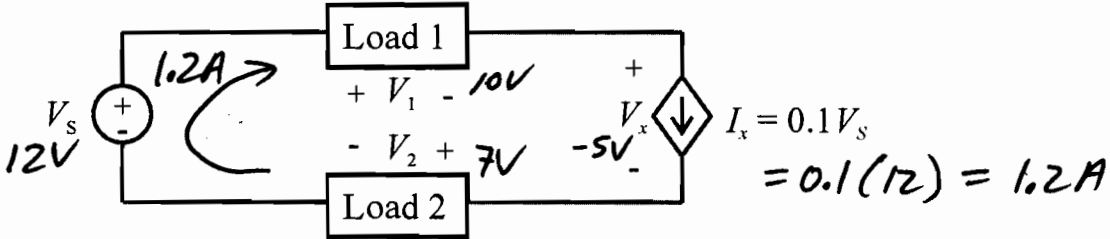1) For the circuit elements shown, calculate the power **absorbed** by each circuit element (remember passive sign convention) if $V_S = 12\text{ V}$, $V_1 = 10\text{ V}$, $V_x = -5\text{ V}$, and $V_2 = 7\text{ V}$,



$$P_{V_S} = -(12)(1.2) = -14.4\text{ W}$$

$$P_1 = +(10)(1.2) = 12\text{ W}$$

$$P_2 = +(7)(1.2) = 8.4\text{ W}$$

$$P_x = +(-5)(1.2) = -6\text{ W}$$

Check $\sum P_{abs} = 0? \Rightarrow -14.4 + 12 + 8.4 - 6 = 0 \therefore$

$P_{V_S} = \underline{-14.4\text{ W}}$ $P_1 = \underline{12\text{ W}}$ $P_x = \underline{-6\text{ W}}$ $P_2 = \underline{8.4\text{ W}}$

2) Solve the given problems involving complex numbers in the specified formats.

used
TI-68

$(-9 + j3) / (5 - j6) = \underline{-1.0328 - j0.6393}$
(express answer in rectangular format)

$(4\angle 45^\circ) + (2\angle -60^\circ) = \underline{3.9823 \angle 15.9805^\circ}$
(express answer in polar/phasor format with angle in degrees)


EE 220 Circuits I (Fall 2017) Quiz #1

Name Key B

Instructions: **Closed** notes & homework. Place answers in indicated spaces & show all work for credit.

Useful equations: $v = iR$, $p = vi = i^2R = v^2/R$, $i = dq/dt$, $v_{ab} = dw/dq$, $\sum_{\text{circuit}} p = 0$, $w = \int p dt$, $q = \int i dt$

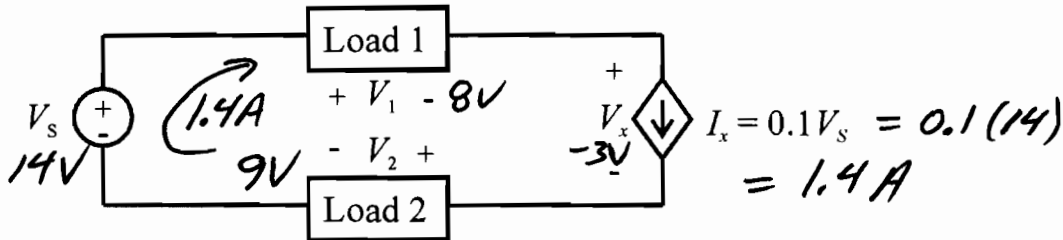- 1) For the circuit elements shown, calculate the power **absorbed** by each circuit element (remember passive sign convention) if $V_s = 14\text{ V}$, $V_1 = 8\text{ V}$, $V_x = -3\text{ V}$, and $V_2 = 9\text{ V}$,



$$P_{Vs} = -(14)(1.4) = -19.6\text{ W}$$

$$P_1 = + (8)(1.4) = 11.2\text{ W}$$

$$P_x = + (-3)(1.4) = -4.2\text{ W}$$

$$P_2 = + (9)(1.4) = 12.6\text{ W}$$

check $\sum P_{abs} = 0? \Rightarrow -19.6 + 11.2 - 4.2 + 12.6 = 0 \therefore$

$$P_{Vs} = \underline{-19.6\text{ W}} \quad P_1 = \underline{11.2\text{ W}} \quad P_x = \underline{-4.2\text{ W}} \quad P_2 = \underline{12.6\text{ W}}$$

- 2) Solve the given problems involving complex numbers in the specified formats.

used
TI-68

$$(8 - j4) / (-5 + j6) = \underline{-1.0492 - j0.4590}$$

(express answer in rectangular format)

$$(6\angle -25^\circ) + (3\angle 30^\circ) = \underline{8.1024 \angle -7.3441^\circ}$$

(express answer in polar/phasor format with angle in degrees)