

EE 220 Circuits I (Fall 2017) Quiz #2

Name


Key A

Instructions: Closed notes & homework. Place answers in indicated spaces & show all work for credit.

Useful equations:

$$v = iR, \quad p = vi = i^2R = v^2/R, \quad G = 1/R, \quad \text{KVL: } \sum_{i, \text{closed loop}} v_{\text{drops}, i} = 0, \quad \text{KCL: } \sum_{n, \text{closed surface}} i_n = 0, \quad R_{\text{eq, Series}} = \sum R_n,$$

$$v_n = v \left(\frac{R_n}{R_{\text{eq}, S}} \right), \quad R_{\text{eq, Parallel}} = \left[\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right]^{-1}, \quad i_n = i \left(\frac{R_{\text{eq}, P}}{R_n} \right) = i \left(\frac{G_n}{G_{\text{eq}, P}} \right)$$

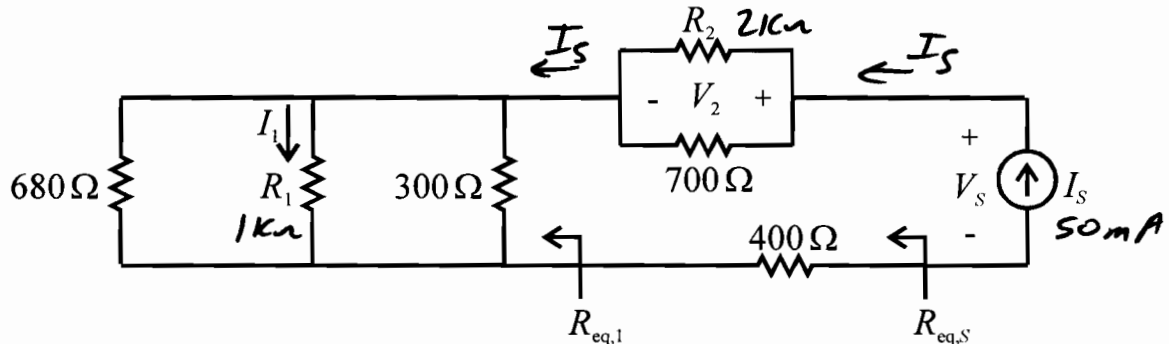Given: $I_S = 50 \text{ mA}$, $R_1 = 1 \text{ k}\Omega$, and $R_2 = 2 \text{ k}\Omega$.1) Determine the equivalent resistance $R_{\text{eq},1}$ and $R_{\text{eq},S}$.

$$R_{\text{eq},1} = 680 \parallel 1000 \parallel 300 = \left[\frac{1}{680} + \frac{1}{1000} + \frac{1}{300} \right]^{-1} = 172.297 \Omega$$

$$R_{\text{eq},S} = R_2 \parallel 700 + R_{\text{eq},1} + 400 = \left[\frac{1}{2000} + \frac{1}{700} \right]^{-1} + 172.297 + 400 = 518.5185 + 172.297 + 400 = 1090.815816 \Omega$$

$$R_{\text{eq},1} = 172.297 \Omega$$

$$R_{\text{eq},S} = 1090.816 \Omega$$

2) Determine the voltage V_S across the current source.

$$V_S = I_S R_{\text{eq},S} = 0.05 (1090.816) = 54.5408 \text{ V}$$

$$V_S = 54.5408 \text{ V}$$

3) Determine the voltage V_2 across resistor R_2 .

$$V_2 = I_S (R_2 \parallel 700) = 0.05 (518.5185) = 25.925926 \text{ V}$$

$$V_2 = 25.9259 \text{ V}$$

4) Determine the current I_1 through resistor R_1 .

$$I_1 = I_S \frac{R_{\text{eq},1}}{R_1} = 50 \text{ mA} \left(\frac{172.297}{1000} \right)$$

$$= 8.614865 \text{ mA}$$

$$I_1 = 8.6149 \text{ mA}$$

EE 220 Circuits I (Fall 2017) Quiz #2

Name


Key B

Instructions: Closed notes & homework. Place answers in indicated spaces & show all work for credit.

Useful equations:

$$v = iR, \quad p = vi = i^2R = v^2/R, \quad G = 1/R, \quad \text{KVL: } \sum_{i, \text{closed loop}} v_{\text{drops}, i} = 0, \quad \text{KCL: } \sum_{n, \text{closed surface}} i_n = 0, \quad R_{\text{eq, Series}} = \sum R_n,$$

$$v_n = v \left(\frac{R_n}{R_{\text{eq}, S}} \right), \quad R_{\text{eq, Parallel}} = \left[\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right]^{-1}, \quad i_n = i \left(\frac{R_{\text{eq}, P}}{R_n} \right) = i \left(\frac{G_n}{G_{\text{eq}, P}} \right)$$

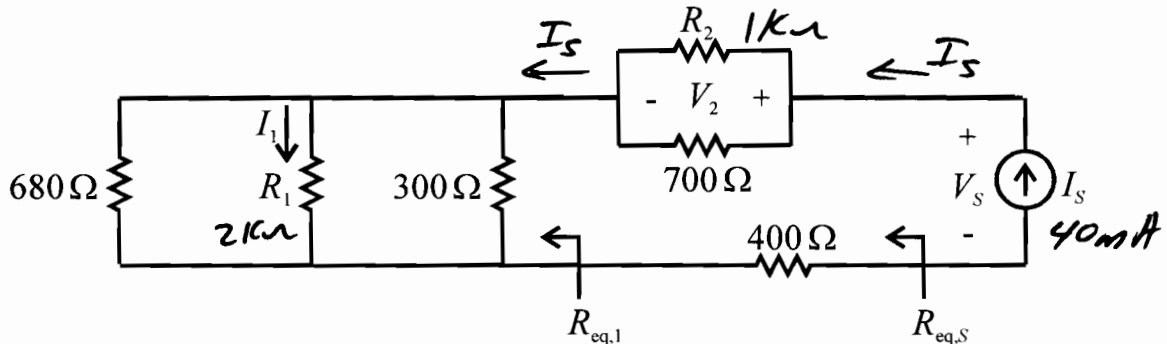Given: $I_S = 40 \text{ mA}$, $R_1 = 2 \text{ k}\Omega$, and $R_2 = 1 \text{ k}\Omega$.

- 1) Determine the equivalent resistance
- $R_{\text{eq},1}$
- and
- $R_{\text{eq},S}$
- .

$$R_{\text{eq},1} = 680 \parallel 2\text{k} \parallel 300 = \left[\frac{1}{680} + \frac{1}{2000} + \frac{1}{300} \right]^{-1} = 188.5397 \Omega$$

$$R_{\text{eq},S} = R_2 \parallel 700 + R_{\text{eq},1} + 400 = \left[\frac{1}{1000} + \frac{1}{700} \right]^{-1} + 188.5397 + 400 = 411.764706 + 188.5397 + 400 = 1000.30447 \Omega$$

$$R_{\text{eq},1} = \underline{188.5397 \Omega}$$

$$R_{\text{eq},S} = \underline{1000.3044 \Omega}$$

- 2) Determine the voltage
- V_S
- across the current source.

$$V_S = I_S R_{\text{eq},S} = 0.04 (1000.3044) = 40.0121778 \text{ V}$$

$$V_S = \underline{40.0122 \text{ V}}$$

- 3) Determine the voltage
- V_2
- across resistor
- R_2
- .

$$V_2 = I_S (R_2 \parallel 700) = 0.04 (411.7647) = 16.47058823 \text{ V}$$

$$V_2 = \underline{16.4706 \text{ V}}$$

- 4) Determine the current
- I_1
- through resistor
- R_1
- .

$$I_1 = I_S \frac{R_{\text{eq},1}}{R_1}$$

$$= 40 \text{ mA} \left(\frac{188.5397}{2000} \right) = 3.7708 \text{ mA}$$

$$I_1 = \underline{3.7708 \text{ mA}}$$