

Homework 3
EE 220 Circuits I Fall 2019
Friday, September 13, 2019

- 1) PP3.2
- 2) PP3.7
- 3) PP3.12 Change 6 V source to 3 V and make $\beta = 150$. Solve using mesh analysis.
- 4) PP3.12 Change 6 V source to 3 V and make $\beta = 150$. Solve using nodal analysis. Hint: Use equivalent circuit model for transistor.
- 5) 3.16
- 6) 3.24 Note: Matlab use is optional.
- 7) 3.43
- 8) 3.58

Due Friday, September 20, 2019