

Homework 6
EE 220 Circuits I Fall 2019
Friday, October 18, 2019

- 1) pp6.2
- 2) pp6.7 Also, find C_{eq} seen by source and charge stored by each capacitor.
- 3) 6.11
- 4) 6.18
- 5) 6.39
- 6) 6.40
- 7) 6.47 Also, find voltage across capacitor, current through inductor, and energy stored by each for this value of R .
- 8) 6.56

Due Wednesday, October 23, 2019