

**Homework 9**  
**EE 220 Circuits I Fall 2019**  
**Monday, November 18, 2019**

- 1) PP9.1 Also, express sinusoid as a phasor.
- 2) PP9.9 Also, draw phasor equivalent circuit.
- 3) PP9.12 Also, find the equivalent impedance  $Z_{eq}$  'seen' by the source.
- 4) 9.16
- 5) 9.23
- 6) 9.34 Also, draw the phasor equivalent circuit and find the equivalent impedance  $Z_{eq}$  'seen' by the source at frequency  $\omega$ .
- 7) 9.46 Also, draw phasor equivalent circuit and use phasor analysis to find the equivalent impedance  $Z_{eq}$  'seen' by the source.
- 8) 9.66 Also, find  $Y_T$ . Express answers for  $Y_T$  and  $Z_T$  in both rectangular and polar (angle in degrees) forms.

- Notes:
- For this class, always define phasors in terms of the **cos()** function.
  - Unless told otherwise, always put current & voltage phasors in polar form with angle in degrees (e.g.,  $A\angle\theta$ ).
  - Unless told otherwise, always put time-domain sinusoidal currents & voltages in terms of the **cos()** function.
  - Unless told otherwise, always put impedances & admittances in rectangular form (e.g.,  $A + jB$ ).

**Due Friday, November 22, 2019.**