

Homework 11 (Extra Credit)
EE 220 Circuits I Fall 2019
Friday, December 6, 2019

- 1) PP11.14 Also, if the loads are supplied with $120\angle 0^\circ$ V_{rms}, find the input rms phasor current and equivalent impedance.
- 2) If $v(t) = 318 \cos(377t)$ V and $i(t) = 6 \sin(377t + 65^\circ)$ A for a load, find the RMS phasor current and voltage. Then, calculate the load impedance, power factor, and the instantaneous, apparent, complex, time-average real, & reactive powers.
- 3) 11.17 First, find and sketch the Thevenin equivalent 'seen' by the load.
- 4) 11.30
- 5) 11.50 Also, find power factor (don't forget to specify 'leading' or 'lagging').
- 6) 11.51 For circuit shown in **Fig. 10.97**. Per note on bottom of page 488, assume voltage source is rms phasor.
- 7) 11.54 Per note on bottom of page 488, assume current source is rms phasor.
- 8) 11.69 Also, find the rms phasor current from the source before and after the capacitor is connected.

Notes:

- This is an extra credit opportunity. If completed, the grade for HW #11 will replace your lowest HW *or* quiz grade (whichever helps most).
- Extra motivation- There will be *at least* one similar question dealing with AC power on the final.

Due by 4 pm Tuesday, December 10, 2019.