

## EE 220/220L Circuits I (Fall 2019)

### Laboratory 5 Mesh Analysis

#### Background

The goals of this lab are to analyze the DC operation of an npn bipolar junction transistor (BJT) in the **active** mode and experimentally verify the results for the circuit shown in Figure 1. For analysis, assume that  $V_{CC} = 17.8\text{ V}$ ,  $R_1 = 39\text{ k}\Omega$ ,  $R_2 = 5.6\text{ k}\Omega$ ,  $R_C = 680\text{ }\Omega$ , &  $R_E = 130\text{ }\Omega$  with a transistor where  $\beta = 190$  and  $V_{BE} = 0.67\text{ V}$ . Datasheet(s) with information on the Fairchild PN2222A transistors used is available on the course web page (purchased 2009-2013).

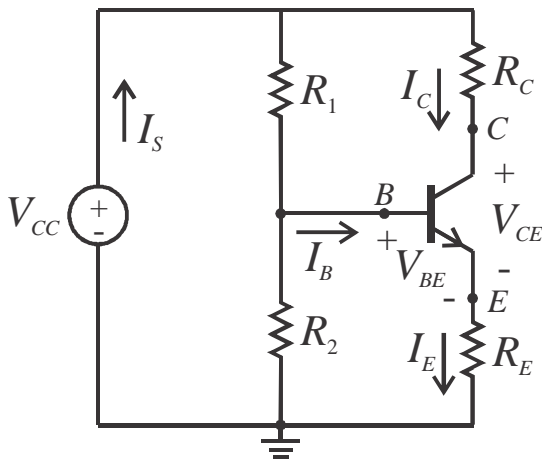


Figure 1 Transistor Circuit

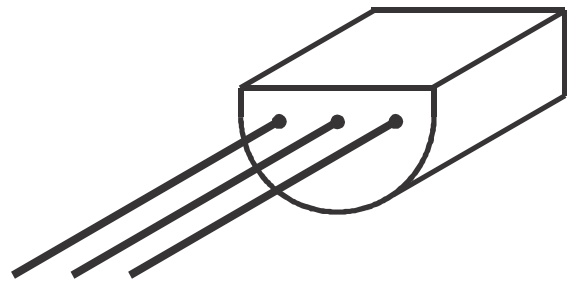


Figure 2 PN2222A Transistor TO-92 Package

#### Preliminary

- 1) Using transistor datasheet(s) (insert relevant parts in logbook), label the transistor leads in Figure 2 (e.g., B, C, & E). Then, insert information/graphs on absolute maximum ratings, DC current gain  $h_{FE}$  (AKA:  $\beta$ ), and  $V_{BE}$  for the **active** (AKA: on) mode, **NOT** saturation or cut-off modes.
- 2) Using the equivalent circuit model for the transistor (see section 3.9 in the text), analyze the transistor circuit shown in Figure 1 using **mesh analysis** to find the mesh currents  $I_S$ ,  $I_C$ , &  $I_E$ . Also, calculate the base current  $I_B$ , collector voltage  $V_C$ , emitter voltage  $V_E$ , base voltage  $V_B$ , and collector-emitter voltage  $V_{CE}$ . [Note: **Do NOT** rename variables.]
- 3) Using the values calculated in part 2, mark and read off the expected value of  $V_{BE}$  on the datasheet excerpts of part 1. Does the datasheet agree with the given  $V_{BE}$  value? Do the values calculated in part 2 correspond to one of the DC current gain conditions? If so, mark which one.
- 4) Calculate the power absorbed by each circuit component. (Hint: To find the amount of power absorbed by the transistor  $P_Q$ , calculate  $|P_{source}|$  and subtract powers dissipated by the resistors.)

SHOW ALL WORK IN LOGBOOK!

- 5) Have the lab instructor or TA sign-off on your preliminary before you begin the experiment.

#### Experiment

- 1) Using a digital multimeter (DMM), measure and record actual value of each resistor. Also, measure  $\beta_{DMM}$  (AKA:  $h_{FE}$ ) for the BJT using the DMM (see upper righthand corner on front).
- 2) Build the circuit on a breadboard. Measure and record the currents  $I_S$ ,  $I_C$ ,  $I_E$ , &  $I_B$  and the voltages  $V_{BE}$ ,  $V_{CE}$ ,  $V_E$ ,  $V_C$ ,  $V_B$ , &  $V_{CC}$ . [Note: Due to measurement error, it is possible to measure  $I_C > I_E$ .]
- 3) Have the lab instructor or a TA sign-off on your data before you tear down the circuit.

**Analysis and Conclusions**

- Use experimental data to calculate the actual  $\beta_{\text{meas}} = I_C / I_B$  and power absorbed by each circuit component.
- Prepare a neat table in your logbook to compare the calculated/nominal resistor values, source voltage, voltages, currents,  $\beta$  (include both  $\beta_{\text{DMM}}$  and  $\beta_{\text{meas}}$  on separate lines), and powers to those measured. Put the variable name/label in first column, calculated/nominal values in second column, measured values in third column, and percent difference between the calculated/nominal and measured values in fourth column.
- Analyze the data and discuss the results. Explain differences from calculated/predicted values.
- Why might  $\beta_{\text{DMM}}$  be different from  $\beta_{\text{meas}}$ ?