

## EE 220/220L Circuits I (Fall 2019)

### Laboratory 7 Thevenin and Norton Circuits

#### Background

The goal of this lab is to demonstrate the validity of Thevenin's and Norton's theorems. These theorems are useful for analyzing linear circuits by reducing them to a single independent source and resistor with respect to a pair of terminals where loads can be changed in and out.

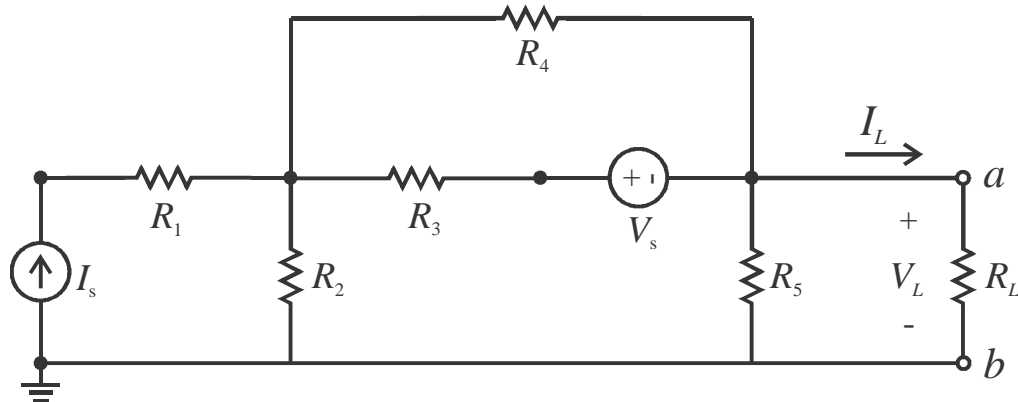


Figure 1 Circuit layout

#### Preliminary

We are interested in determining the power dissipated by a load resistor  $R_L$  connected between terminals  $a$  and  $b$  in the circuit shown above.

- 1) For  $R_L = 100 \Omega$ , use circuit analysis (e.g., nodal or mesh analysis) to find the voltage  $V_L$  across and current  $I_L$  through the load resistor  $R_L$  in Figure 1. Given:  $V_s = 20 \text{ V}$ ,  $I_s = 30 \text{ mA}$ ,  $R_1 = 220 \Omega$ ,  $R_2 = 470 \Omega$ ,  $R_3 = 680 \Omega$ ,  $R_4 = 330 \Omega$ , and  $R_5 = 1.5 \text{ k}\Omega$ . Then, calculate the power  $P_L$  dissipated by the load resistor. **SHOW ALL WORK IN LOGBOOK!**
- 2) Verify your results in step 1) using PSpice. Attach the PSpice circuit with voltage and current outputs displayed in the logbook with text showing EE 220L-xx, Lab #7, *your name, date, & description* of work.
- 3) Next, for the circuit shown in Fig. 1, remove  $R_L$  and calculate the equivalent resistance seen at terminals  $a$ - $b$ . This equivalent resistance is the Thevenin ( $R_T$ ) and Norton ( $R_N$ ) equivalent resistances. Then, calculate the open circuit voltage  $V_{oc} = V_T$  across terminals  $a$ - $b$ . By source transformation, the Norton equivalent current  $I_N = V_T / R_T$  [ **OR** Calculate the short circuit current  $I_{sc} = I_N$  flowing from terminal  $a$  to  $b$ . The Thevenin equivalent voltage  $V_T = I_N * R_N$ .] Draw fully labeled Thevenin and Norton equivalent circuits.
- 4) Verify your results in step 3) using PSpice. To get  $V_{oc}$ , replace  $R_L$  with an open circuit, simulate, display voltages, and print. [Hint: Delete  $R_L$  or set  $R_L$  equal to a large resistance, e.g.,  $10 \text{ G}\Omega$ .] To get  $I_{sc}$ , replace  $R_L$  with a short circuit, simulate, display currents, and print. [Hint: Set  $R_L$  equal to a very small resistance, e.g.,  $0.1 \text{ m}\Omega$ .] The equivalent resistance  $R_{eq} = R_T = R_N = V_{oc} / I_{sc}$ . Attach the PSpice circuits with voltage and current outputs displayed in logbook with text showing EE 220L-xx, Lab #7, *your name, date, & descriptions* of work.
- 5) Connect  $R_L = 100 \Omega$  to **both** the Thevenin and Norton equivalent circuits. Then, calculate  $V_L$ ,  $I_L$ , and  $P_L$  for **both** equivalent circuits. Compare with results of parts 1) & 2).
- 6) Have the lab instructor or TA sign-off on your preliminary before you begin the experiment.

## Experiment

- 1) After measuring the resistors (including  $R_L$ ), build the circuit shown in Figure 1. Remember to set the current and voltage sources with the power supply connected to the complete circuit. Measure and record  $V_S$ ,  $I_S$ ,  $V_L$ , and  $I_L$ . Then, calculate the power  $P_L$  dissipated by the load resistor. Record all results (including resistor and source values) in a table.
- 2) Next, experimentally determine the Thevenin and Norton equivalent circuits for the circuit shown in Figure 1. **Remember the current source must be checked and re-set whenever the circuit is changed** (e.g.,  $R_L$  is removed or changed).
  - a) Remove  $R_L$ , then measure and record the open circuit voltage  $V_{oc,meas}$  (i.e.,  $V_{T,meas}$ ) across terminals  $a$ - $b$ .
  - b) Remove  $R_L$  and replace with short circuit (i.e., ammeter). Measure and record short circuit current  $I_{sc,meas}$  (i.e.,  $I_{N,meas}$ ) from terminal  $a$  to  $b$ . Compute  $R_{eq,meas1} = V_{oc,meas} / I_{sc,meas}$ .
  - c) Measure and record the equivalent resistance  $R_{eq,meas2}$  (i.e.,  $R_T = R_N$ ) with ohmmeter. [Hint: Disconnect the voltage source & replace with a wire (i.e., short circuit) and disconnect the current source (i.e., open circuit).] How does  $R_{eq,meas1}$  compare with  $R_{eq,meas2}$ ?
  - d) Record analytic and experimental results for  $V_T$ ,  $I_N$ , and  $R_{eq} = R_T = R_N$  (both) in a table. Table format- variable name in first column, calculated values in second column, measured values in third column, and percent difference in the fourth column.
- 3) Based on the results of part 2), build the Thevenin equivalent circuit. I.e., set voltage source equal to  $V_{T,meas}$  and come up with a resistor or resistor combination close to  $R_{T,meas2}$  to connect in series (sketch your resistor/resistor combination). Measure and record  $V_{T,exp}$  and  $R_{T,exp}$ . Then, successively measure & connect load resistances of  $150 \Omega$ ,  $1 \text{ k}\Omega$ , and  $R_T$ . Measure  $V_L$  and  $I_L$  (use to get measured  $P_L$ ) for each  $R_L$ .
- 4) Have the lab instructor or a TA sign-off on your data.

## Analysis and Conclusions

- Using the experimental Thevenin equivalent circuit (i.e.,  $V_{T,exp}$  and  $R_{T,exp}$ ), calculate  $V_L$ ,  $I_L$ , and  $P_L$  when  $R_L = 150 \Omega$ ,  $1 \text{ k}\Omega$ , and  $R_T$ . Put results in a single table with the experimental results of part 3). Table format: column 1 nominal  $R_L$ , column 2 measured  $R_L$ , column 3 calculated  $V_L$ , column 4 measured  $V_L$ , column 5 calculated  $I_L$ , column 6 measured  $I_L$ , column 7 calculated  $P_L$ , and column 8 measured  $P_L$ .
- On a single graph, use **Matlab** to plot load power  $P_L$  (mW) versus load resistance  $R_L$  ( $\Omega$ ) for both the analytical (**solid line**) and experimental (**individual dots**) cases. For the analytic trace, use  $V_{T,exp}$  and  $R_{T,exp}$  values in your equation for  $P_L$ . Use enough data points (i.e.,  $R_L$  values) to achieve a smooth line [as a suggestion make step size  $\Delta R_L \leq 50 \Omega$ ]. Make the horizontal ( $R_L$ ) axis go from 0 to  $1500 \Omega$ . Label results using a legend. Insert both graph and m-file (include EE 220L-xx, Lab #7, *your name, date, & description of work* in comment lines) in logbook. Keeping in mind the maximum power transfer theorem, comment on the results shown by the graph.
- Analyze the data and discuss the results. Explain differences between measured and calculated/predicted values.