

In the lab, the nominal AC circuit was set up with $v_S(t) = 8 \cos(1000t)$ V and the component values shown.

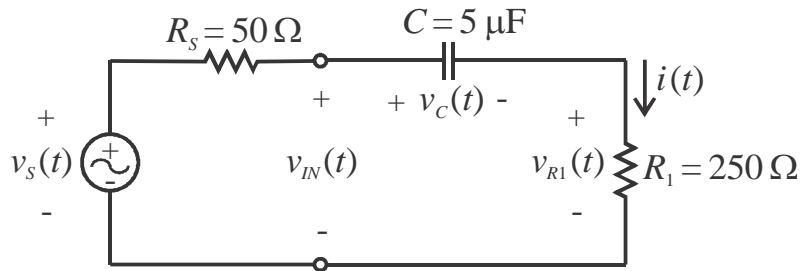


Figure 1 Nominal time-domain circuit

We will use experimental measurements to determine the values for the following phasor equivalent circuit and later the ‘real’ time-domain circuit.


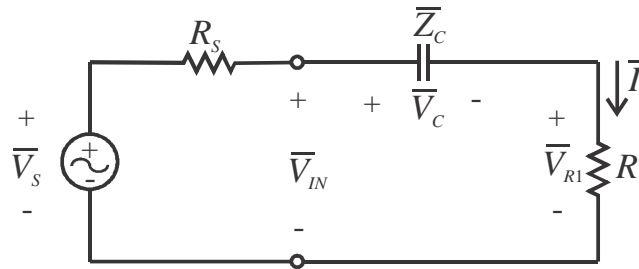


Figure 2 Phasor equivalent circuit

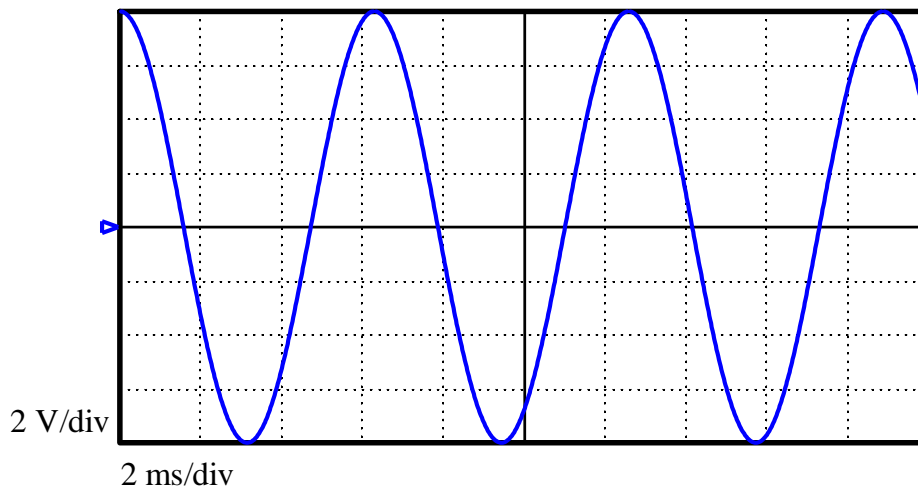
- 1) Assume that $\underline{R}_S = 50 \Omega$ as specified by function generator specifications.
- 2) Use a digital multimeter to measure $\underline{R}_1 = 251.48 \Omega$.
- 3) Use an oscilloscope connected directly to the function generator to set up $v_S(t)$ with the screen display shown below.



Using the oscilloscope measurements menu, determine:

the peak-to-peak voltage is $15.98 \text{ V} \Rightarrow \underline{V_{S,m}} = 7.99 \text{ V}$, and
the period is $\underline{T = 6.283 \text{ ms}}$.

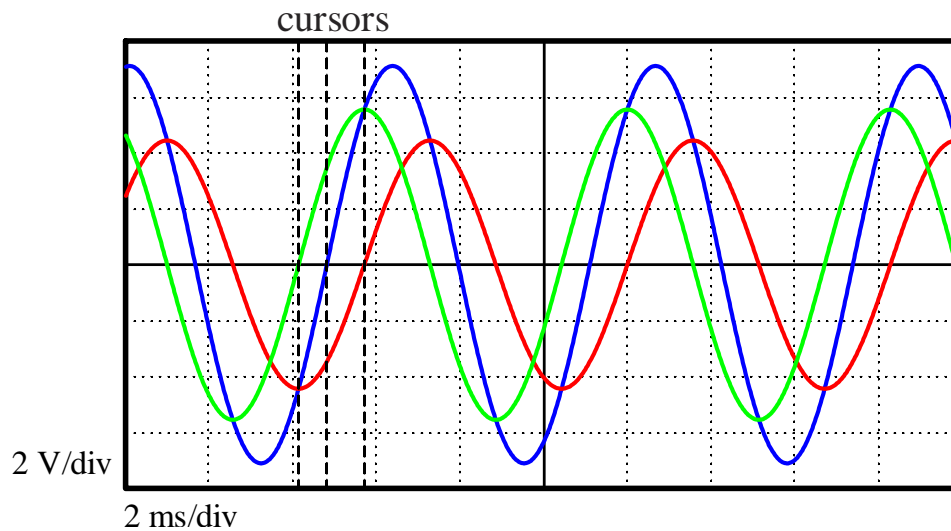- 4) Connect the circuit shown in Figure 1. Then, set up and connect the oscilloscope to measure $v_{IN}(t)$ [ch 1- blue line], $v_{R1}(t)$ [ch 2- green line], & $v_C(t)$ [math- red line] with the screen display shown below.



Using the oscilloscope measurements menu, determine:

the peak-to-peak voltage for $v_{IN}(t)$ is 14.38 V \Rightarrow $V_{IN,m} = 7.19$ V,

the peak-to-peak voltage for $v_{R1}(t)$ is 11.22 V \Rightarrow $V_{R1,m} = 5.61$ V, and

the period is $T = 6.283$ ms (no change).

Using the oscilloscope cursors menu, determine:

the peak-to-peak voltage for $v_C(t)$ is 8.98 V \Rightarrow $V_{C,m} = 4.49$ V,

the time offset between $v_{IN}(t)$ & $v_{R1}(t)$ is +673 μ s

now calculate \Rightarrow $\theta_{R1} = 0.673/6.283 * 360^\circ = 38.56^\circ$,

the time offset between $v_{IN}(t)$ & $v_C(t)$ is -900 μ s

now calculate \Rightarrow $\theta_C = -0.900/6.283 * 360^\circ = -51.57^\circ$,

Hints:

- To determine the magnitude of sinusoidal signals, measure the peak-to-peak voltage V_{pp} . Then, the sinusoidal voltage magnitude $V_m = V_{pp}/2$.
- To calculate the phase angle of sinusoidal voltages relative to our reference signal $v_{IN}(t)$:
 - a) Measure period T of the sinusoidal voltages. Remember one period T is equivalent to 360° of phase.
 - b) Measure time offset Δt_{off} (positive number) between the sinusoidal voltage with respect to $v_{IN}(t)$. The magnitude of the offset angle is $\theta_{off} = (\Delta t_{off}/T) * 360^\circ$.
 - c) Comparing similar points on the sinusoidal voltages (e.g., zero crossings with positive slopes), if the voltage is shifted to the left of $v_{IN}(t)$, θ_{off} is leading (positive angle). If the voltage is shifted to the right of $v_{IN}(t)$, θ_{off} is lagging (negative angle).

- 5) Assuming $v_{IN}(t)$ to be the reference voltage, determine the phasors \bar{V}_{IN} , \bar{V}_{R1} , & \bar{V}_C from the oscilloscope data:

$$\begin{aligned}\bar{V}_{IN} &= V_{IN,m} \angle 0^\circ \Rightarrow \underline{\bar{V}_{IN} = 7.19 \angle 0^\circ \text{ V}} \\ \bar{V}_{R1} &= V_{R1,m} \angle \theta_{R1} \Rightarrow \underline{\bar{V}_{R1} = 5.61 \angle 38.56^\circ \text{ V}} \\ \bar{V}_C &= V_{C,m} \angle \theta_C \Rightarrow \underline{\bar{V}_C = 4.49 \angle -51.57^\circ \text{ V}}\end{aligned}$$

- 6) Using Ohm's Law, \bar{V}_{R1} , & the measured R_1 , determine the phasor current \bar{I} when $v_{IN}(t)$ is the reference:

$$\bar{I} = \bar{V}_{R1} / R_1 = 5.61 \angle 38.56^\circ / 251.48 \Rightarrow \underline{\bar{I} = 22.308 \angle 38.56^\circ \text{ mA}}$$

- 7) Using KVL, \bar{V}_{IN} , \bar{I} , R_1 , and Ohm's Law, determine the phasor source voltage \bar{V}_S when $v_{IN}(t)$ is the reference:

$$\bar{V}_S = \bar{I} R_S + \bar{V}_{IN} = (0.0223 \angle 38.56^\circ) 50 + 7.19 \angle 0^\circ = 8.09 \angle 4.93^\circ \text{ V}$$

However, we earlier measured $V_{S,m} = 7.99 \text{ V}$. So, adjusting the magnitude while keeping the phase angle, yields

$$\Rightarrow \underline{\bar{V}_S = 7.99 \angle 4.93^\circ \text{ V}}$$

- 8) Make $v_S(t)$ the reference signal by subtracting 4.93° from all the phasor angles

$$\begin{aligned}\bar{V}_S &= 7.99 \angle (4.93 - 4.93)^\circ \text{ V} \Rightarrow \underline{\bar{V}_S = 7.99 \angle 0^\circ \text{ V}} \\ \bar{V}_{IN} &= 7.19 \angle (0 - 4.93)^\circ \Rightarrow \underline{\bar{V}_{IN} = 7.19 \angle -4.93^\circ \text{ V}} \\ \bar{V}_{R1} &= 5.61 \angle (38.56 - 4.93)^\circ \Rightarrow \underline{\bar{V}_{R1} = 5.61 \angle 33.63^\circ \text{ V}} \\ \bar{V}_C &= 4.49 \angle (-51.57 - 4.93)^\circ \Rightarrow \underline{\bar{V}_C = 4.49 \angle -56.50^\circ \text{ V}} \\ \bar{I} &= 22.308 \angle (38.56 - 4.93)^\circ \Rightarrow \underline{\bar{I} = 22.308 \angle 33.63^\circ \text{ mA}}\end{aligned}$$

- 9) Using \bar{V}_C , \bar{I} , and Ohm's Law, determine the impedance \bar{Z}_C and the measured phasor equivalent circuit:

$$\bar{Z}_C = \bar{V}_C / \bar{I} = (4.49 \angle -56.50^\circ) / (0.02231 \angle 33.63^\circ) \approx -0.46 - j201.25 \Omega$$

$$\text{Neglect small real part to get} \Rightarrow \underline{\bar{Z}_C = -j201.25 \Omega}$$

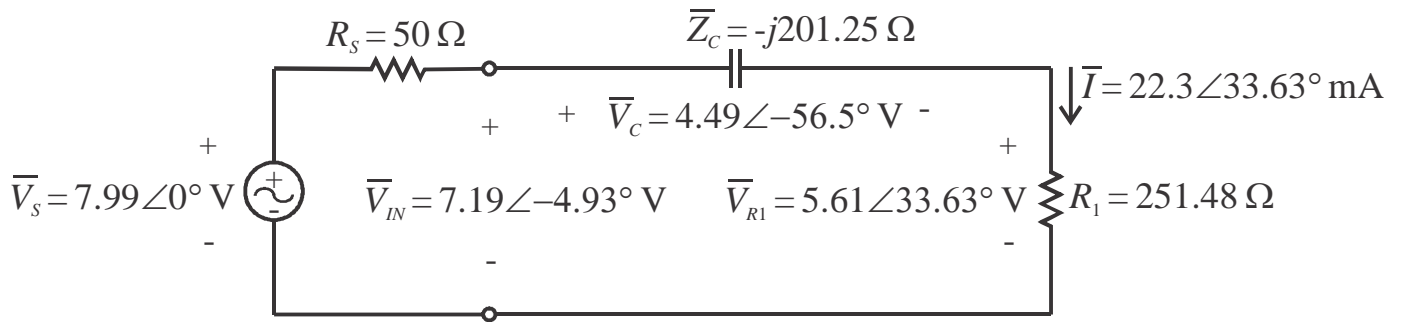


Figure 3 Measured phasor equivalent circuit

10) Using \bar{Z}_C , $\omega = 2\pi/T$, and the definition of the impedance of a capacitor, determine the measured capacitance C :

$$\bar{Z}_C = -j201.25 \Omega = \frac{-j}{\omega C} = \frac{-j}{(2\pi/T)C} = \frac{-j}{(2\pi/0.006283)C}$$

Solving for C , we get $\Rightarrow C = 4.969 \mu\text{F}$

11) Using the phasors, $\omega = 2\pi/T$, and Euler's identity, determine the measured time-domain circuit:

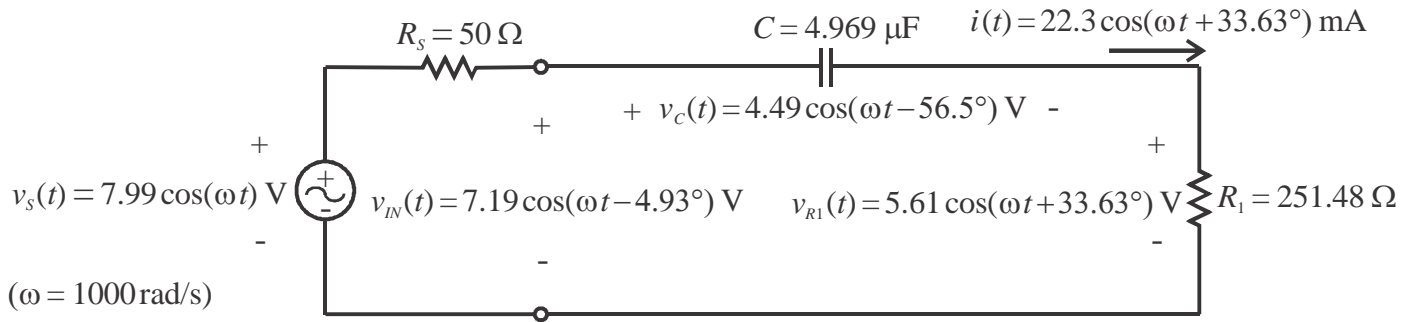


Figure 4 Measured time-domain circuit