

EE 220/220L Circuits I

Final Examination Review Topics



- This is NOT a complete list. Use as a starting point.

Chapter 1 Basic Concepts

- Units & prefixes:


| Prefix | Symbol | Multiplier | example |
|--------|--------|------------|------------------------------------|
| Tera- | T | 10^{12} | 2 THz = 2×10^{12} Hz |
| Giga- | G | 10^9 | 2.4 GHz = 2.4×10^9 Hz |
| Mega- | M | 10^6 | 101.9 MHz = 101.9×10^6 Hz |
| kilo- | k | 10^3 | 1340 kHz = 1340×10^3 Hz |
| centi- | c | 10^{-2} | 10 cm = 10×10^{-2} m |
| milli- | m | 10^{-3} | 90 mH = 90×10^{-3} mH |
| micro- | μ | 10^{-6} | 47 μ F = 47×10^{-6} F |
| nano- | n | 10^{-9} | 100 nH = 100×10^{-9} nH |
| pico- | p | 10^{-12} | 150 pF = 150×10^{-12} F |

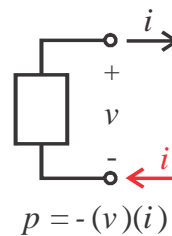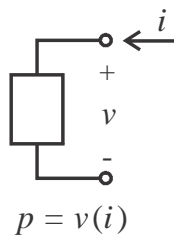- Charge $q = \int i dt$ (C)
- Current $i = dq/dt$ (A)
- Voltage $v_{ab} = dw/dq$ (V)
- Work: $w = \int p dt$ (J)
- Power $p = dw/dt = dw/dq \cdot dq/dt = v i$ (W)
- Conservation of power : $\sum_{\text{circuit}} p = 0$
- Passive sign convention for power absorbed (see below)- $p > 0 \Rightarrow$ element absorbs power and if $p < 0 \Rightarrow$ element supplies power



Chapter 2 Basic Laws

- Ohm's Law: $v = i R$ or $i = v G$
- Power & resistors: $p = v i = i^2 R = v^2 / R = i^2 / G = v^2 G$
- branches (b), nodes (n), & meshes/independent loops (l): $b = l + n - 1$
- Kirchoff's Current Law (KCL) : $\sum_{\text{node}} i_{\text{entering}} = 0$ or $\sum_{\text{node}} i_{\text{leaving}} = 0$ or $\sum_{\text{node}} i_{\text{entering}} = \sum_{\text{node}} i_{\text{leaving}}$
- Kirchoff's Voltage Law (KVL): $\sum_{\text{loop}} v_{\text{drops}} = 0$

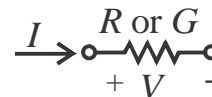


- Series resistors & voltage division: $R_{eq, Series} = \sum R_n$ & $v_n = v \frac{R_n}{R_{eq, S}}$
- Parallel resistors & current division: $R_{eq, Parallel} = \left[\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right]^{-1}$ & $i_n = i \frac{R_{eq, P}}{R_n} = i \frac{G_n}{G_{eq, P}}$
- Wye \leftrightarrow Delta transformations

| | | |
|---|---|---|
| | $\Delta \rightarrow Y$ | $Y \rightarrow \Delta$ |
| | $R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$ | $R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$ |
| | $R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$ | $R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$ |
| | $R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$ | $R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$ |
| | Balanced $\Delta \rightarrow Y$ | Balanced $Y \rightarrow \Delta$ |
| When $R_a = R_b = R_c = R_\Delta$, $R_Y = R_\Delta / 3$ | When $R_1 = R_2 = R_3 = R_Y$, $R_\Delta = 3R_Y$ | |

Chapter 3 Methods of Analysis


- Nodal Analysis
 - Designate reference node and label all other node voltages (e.g., V_1, V_2, \dots).
 - Apply KCL to all non-reference nodes, putting currents through resistors in terms of node voltages using Ohm's Law. Know how to deal with voltage sources (Case 1- $V_{node} = \pm V_S$ or Case 2- auxiliary & supernode equations). Express dependent sources in terms of node voltages.
 - Solve resulting set of equations for node voltages.
- Mesh Analysis
 - Select direction and label all mesh currents (e.g., I_1, I_2, \dots).
 - Apply KVL around meshes, putting voltage drops across resistors in terms of mesh currents using Ohm's Law. Know how to deal with current sources (Case 1- $I_{mesh} = \pm I_S$ or Case 2- auxiliary & supermesh equations). Express dependent sources in terms of mesh currents.
 - Solve resulting set of equations for mesh currents.
- DC npn bipolar junction transistor (BJT)

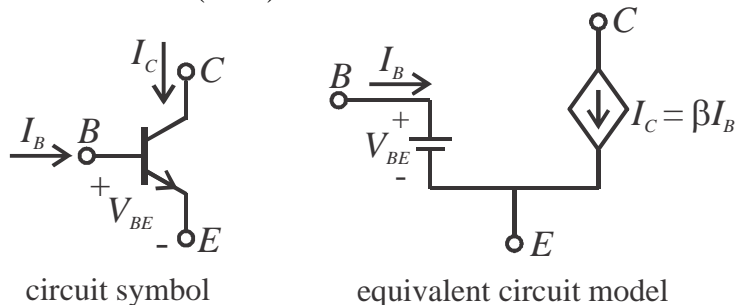


Chapter 4 Circuit Theorems

• Superposition Principle

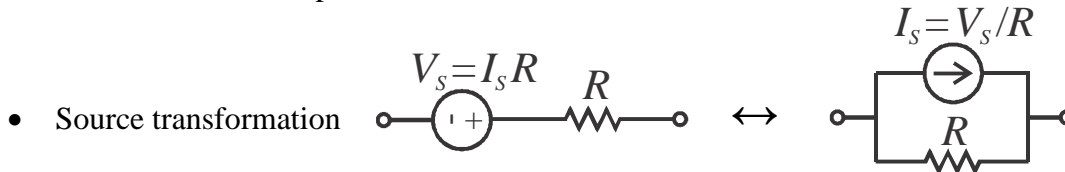
- 1) Set all independent sources to zero except one, i.e., $V_S = 0$ (short) and $I_S = 0$ (open). Leave dependent sources in circuit. Determine contributions to current(s) &/or voltage(s) of interest by this source using technique(s) of choice.
- 2) Repeat step 1) for all remaining independent sources.
- 3) Determine overall current(s) &/or voltage(s) by adding up contributions due to each of the individual independent sources.




- Thevenin's and Norton's Theorems. A linear two-terminal circuit can be replaced by a Thevenin or Norton equivalent circuit. The Thevenin voltage V_T is equal to the open circuit voltage at the terminals. The Norton current I_N is equal to the short circuit current between the terminals. The Thevenin R_T and Norton R_N resistances are the equivalent resistances at the terminals with independent sources turned off. Note: $R_T = R_N = V_T / I_N = v_{oc} / i_{sc}$

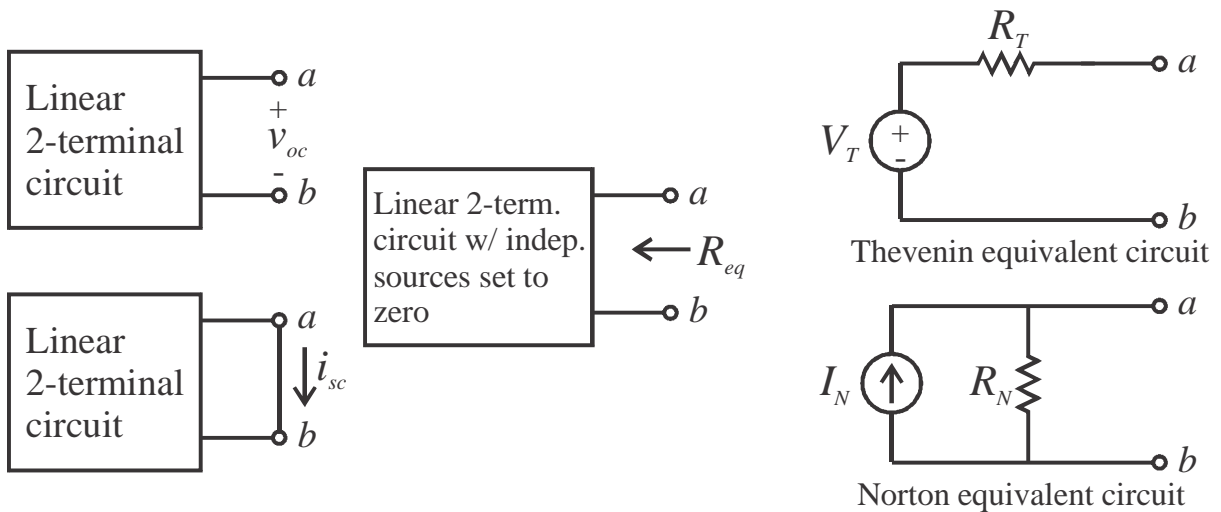

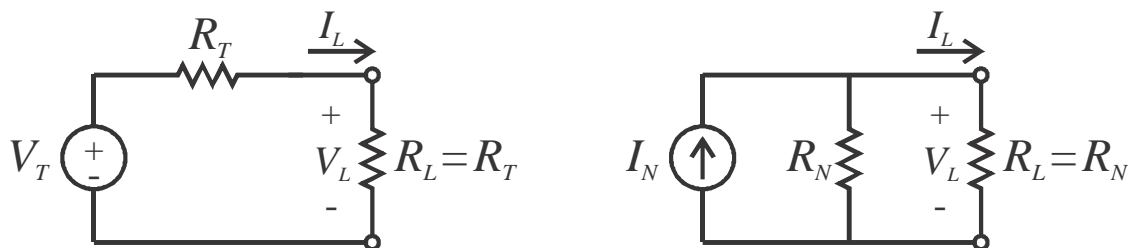- Maximum power transfer to load occurs when $R_L = R_T$ (when using Thevenin equivalent circuit), or $R_L = R_N$ (when using Norton equivalent circuit)



Chapter 5 Operational Amplifiers

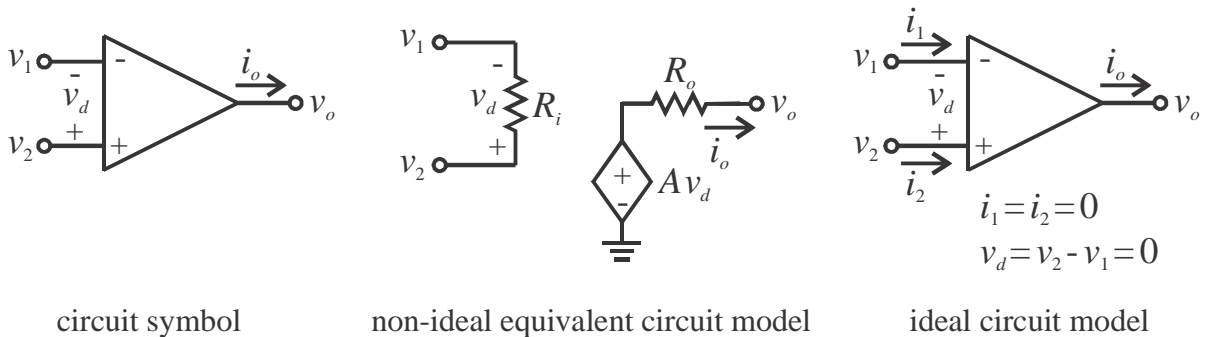


- Non-ideal op-amp equivalent circuit model where R_i is input resistance, R_o is output resistance, and A is open-loop voltage gain
- Know ideal op-amp circuit analysis both with single and multiple op-amps
- Know inverting, non-inverting, voltage follower, summing, difference, and instrumentation amplifier circuits.

Chapter 6 Capacitors and Inductors

- Capacitor: $q = Cv$, $i = C \frac{dv}{dt}$, $v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt = \frac{1}{C} \int_{t_0}^t i(t) dt + v(t_0)$, $w = \frac{1}{2} Cv^2 = \frac{q^2}{2C}$

- Capacitor properties:

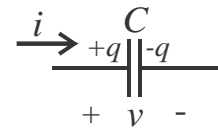- 1) Key parameters- capacitance C in Farads (F) & rated voltage
- 2) Open circuit at DC, i.e., $i = 0$, $v = ?$.
- 3) Voltage cannot change abruptly, but current can change quickly.
- 4) Ideal capacitors do not dissipate energy.
- 5) Parallel capacitors $C_{eq, parallel} = C_1 + C_2 + \dots + C_N$.




- 6) Series capacitors $C_{eq, series} = \left[\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right]^{-1}$ & voltage division $v_n = v \left(\frac{C_{eq, series}}{C_n} \right)$.

- Inductor: $v = L \frac{di}{dt}$, $i(t) = \frac{1}{L} \int_{-\infty}^t v(t) dt = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$, $w = \frac{1}{2} Li^2$

- Inductor properties:

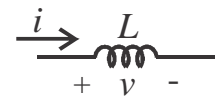- 1) Key parameters- inductance L in Henries (H) & rated current
- 2) Short circuit at DC, i.e., $v = 0$, $i = ?$.
- 3) Current cannot change abruptly.
- 4) Voltage can change quickly.
- 5) Ideal inductors do not dissipate energy.
- 6) Series inductors $L_{eq, series} = L_1 + L_2 + \dots + L_N$.



- 7) Parallel inductors $L_{eq, parallel} = \left[\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right]^{-1}$ & current division $i_n = i \left(\frac{L_{eq, parallel}}{L_n} \right)$.

Chapter 7 First-Order Circuits

- Source-free RC circuit analysis: $v(t) = V_0 e^{-t/\tau}$ $t \geq 0$ where V_0 is the initial voltage across the capacitor and time constant $\tau = RC$. R is equivalent resistance 'seen' by C .
- Source-free RL circuit analysis: $i(t) = I_0 e^{-t/\tau}$ $t \geq 0$ where I_0 is the initial current through the inductor and time constant $\tau = L/R$. R is equivalent resistance 'seen' by L .
- Step response RC circuit analysis: $v(t) = \begin{cases} V_0 & t < 0 \\ V_{SS} + V_0 - V_{SS} e^{-t/\tau} & t \geq 0 \end{cases}$ where $V_{SS} = v(\infty)$ is the steady-state voltage across the capacitor.
- Step response RL circuit analysis: $i(t) = \begin{cases} I_0 & t < 0 \\ I_{SS} + I_0 - I_{SS} e^{-t/\tau} & t \geq 0 \end{cases}$ where $I_{SS} = i(\infty)$ is the steady-state current through the inductor.
- Singularity/switching functions. In particular, unit step function $u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$.

Chapter 8 Second-Order Circuits

- Know how to determine initial & final conditions
- Source-free series RLC circuits: characteristic equation $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$
- Source-free parallel RLC circuits: characteristic equation $s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$
- Three solution forms for currents/voltages depending on roots of characteristic equation:

$$x(t) = \begin{cases} A_1 e^{s_1 t} + A_2 e^{s_2 t} & \text{overdamped (} s_1 \text{ \& } s_2 \text{ are real, negative, \& unequal)} \\ A_2 + A_1 t e^{-\alpha t} & \text{critically-damped (} s_1 = s_2 = -\alpha \text{ are real, negative, \& equal)} \\ e^{-\alpha t} (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)) & \text{underdamped (} s_{1/2} = -\alpha \pm j\omega_d \text{ are complex)} \end{cases}$$
- Step response parallel & series RLC circuits: current/voltage solution $x(t)$ consists of a forced response $x_f(t) = x_{SS} = x(\infty)$ (circuit at steady-state w/ source on) plus a natural response $x_n(t)$ (circuit w/ sources set to 0)

$$x(t) = x_f(t) + x_n(t) = \begin{cases} x_{SS} + A_1 e^{s_1 t} + A_2 e^{s_2 t} & \text{overdamped} \\ x_{SS} + A_2 + A_1 t e^{-\alpha t} & \text{critically-damped} \\ x_{SS} + e^{-\alpha t} (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)) & \text{underdamped} \end{cases}$$

- General second-order circuits (not included in final)

Chapter 9 Sinusoids and Phasors

- Sinusoids $x(t) = X_m \cos(\omega t + \theta) = X_m \sin(\omega t + \phi)$ - know what each of the components represents (e.g., $\omega = 2\pi f = 2\pi / T$) and how to convert from sin() form to cos() form
- Phasors $\bar{X} = X_m \angle \theta$ - complex number based on cos() form of sinusoid. Phasors allow for steady-state linear AC circuit analysis w/out need for difficult trigonometric identities.

- Phasor/frequency domain $\bar{X} = X_m \angle \theta \leftrightarrow$ time-domain $x(t) = \text{Re}\{\bar{X} e^{j\omega t}\} = X_m \cos(\omega t + \theta)$, using Euler's identity $e^{\pm jA} = \cos(A) \pm j \sin(A)$
- Impedance \bar{Z} (Ω) for $R, L,$ & C : $\bar{Z}_R = R$, $\bar{Z}_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$, & $\bar{Z}_L = j\omega L$
- Admittance \bar{Y} (S) for $R, L,$ & C : $\bar{Y}_R = \frac{1}{R} = G$, $\bar{Y}_C = j\omega C$, & $\bar{Y}_L = \frac{1}{j\omega L} = \frac{-j}{\omega L}$
- Phasor Ohm's Law $\bar{V} = \bar{I} \bar{Z}$ or $\bar{I} = \bar{V} \bar{Y}$
- Series equivalent impedances $\bar{Z}_{eq,S} = \bar{Z}_1 + \bar{Z}_2 \dots + \bar{Z}_N$ & voltage division $\bar{V}_n = \bar{V} \frac{\bar{Z}_n}{\bar{Z}_{eq,S}}$
- Parallel equivalent impedances $\bar{Z}_{eq,P} = \left[\frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} \dots + \frac{1}{\bar{Z}_N} \right]^{-1}$ & current division $\bar{I}_n = \bar{I} \frac{\bar{Z}_{eq,P}}{\bar{Z}_n}$
- Wye \leftrightarrow Delta impedance transformations

| | | |
|---|---|---|
| | $\Delta \rightarrow Y$ | $Y \rightarrow \Delta$ |
| | $\bar{Z}_1 = \frac{\bar{Z}_b \bar{Z}_c}{\bar{Z}_a + \bar{Z}_b + \bar{Z}_c}$ | $\bar{Z}_a = \frac{\bar{Z}_1 \bar{Z}_2 + \bar{Z}_2 \bar{Z}_3 + \bar{Z}_1 \bar{Z}_3}{\bar{Z}_1}$ |
| | $\bar{Z}_2 = \frac{\bar{Z}_a \bar{Z}_c}{\bar{Z}_a + \bar{Z}_b + \bar{Z}_c}$ | $\bar{Z}_b = \frac{\bar{Z}_1 \bar{Z}_2 + \bar{Z}_2 \bar{Z}_3 + \bar{Z}_1 \bar{Z}_3}{\bar{Z}_2}$ |
| | $\bar{Z}_3 = \frac{\bar{Z}_a \bar{Z}_b}{\bar{Z}_a + \bar{Z}_b + \bar{Z}_c}$ | $\bar{Z}_c = \frac{\bar{Z}_1 \bar{Z}_2 + \bar{Z}_2 \bar{Z}_3 + \bar{Z}_1 \bar{Z}_3}{\bar{Z}_3}$ |
| | Balanced $\Delta \rightarrow Y$ | Balanced $Y \rightarrow \Delta$ |
| When $\bar{Z}_a = \bar{Z}_b = \bar{Z}_c = \bar{Z}_\Delta$, $\bar{Z}_Y = \bar{Z}_\Delta / 3$ | When $\bar{Z}_1 = \bar{Z}_2 = \bar{Z}_3 = \bar{Z}_Y$, $\bar{Z}_\Delta = 3\bar{Z}_Y$ | |

- Kirchoff's Current Law (KCL) in phasor domain: $\sum_{\text{node}} \bar{I}_{\text{in}} = 0$, $\sum_{\text{node}} \bar{I}_{\text{out}} = 0$, or $\sum_{\text{node}} \bar{I}_{\text{in}} = \sum_{\text{node}} \bar{I}_{\text{out}}$
- Kirchoff's Voltage Law (KVL) in phasor domain: $\sum_{\text{loop}} \bar{V}_{\text{drops}} = 0$

Chapter 10 Sinusoidal Steady-State Analysis

- Nodal Analysis w/ phasors- same process/procedure as for DC circuits (see Chapter 3)
- Mesh Analysis w/ phasors- same process/procedure as for DC circuits (see Chapter 3)
- Superposition Theorem - nearly same process/procedure as for DC circuits (see Chapter 4) with caveat that all results found using phasors must be converted back into time-domain before adding them up.
- Source Transformation w/ phasors- same process/procedure as for DC circuits (see Chapter 4)
- Thevenin and Norton Equivalent Circuits w/ phasors- same process/procedure as for DC circuits (see Chapter 4)


Chapter 11 AC Power Analysis

- Instantaneous Power $p(t) = v(t) i(t)$ (W)
- Effective/RMS values: $X_{\text{RMS}} \equiv \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} [x(t)]^2 dt}$. For a sinusoidal current or voltage
 $x(t) = X_m \cos(\omega t + \theta) \Rightarrow X_{\text{RMS}} = X_m / \sqrt{2}$
- Time-average real power $P_{\text{ave}} = \frac{1}{T} \int_0^T p(t) dt$ (W) in general. For sinusoidal steady-state circuits:


$$\begin{aligned} P_{\text{ave}} &= 0.5 V_m I_m \cos(\theta_V - \theta_I) = V_{\text{rms}} I_{\text{rms}} \cos(\theta_V - \theta_I) \\ &= 0.5 \text{Re}[\bar{V} \bar{I}^*] = \text{Re}[\bar{V}_{\text{rms}} \bar{I}_{\text{rms}}^*] \\ &= 0.5 |\bar{I}|^2 \text{Re} \bar{Z} = I_{\text{rms}}^2 \text{Re} \bar{Z} \text{ (W)} \end{aligned}$$

- Maximum average power transfer occurs when $\bar{Z}_L = \bar{Z}_T^*$ where \bar{Z}_T is the Thevenin impedance of the source
- Apparent power $S = V_{\text{rms}} I_{\text{rms}} = 0.5 V_m I_m$ (VA)
- Power factor $pf = P_{\text{ave}} / S = \cos(\theta_V - \theta_I) = \cos(\theta_z) = \cos(\theta_S)$ **leading** if $\theta_z < 0$ & **lagging** if $\theta_z > 0$
- Complex power $\bar{S} = S \angle \theta_s = P_{\text{ave}} + jQ = 0.5 \bar{V} \bar{I}^* = \bar{V}_{\text{rms}} \bar{I}_{\text{rms}}^*$ (VA) where $P_{\text{ave}} \equiv$ time-average real power = $\text{Re} \bar{S}$ (W) and $Q \equiv$ reactive power = $\text{Im} \bar{S}$ (VAR)
- Power triangle

Resistive-inductive load
(lagging pf)

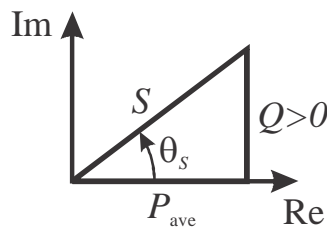

Resistive-inductive load
(leading pf)

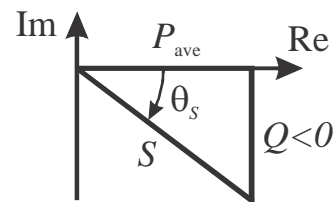

- Conservation of AC power $\sum \bar{S}_{\text{supplied}} = \sum \bar{S}_{\text{absorbed}}$
- Power factor correction (not included in final)