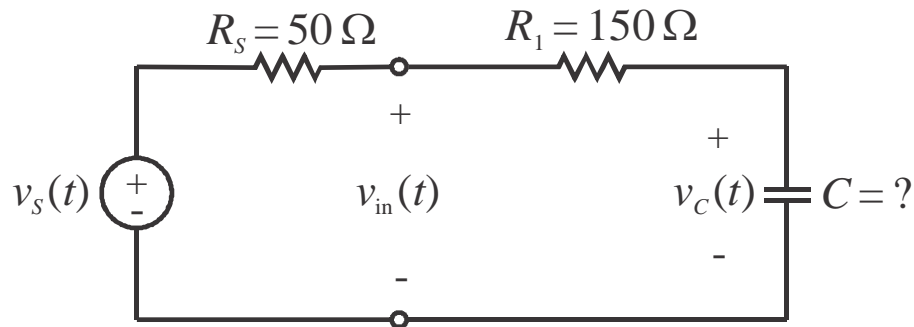


In the lab, the first-order  $RC$  circuit was set up with  $v_S(t) = 8 [u(t) - u(t - 6 \text{ ms})]$  V and the known/nominal component values shown.

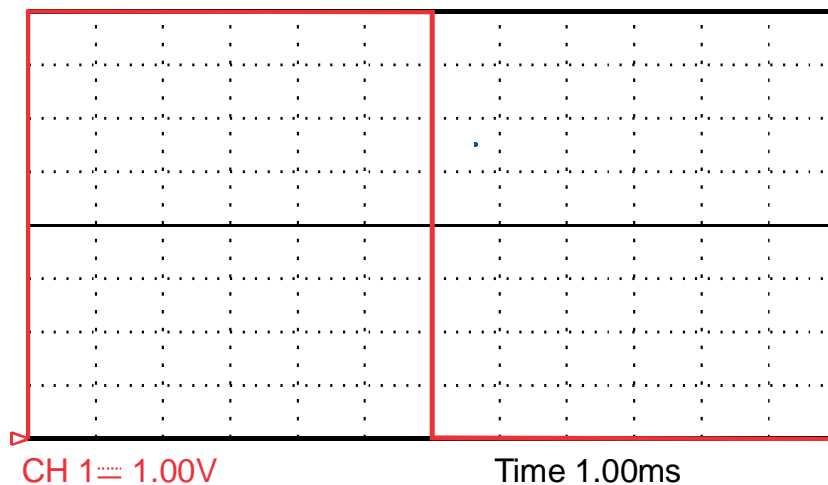


**Figure 1** First-order  $RC$  circuit

We will use experimental measurements to determine the time-constant  $\tau_{RC}$  for the capacitor voltage  $v_C(t)$  waveform. This measured time-constant  $\tau_{RC}$  and the known/measured resistor/resistance values will be used to determine the unknown capacitance  $C$ .


### Steps

- 1) Assume that  $\underline{R_S = 50 \Omega}$  as specified by function generator manual.
- 2) Use a digital multimeter to measure the resistance of resistor  $\underline{R_1 = 146.87 \Omega}$ .
- 3) Connect the function generator directly to channel 1 of the oscilloscope to set up  $v_S(t)$ . The screen display is shown below. [Note ‘CH 1 1.00V’ means 1 V per division in the vertical direction and ‘Time 1.00ms’ means 1 ms per division in the horizontal direction.]



Using the oscilloscope measurements menu, determine that the minimum voltage is 0.00 V, maximum voltage is 8.00 V, pulse width is 6.00 ms and period is 12.00 ms.

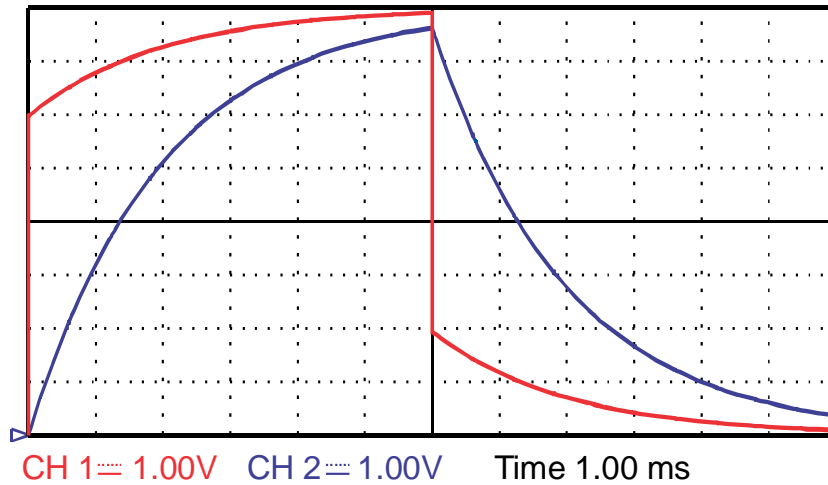- 4) Connect circuit shown in Figure 1. Then, connect the oscilloscope to measure  $v_{IN}(t)$  [CH 1- blue line] &  $v_C(t)$  [CH 2- red line] with the screen display shown below. Note that  $v_{IN}(t) \neq v_S(t)$  due to the voltage drop across  $R_S$ .



Using the oscilloscope cursors menu, measure the  $v_C(t)$  at 1 ms intervals (i.e., where the  $v_C(t)$  trace crosses the dashed vertical lines).

**Table 1** Measured capacitor voltages versus time

Time (ms)	$v_C$ (V)	Time (ms)	$v_C$ (V)
0	0	7	4.60
1	3.15	8	2.78
2	5.12	9	1.66
3	6.24	10	0.98
4	6.96	11	0.66
5	7.44	12	0.38
6	7.68		

- 5) For  $t \geq 6$  ms, the capacitor voltage decays in the mathematical form

$$v_C(t) = v_C(6 \text{ ms}) e^{-(t-0.006)/\tau} = 7.68 e^{-(t-0.006)/\tau} \text{ V } t \geq 6 \text{ ms.}$$

Doing a time-shift (i.e., treat  $t = 6$  ms as  $t = 0$ ), this equation can be put in form

$$v_C(t) = V_0 e^{-t/\tau} = 7.68 e^{-t/\tau} \text{ V } t \geq 0$$

where  $V_0$  is the peak voltage of  $v_C(t)$ . We can solve for the time constant

$$\tau_{RC, \text{meas}} = \frac{-\Delta t}{\ln(v_C(\Delta t)/V_0)}$$

by choosing measured voltage data points  $v_C(\Delta t)$  where  $t = \Delta t$  is the time interval between the peak voltage  $V_0$  and the measured voltage(s)  $v_C(\Delta t)$ .

To try to minimize measurement errors, we will solve for the time constant using several data points and take an average.

$$\tau_{RC,1} = \frac{-1\text{ms}}{\ln(v_c(1\text{ms})/V_0)} = \frac{-1e-3}{\ln(4.60/7.68)} = 1.951e-3 \text{ s} \Rightarrow \underline{\tau_{RC,1} = 1.951 \text{ ms}},$$

$$\tau_{RC,2} = \frac{-2\text{ms}}{\ln(v_c(2\text{ms})/V_0)} = \frac{-2e-3}{\ln(2.78/7.68)} = 1.968e-3 \text{ s} \Rightarrow \underline{\tau_{RC,2} = 1.968 \text{ ms}}, \text{ and}$$

$$\tau_{RC,3} = \frac{-3\text{ms}}{\ln(v_c(3\text{ms})/V_0)} = \frac{-3e-3}{\ln(1.66/7.68)} = 1.9585e-3 \text{ s} \Rightarrow \underline{\tau_{RC,3} = 1.9585 \text{ ms}}$$

$$\tau_{RC} = (1.951 + 1.968 + 1.9585)/3 \Rightarrow \underline{\tau_{RC} = 1.96 \text{ ms}}$$

- 6) Next, we can use the definition of the  $RC$  circuit time constant  $\tau_{RC}$  and the known/measured resistor values to determine the unknown capacitance  $C$ .

$$\tau_{RC} = RC \Rightarrow C = \tau_{RC}/R$$


where  $R$  is the equivalent resistance ‘seen’ by the capacitor in Figure 1. Solving for the capacitance  $C$ , we get

$$\begin{aligned} C &= \tau_{RC}/R = \tau_{RC}/(R_1 + R_S) \\ &= 1.96 \text{ ms} / (146.87 + 50) \\ &= 0.00196 / 196.87 \end{aligned}$$

$$\Rightarrow \underline{C = 0.000009956 \text{ F} = 9.956 \mu\text{F}}$$

Apparently, our capacitor had a  $10 \mu\text{F}$  nominal/rated value.

- 7) Last, we can now draw our actual  $RC$  circuit with the measured component values as shown below in Figure 2.

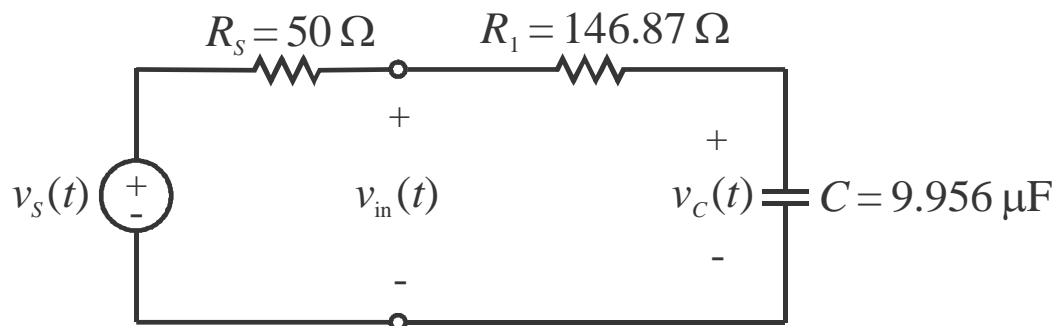

**Figure 2** Measured first-order  $RC$  circuit