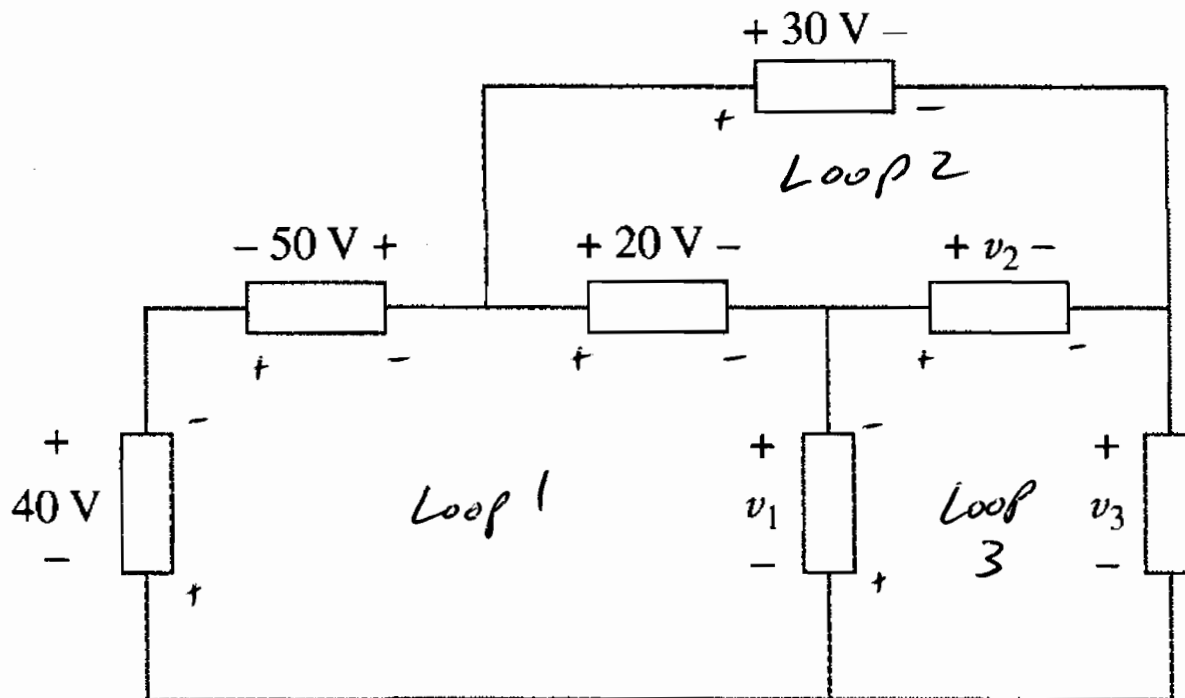


2.12 In the circuit, obtain v_1 , v_2 , and v_3 . Use KVL.



$$\text{Loop 1: } -40V - 50V + 20V + v_1 = 0$$

$$\hookrightarrow \underline{\underline{v_1 = 70V}}$$

$$\text{Loop 2: } 30V - v_2 - 20V = 0$$

$$\underline{\underline{v_2 = 10V}}$$

$$\text{Loop 3: } -v_1 + v_2 + v_3 = 0$$

$$v_3 = v_1 - v_2 = 70 - 10$$

$$\underline{\underline{v_3 = 60V}}$$