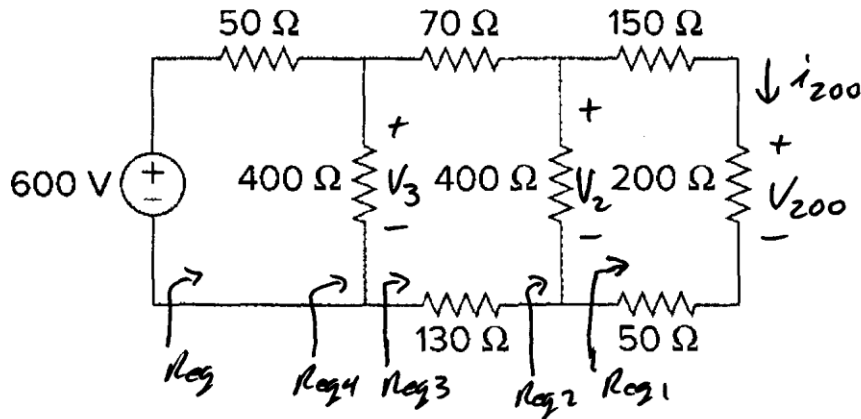


**2.34** Using series/parallel resistance combination, find the equivalent resistance seen by the source in the circuit. Find the overall absorbed power by the resistor network.




- Also, find the equivalent conductance  $G_{eq}$  seen by the voltage source as well as the current through and voltage across the 200 Ω resistor.

Series  $R_{eq1} = 150 + 200 + 50 = 400\Omega$

parallel  $R_{eq2} = 400 \parallel R_{eq1} = \left[ \frac{1}{400} + \frac{1}{400} \right]^{-1} = 200\Omega$


↓ Reduced circuit

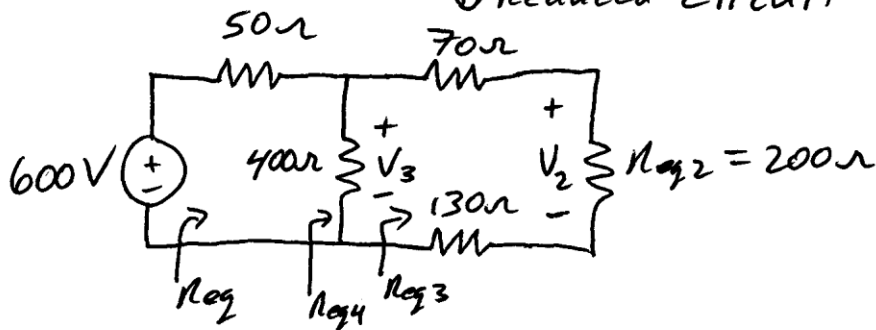

Series  $R_{eq3} = 70 + R_{eq2} + 130 = 70 + 200 + 130 = 400\Omega$

parallel  $R_{eq4} = 400 \parallel R_{eq3} = \left[ \frac{1}{400} + \frac{1}{400} \right]^{-1} = 200\Omega$

↓ Reduced circuit

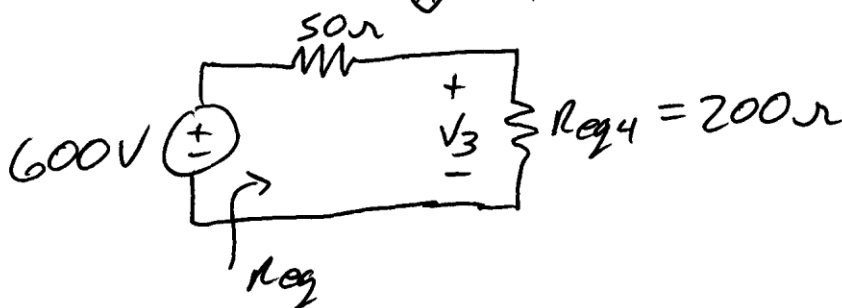

series  $R_{eq} = 50 + R_{eq4} = 50 + 200 \Rightarrow \underline{\underline{R_{eq} = 250 \Omega}}$

$$G_{eq} = \frac{1}{R_{eq}} = \frac{1}{250} = 0.004 \text{ S} \Rightarrow \underline{\underline{G_{eq} = 4 \text{ mS}}}$$

Overall power  $P = \frac{600^2}{R_{eq}} = \frac{600^2}{250} = \underline{\underline{1440 \text{ W} = 1.44 \text{ kW}}}$

Use voltage division to calculate  $V_3$ .

$$V_3 = 600 \text{ V} \frac{R_{eq4}}{R_{eq}} = 600 \left( \frac{200}{250} \right) = 480 \text{ V}$$

Use voltage division to calculate  $V_2$ .

$$V_2 = V_3 \frac{R_{eq2}}{R_{eq3}} = 480 \frac{200}{400} = 240 \text{ V}$$

Use voltage division to calculate  $V_{200}$ .

$$V_{200} = V_2 \frac{200 \Omega}{R_{eq1}} = 240 \frac{200}{400}$$

$$\underline{\underline{V_{200} = 120 \text{ V}}}$$

Use Ohm's Law to get  $i_{200}$ .

$$i_{200} = \frac{V_{200}}{200} = \frac{120}{200}$$

$$\underline{\underline{i_{200} = 0.6 \text{ A} = 600 \text{ mA}}}$$