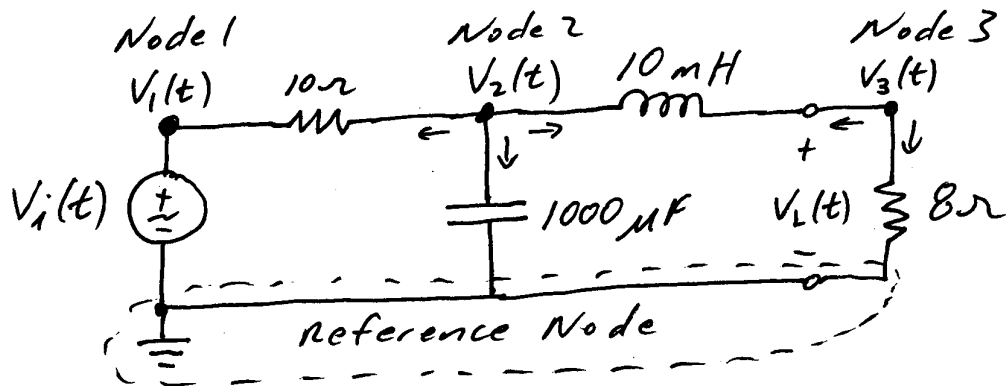


Ex. Find I/O differential equation for the lowpass filter (part of a stereo speaker crossover network) shown.



Define: input $x(t) = V_i(t)$
output $y(t) = V_L(t)$

Apply KCL/Nodal Analysis

$$\text{Node 1: } V_1(t) = V_i(t) = x(t) \quad (1)$$

$$\text{Node 2: } \frac{V_2(t) - V_1(t)}{10} + 1000 \times 10^{-6} \frac{d(V_2(t) - 0)}{dt} + \frac{1}{10 \times 10^{-3}} \int_{-\infty}^t [V_2(\lambda) - V_3(\lambda)] d\lambda = 0 \quad (2)$$

$$\text{Node 3: } \frac{1}{10 \times 10^{-3}} \int_{-\infty}^t [V_3(\lambda) - V_2(\lambda)] d\lambda + \frac{V_3(t) - 0}{8} = 0 \quad (3)$$

To avoid an integro-differential equation, take $\frac{d}{dt}$ of equations (2) and (3).

$$0.1 \frac{dV_2}{dt} - 0.1 \frac{dx}{dt} + 0.001 \frac{d^2 V_2}{dt^2} + 100 V_2(t) - 100 y(t) = 0 \quad (2)'$$

$$100 y(t) - 100 V_2(t) + 0.125 V_3(t) = 0 \quad (3)'$$

Use (3)' to find V_2 , $\frac{dV_2}{dt}$, + $\frac{d^2V_2}{dt^2}$ in terms of y

$$V_2 = \frac{1}{100} \left[100y + 0.125 \frac{dy}{dt} \right] = y + 0.00125 \frac{dy}{dt} \quad (a)$$

$$\frac{d}{dt} \hookrightarrow \frac{dV_2}{dt} = \frac{dy}{dt} + 0.00125 \frac{d^2y}{dt^2} \quad (b)$$

$$\frac{d}{dt} \hookrightarrow \frac{d^2V_2}{dt^2} = \frac{d^2y}{dt^2} + 0.00125 \frac{d^3y}{dt^3} \quad (c)$$

Substitute equations (a), (b), & (c) into (2)'

$$0.1 \left(\frac{dy}{dt} + 0.00125 \frac{d^2y}{dt^2} \right) - 0.1 \frac{dx}{dt} + 0.001 \left(\frac{d^2y}{dt^2} + 0.00125 \frac{d^3y}{dt^3} \right)$$

$$100 \left(y + 0.00125 \frac{dy}{dt} \right) - 100y = 0$$

↓ gather terms & re-arrange

$$1.25 \times 10^{-6} \frac{d^3y}{dt^3} + 1.125 \times 10^{-3} \frac{d^2y}{dt^2} + 0.225 \frac{dy}{dt} = 0.1 \frac{dx}{dt}$$

Since the $y(t)$ terms cancelled, integrate &

divide by 1.25×10^{-6} to get

$$\frac{d^2y}{dt^2} + 900 \frac{dy}{dt} + 180,000 y = 80,000 x$$

The analysis yielded a 2nd order ODE.