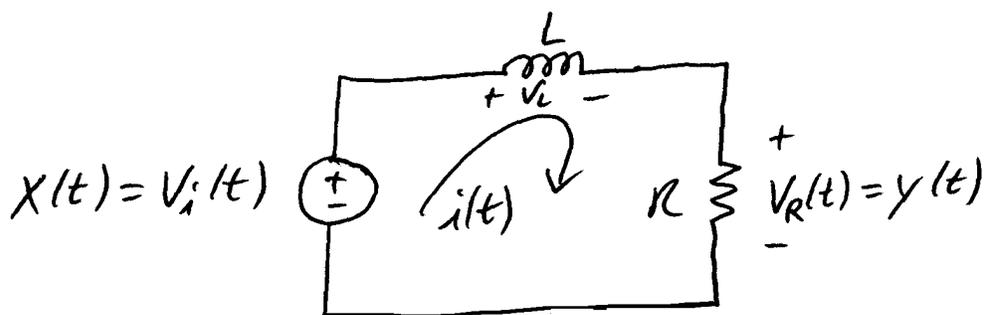


ex. Impulse Response - Series RL Circuit



To get $h(t)$, the impulse response, we'll first determine the unit step response $g(t)$.

From Circuits I, $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$ $t \geq 0$
for a step input $\tau = L/R$

* Since $V_i(t) = u(t) = 0$ for $t < 0$, $i(0^-) = 0$

For inductors, the current can not change instantaneously. So, $i(0) = i(0^-) = \underline{0}$

* As $t \rightarrow \infty$, the circuit is in a steady-state.

Therefore, $V_L(t) = L \frac{di}{dt} = 0 \Rightarrow i'(t \rightarrow \infty) = \frac{V_i(t)}{R} = \underline{\frac{1}{R}}$

So, $i(t) = \frac{1}{R} + [0 - \frac{1}{R}]e^{-t/(L/R)} = \frac{1}{R} - \frac{1}{R}e^{-t/(L/R)}$ $t \geq 0$

By Ohm's Law, $V_R(t) = i(t)R = 1 - e^{-t/(L/R)}$ $t \geq 0$

For a step input, $x(t) = u(t)$ and $y(t) = V_R(t) = g(t)$

ex. cont.


$$g(t) = 1 - e^{-t/(4R)} \quad (V) \quad t \geq 0$$

$$= 0 \quad t < 0$$



Using the derivative property of convolution

$$h(t) = \frac{dg(t)}{dt} = \frac{d\{1 - e^{-t/(4R)}\}}{dt} = 0 - e^{-t/(4R)} \left(\frac{-1}{(4R)}\right)$$


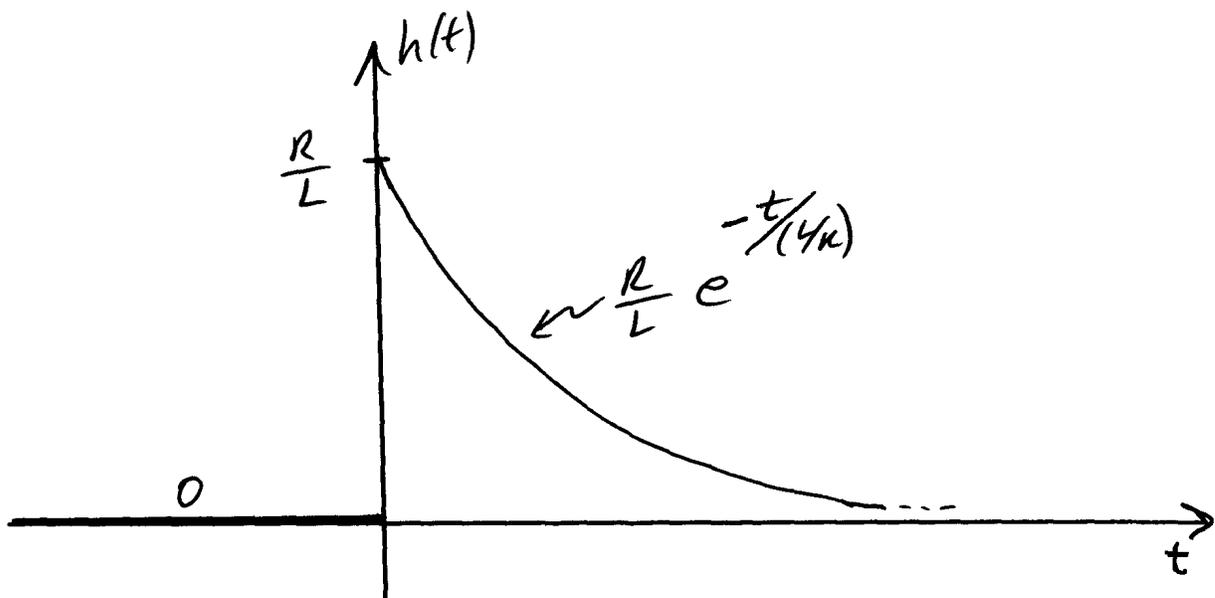
$$h(t) = \begin{cases} \frac{R}{L} e^{-t/(4R)} \quad (V/s) \quad t \geq 0 \\ 0 \quad t < 0 \end{cases}$$



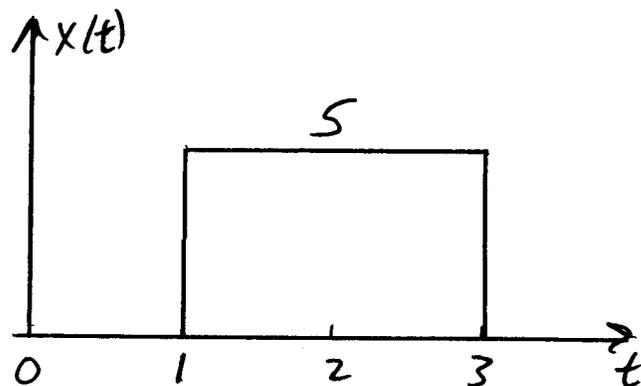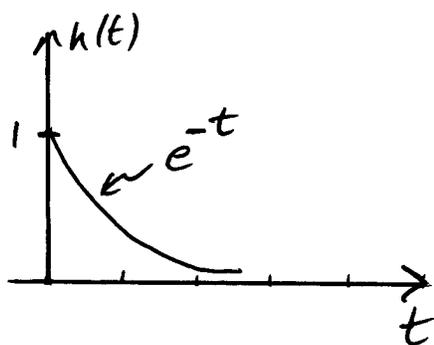
Find the output of the series RL circuit to the input $x(t) = 5p_2(t-2)$ V when $R=1\Omega$ and $L=1$ H.


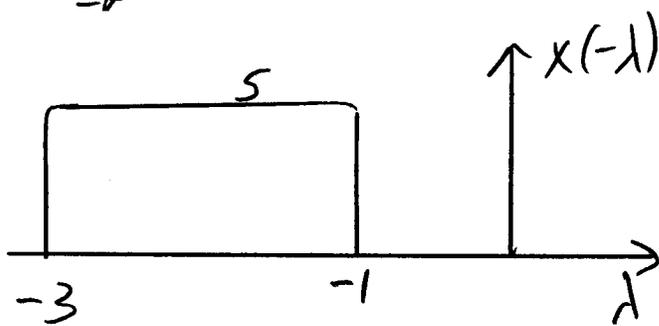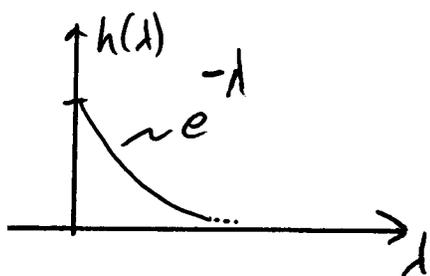
$$y(t) = x(t) * h(t) = h(t) * x(t) = \int_{-\infty}^{\infty} h(\lambda) x(t-\lambda) d\lambda$$



↓ Time-shift by t

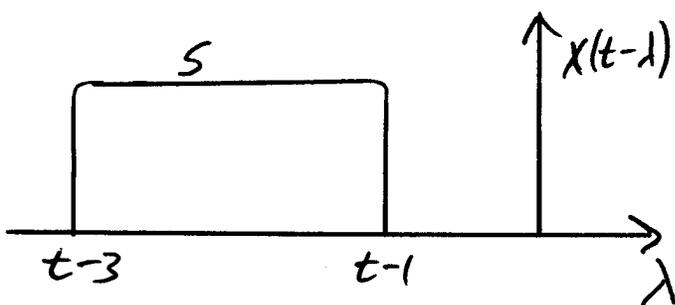


Time Interval $t < 1$ s

$h(\lambda)$ & $x(t-\lambda)$ do Not overlap, i.e., $h(\lambda)x(t-\lambda) = 0$

$$y(t < 1s) = \int_{-\infty}^{\infty} 0 d\lambda = \underline{\underline{0}}$$

ex. cont.

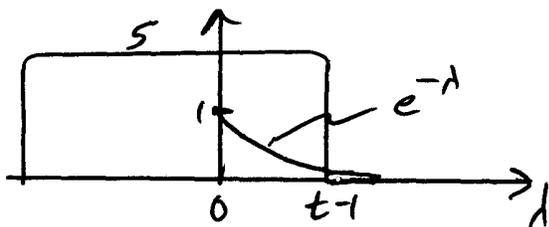Time Interval $1 \leq t < 3s$ As shown, the leading edge of $x(t-d)$ overlaps $h(d)$ 


$$y(1 \leq t < 3) = \int_0^{t-1} e^{-\lambda} (5) d\lambda = -5e^{-\lambda} \Big|_0^{t-1}$$

$$= -5e^{-(t-1)} + 5e^0 = -5e^{-t} + 5$$

$$\underline{y(1 \leq t < 3s) = 5[1 - e^{-(t-1)}]}$$

Time Interval $t \geq 3s$

The signals fully overlap

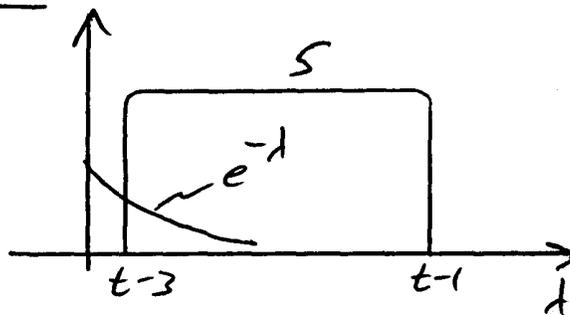

$$y(t \geq 3s) = \int_{t-3}^{t-1} e^{-\lambda} (5) d\lambda = -5e^{-\lambda} \Big|_{t-3}^{t-1}$$

$$= -5e^{-(t-1)} + 5e^{-(t-3)} = -5e^{-t} e^1 + 5e^{-t} e^3$$


$$\underline{y(t \geq 3s) = 5e^{-t} [e^3 - e^1]}$$

```

% chap2_series_RL_convolution_response.m
% CT Convolution Example
% Plot the result of the CT convolution
%  $y(t) = x(t) * h(t)$  where
%  $x(t) = 5p_2(t-2)$  and
%  $v(t) = e^{(-t/\tau)}u(t)$  where  $\tau = R/L$ 
%
clear; clc; close all;
R = 1; L = 1; tau = R/L;
t0 = -2:0.025:1; t1 = 1:0.025:3; t2 = 3:0.025:8;
x0 = 0*t0; x1 = 5*ones(1,length(t1)); x2 = 0*t2;
y0 = 0*t0; y1 = 5*(1-exp(-t1+1)); y2 = 5*exp(-t2)*(exp(3)-exp(1));
t = [t0 t1 t2]; x = [x0 x1 x2]; y = [y0 y1 y2];
for i=1:length(t),
    if(t(i)<0),
        h(i) = 0;
    else
        h(i) = R/L*exp(-t(i)/(L/R));
    end
end
end
plot(t,x,'r-'), axis([-2 8 0 6]),
ylabel('\itx}(\itt)', 'fontsize',14,'fontname','times'),
xlabel('\itt} (s)', 'fontsize',14,'fontname','times'),
title({'Series RL Circuit Convolution Example',...
    'Input Signal {\itx}(\itt) = 5{\itp}_2(\itt-2)',...
    'fontsize',16,'fontname','times')},...
figure, plot(t,h,'r-'), axis([-2 8 0 1.1]),
ylabel('\ith}(\itt)', 'fontsize',14,'fontname','times'),
xlabel('\itt} (s)', 'fontsize',14,'fontname','times'),
title({'Series RL Circuit Convolution Example',...
    'Impulse Response {\ith}(\itt) = e^{-\itt} {\itu}(\itt)',...
    'fontsize',16,'fontname','times')},...
figure,plot(t,y,'r-'), axis([-2 8 0 5]),
ylabel('\ity}(\itt)', 'fontsize',14,'fontname','times'),
xlabel('\itt} (s)', 'fontsize',14,'fontname','times'),
title({'Series RL Circuit Convolution Example',...
    'Output Signal {\ity}(\itt) = {\itx}(\itt) *
{\ith}(\itt)'},...
    'fontsize',16,'fontname','times')},...
text(-0.4,3,'5 [1-e^{-(\itt)-1}]', 'fontsize',14,'fontname','times')
text(3.7,3,'5 e^{-\itt} [e^3 -
e^1]', 'fontsize',14,'fontname','times')
set(findobj('type','line'),'linewidth',2,'markersize',18)
set(findobj('type','axes'),'linewidth',2,'fontname','times')

```

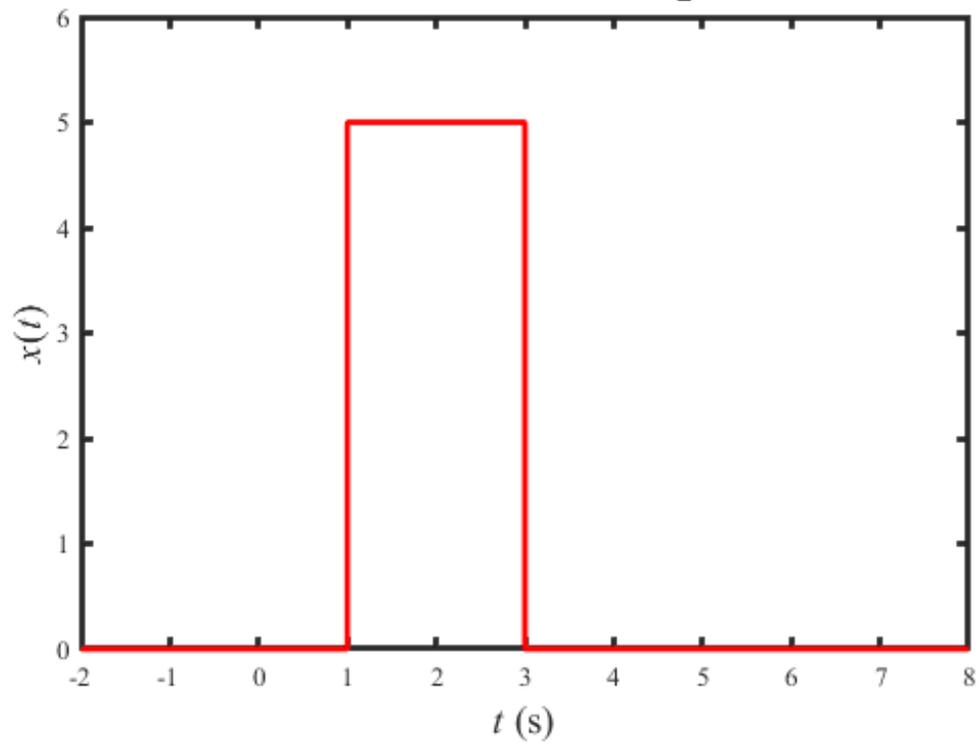Series RL Circuit Convolution Example
Input Signal $x(t) = 5p_2(t-2)$



Series RL Circuit Convolution Example
Impulse Response $h(t) = e^{-t} u(t)$

