

EE 313 Signals and Systems (Fall 2024)

Project 2 Fourier Analysis of Systems- AC/DC Rectification, Part B

Introduction

<snip> selected between <snip> half-wave rectifying <snip> and full-wave rectifying circuit <snip>

In Part B of this project, we will explore how to make our choice of rectifying circuit suitable for a DC power supply. An inexpensive and effective option to implement a DC power supply is to add a capacitor C in parallel with the load resistance R_L <snip> the capacitor acts as a lowpass filter <snip>

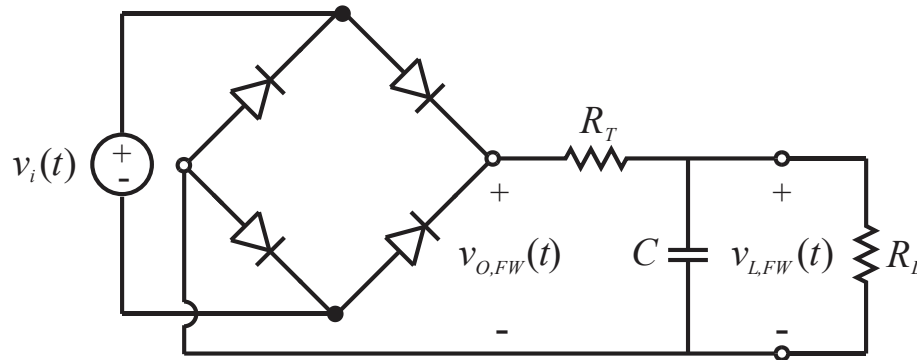


Figure 2 Modified full-wave rectifying circuit with lowpass filtering

Project

Per part A of the project, $v_i(t) = V_m \cos(\omega t)$ w/ $V_m = 176 \text{ V}$, $f = 400 \text{ Hz}$, $T = 1/f$, $R_T = 4 \Omega$, and $R_L = 4 \Omega$.

- 1) Based on the type of rectification selected in part A of the project, select <snip> Figure 2 (**xx = FW**), Then, complete the following:

- a) Find the general <snip> frequency domain transfer function <snip>, i.e., $H_3(\omega) = \frac{V_{L,xx}(\omega)}{V_{O,xx}(\omega)}$.

The relation between $V_{L,FW}$ and $V_{O,FW}$ is found by simple voltage division in the frequency-domain

$$V_{L,FW}(\omega) = \frac{\left(\frac{1}{j\omega C} \parallel R_L \right)}{R_T + \left(\frac{1}{j\omega C} \parallel R_L \right)} V_{O,FW}(\omega).$$

After some simplification, the transfer function is found to be:



$$H_3(\omega) = \frac{V_{L,FW}(\omega)}{V_{O,FW}(\omega)} = \frac{R_L}{(R_L + R_T) + j\omega R_L R_T C} = \frac{1}{(1 + R_T / R_L) + j\omega R_T C} \quad -\infty < \omega < \infty.$$

- b) Assuming $C = 500 \mu\text{F}$ and the given resistor values, find the specific transfer function $H_3(\omega)$.

$$H_3(\omega) = \frac{R_L}{(R_L + R_T) + j\omega R_L R_T C} = \frac{4}{(4 + 4) + j\omega 4(4) 500 \cdot 10^{-6}}$$



$$H_3(\omega) = \frac{4}{8 + j\omega 0.008} = \frac{1}{2 + j\omega 0.002} = \frac{0.5}{1 + j\omega 0.001} \quad -\infty < \omega < \infty$$

- c) **<snip>** plot **<snip>** $|H_3(\omega)|$ (unitless, 0 to 0.55 vertical scale) and $|H_3(\omega)|$ (dB, 0 to -40 vertical scale) for $0 \leq \omega \leq 6.8\omega_{0,\text{FW}}$ (2 plots). Also, evaluate **<snip>** $H_3(\omega_k)$ for $0 \leq k \leq 6$, and place **labeled** markers (dots) corresponding to $|H_3(\omega_k)|$ on the same plots. Include m-file.

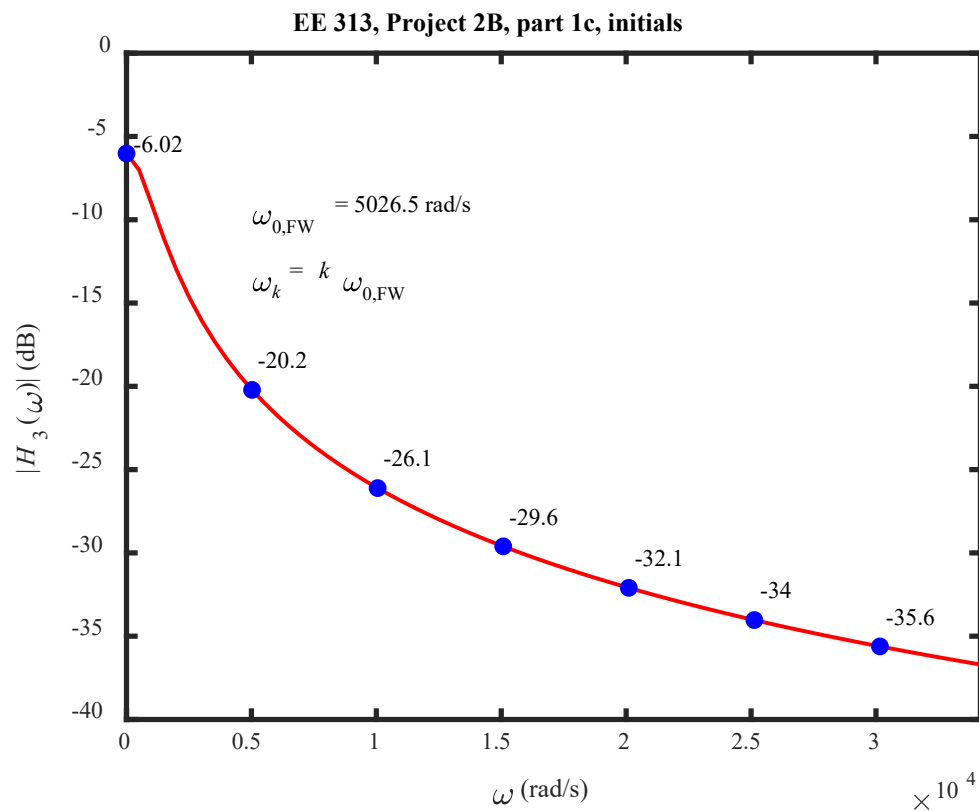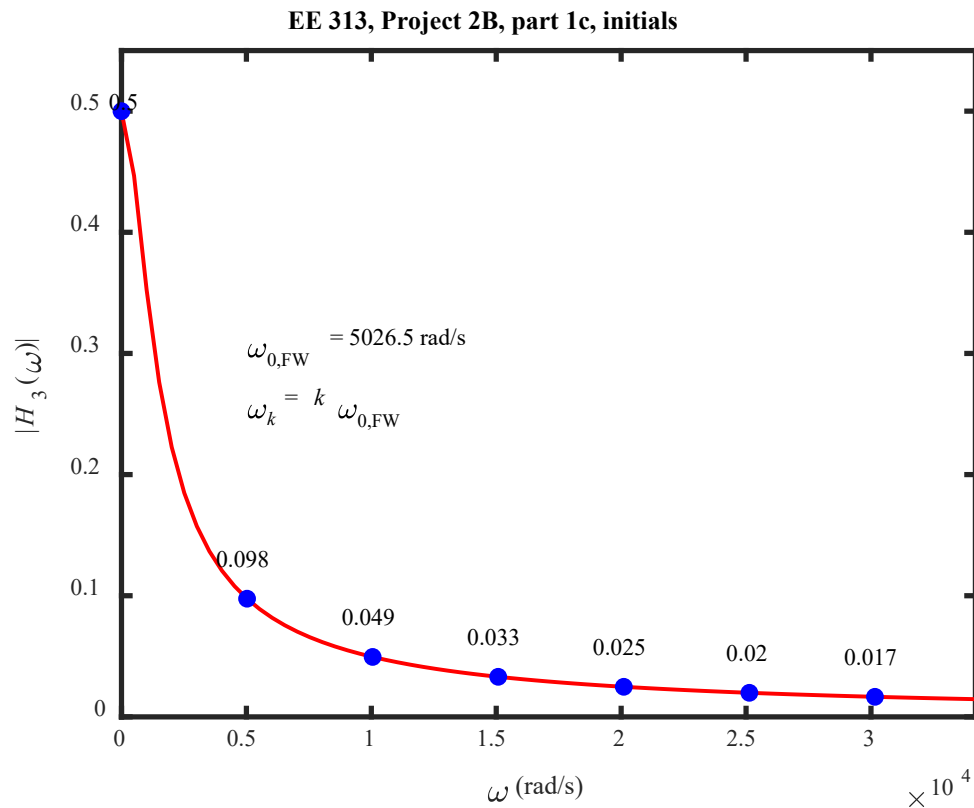

<snip>

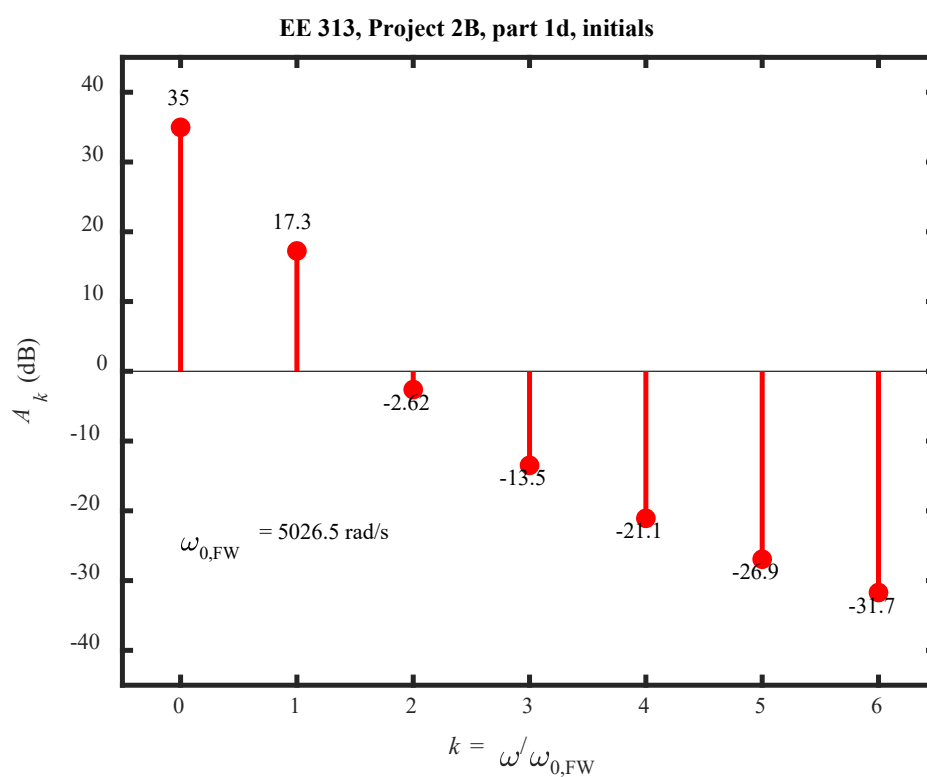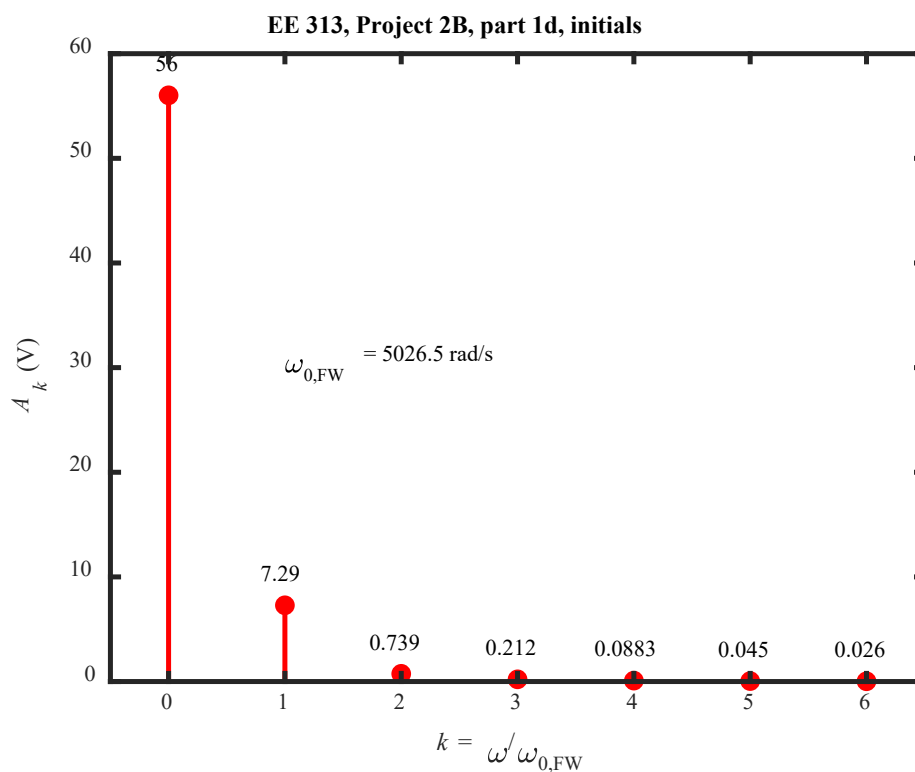- d) <snip> create two stem plots of the filtered **amplitude**/ A_k (vertical scale of 0 to 60 V) line spectra for $v_{L,ex}(t)$ versus <snip> ω_k , i.e., $0 \leq k \leq 6$ with horizontal scale ranging from -0.5 to 6.5 <snip> Next, create a stem plot of the **amplitude**/ A_k line spectra in decibels ($-45 \leq \text{dB} \leq 45$) with same horizontal scale. For all plots, label all stems. Include m-file(s).



<snip>

- e) Estimate the total power $P_{L,FW}$ in the filtered load voltage by adding the power in the dc plus first ten harmonics. For the three largest line spectra, fill-in the table below. What fraction of the total power is contained in these three?

Table 1 Power in three largest line spectra for filtered full-wave rectification

harmonic #	f (Hz)	amplitude (V)	P (W)	% of $P_{L,xx}$
0	0	56.02254	784.631246	99.151621
1	800	7.287407	6.638287	0.8388615
2	1600	0.739373	0.068334	0.008635

➤ $P_{L,FW} \cong 791.344849$ W of which the first three account for 99.999118%.

<snip>

- 2) Next, we will examine the time-domain filtered load voltage $v_{L,xx}(t)$ assuming $C = 500 \mu\text{F}$ and the given resistor values.
- a) Type out the equation for the trigonometric Fourier series of $v_{L,xx}(t)$. **Instructions:** Separate the dc term from the rest of the summation. For simplicity, you may use $|H_3(k\omega_0)|$ and $\angle H_3(k\omega_0)$ in the summation part (i.e., $k = 1, 2, \dots$) of the expression for $v_{L,xx}(t)$ as long as you reference the equation for $H_3(\omega)$.

We have the Fourier series coefficients for the unfiltered $v_{L,FW}(t)$ in Table 3 of part A. The Fourier series coefficients for $v_{O,FW}(t)$ are simply those for the unfiltered $v_{L,FW}(t)$ multiplied by 2 (i.e., divide out $H_2 = 0.5$).

Table 2 Fourier series coefficients for $v_{O,FW}(t)$

Coefficient	Value/expression
$a_{0,FW}$	$2V_m / \pi = 112.04508$ V
$a_{k,FW} \quad (k = 1, 2, \dots)$	$\frac{-4V_m \cos(\pi k)}{\pi(4k^2 - 1)} = \frac{-224.09016 \cos(\pi k)}{4k^2 - 1}$ (V)
$b_{k,FW} \quad (k = 1, 2, \dots)$	0

We get the Fourier series for $v_{L,FW}(t)$ by multiplying the magnitude of each term of $v_{O,FW}(t)$ by $|H_3(k\omega_{0,FW})|$ and adding the phase angle of $H_3(k\omega_{0,FW})$ to the argument of each $\cos(k\omega_{0,FW}t)$ term, i.e., $\cos[k\omega_{0,FW}t + \angle H_3(k\omega_{0,FW})]$.

$$\begin{aligned}
 v_{L,FW}(t) &= |H_3(0)|a_{0,FW} + \sum_{k=1}^{\infty} |H_3(k\omega_{0,FW})|a_{k,FW} \cos(k\omega_{0,FW}t + \angle H_3(k\omega_{0,FW})) \\
 &= (0.5) \frac{2V_m}{\pi} + \sum_{k=1}^{\infty} |H_3(k\omega_{0,FW})| \left(\frac{-4V_m \cos(\pi k)}{\pi(k^2 - 1)} \right) \cos(k\omega_{0,FW}t + \angle H_3(k\omega_{0,FW})) \\
 &= (0.5) \frac{(2)176}{\pi} + \sum_{k=1}^{\infty} |H_3(k1600\pi)| \left(\frac{-4(176) \cos(\pi k)}{\pi(k^2 - 1)} \right) \cos(k1600\pi t + \angle H_3(k1600\pi)) \\
 v_{L,FW}(t) &= 56.0225 + \sum_{k=1}^{\infty} |H_3(k1600\pi)| \left(\frac{-224.09 \cos(\pi k)}{k^2 - 1} \right) \cos(k1600\pi t + \angle H_3(k1600\pi)) \text{ (V)} \quad -\infty < t < \infty
 \end{aligned}$$

where $\omega_{0,FW} = 2\pi f_{0,FW} = 1600\pi = 5026.548 \text{ rad/s}$, and

$$H_3(k\omega_{0,FW}) = H_3(k1600\pi) = \frac{4}{8 + jk1600\pi 0.008} = \frac{0.5}{1 + j1.6\pi k} \quad -\infty < \omega < \infty.$$

- b) Calculate $a_{0,xx}$, $a_{1,xx}$, and $a_{2,xx}$. Calculate $H(0)$, $H(\omega_{0,xx})$, and $H(2\omega_{0,xx})$ [put in polar form w/ angle in degrees]. Type out the equation for a truncated trigonometric Fourier series of $v_{L,xx}(t)$ that includes the dc term plus first **two** harmonics with all terms enumerated.


$$H_3(0) = \frac{0.5}{1 + j0} = 0.5 \quad \& \quad a_{0,FW} = 2(176)/\pi = 112.04508 \text{ V},$$

$$H_3(1600\pi) = \frac{0.5}{1 + j1.6\pi} = 0.09756 \angle -78.748^\circ \quad \& \quad a_{1,FW} = \frac{-4(176) \cos(\pi)}{\pi(4(1)^2 - 1)} = 74.6967 \text{ (V)}$$

$$H_3(3200\pi) = \frac{0.5}{1 + j1.6\pi 2} = 0.04949 \angle -84.319^\circ \quad \& \quad a_{2,FW} = \frac{-4(176) \cos(\pi 2)}{\pi(4(2)^2 - 1)} = -14.9393 \text{ (V)}$$

$$\begin{aligned}
 v_{L,FW}(t) &= (0.5)112.045 + (0.09756)74.7 \cos(\omega_{0,FW}t - 78.748^\circ) - (0.04949)14.9393 \cos(2\omega_{0,FW}t - 84.319^\circ) \\
 &= 56.0225 + 7.2874 \cos(1600\pi t - 78.748^\circ) - 0.7393 \cos(3200\pi t - 84.309^\circ) \text{ (V)} \\
 &= 56.0225 + 7.2874 \cos(5026.55t - 1.3744) - 0.7393 \cos(10053.1t - 1.47165) \text{ (V)} \quad -\infty < t < \infty
 \end{aligned}$$

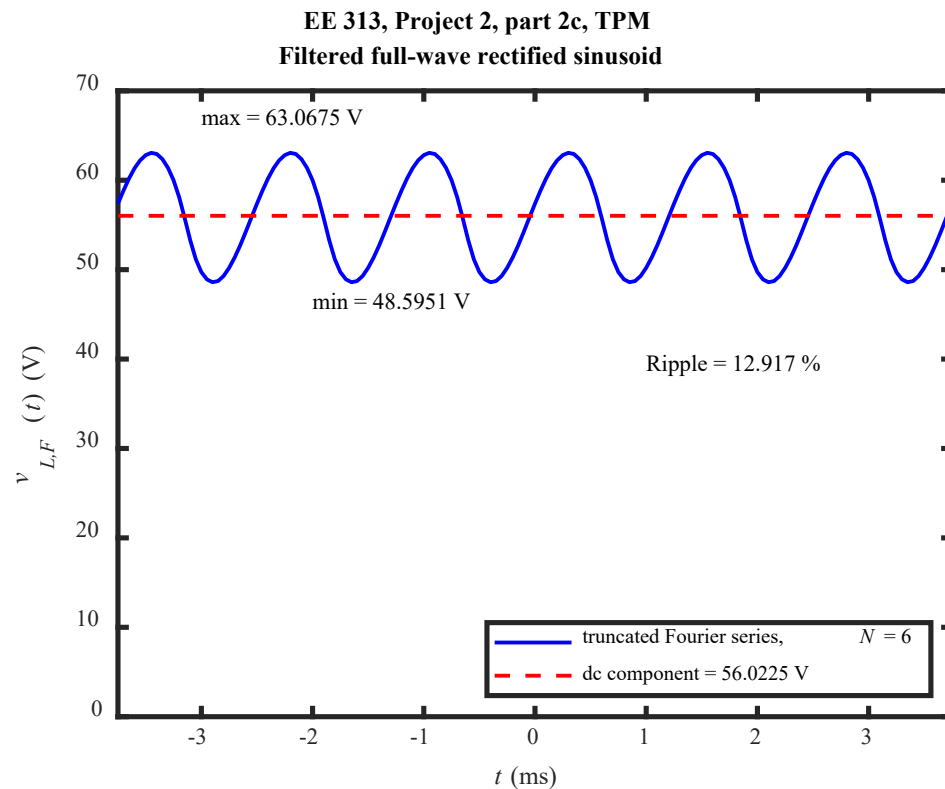- c) Plot the truncated Fourier series of $v_{L,xx}(t)$ using the dc term plus the first six harmonics. Put a labeled horizontal dashed line at the value of the dc term $(v_{L,xx})_{dc}$. For horizontal and vertical scales, use $-1.5T \leq t \leq 1.5T$ and $0 \leq V \leq 70 \text{ V}$, respectively. Determine the maximum $(v_{L,xx})_{max}$ and minimum $(v_{L,xx})_{min}$ values of $v_{L,xx}(t)$ and put on the plot. While ideally the filtered output would be equal to $(v_{L,xx})_{dc}$, the output quality of practical dc power supplies is characterized by their ripple R defined as $R = \left[\left((v_{L,xx})_{max} - (v_{L,xx})_{min} \right) / 2 \right] / (v_{L,xx})_{dc} * 100\%$. Find the ripple R for this circuit.



➤ $(v_{L,FW})_{\max} = 63.0675 \text{ V}$ and $(v_{L,FW})_{\min} = 48.5951 \text{ V}$


➤
$$R = \left(\frac{[(v_{L,F})_{\max} - (v_{L,F})_{\min}] / 2}{(v_{L,F})_{\text{dc}}} \right) 100\% = \left(\frac{[63.0675 - 48.5951] / 2}{56.0225} \right) 100\% \Rightarrow \underline{R = 12.917\%}$$

<snip>

3) <snip> modify our circuit by changing the capacitor value C (other parts of circuit are unchanged). As a ‘rule of thumb’, a 5% ripple is considered acceptable for most dc power supply applications.

a) <snip> determine <snip> $C_{5\%}$ (μF) needed to achieve a 5% ripple. Plot <snip> $v_{L,xx}(t)$ <snip> Put a labeled horizontal dashed line <snip> $(v_{L,xx})_{\text{dc}}$. For horizontal & vertical scales, use $-1.5T \leq t \leq 1.5T$ & $0 \leq V \leq 60 \text{ V}$ <snip> Determine <snip> $(v_{L,xx})_{\max}$ & <snip> $(v_{L,xx})_{\min}$ values of $v_{L,xx}(t)$ & put on plot.

➤ $C_{5\%} = 1310.23 \mu\text{F}$

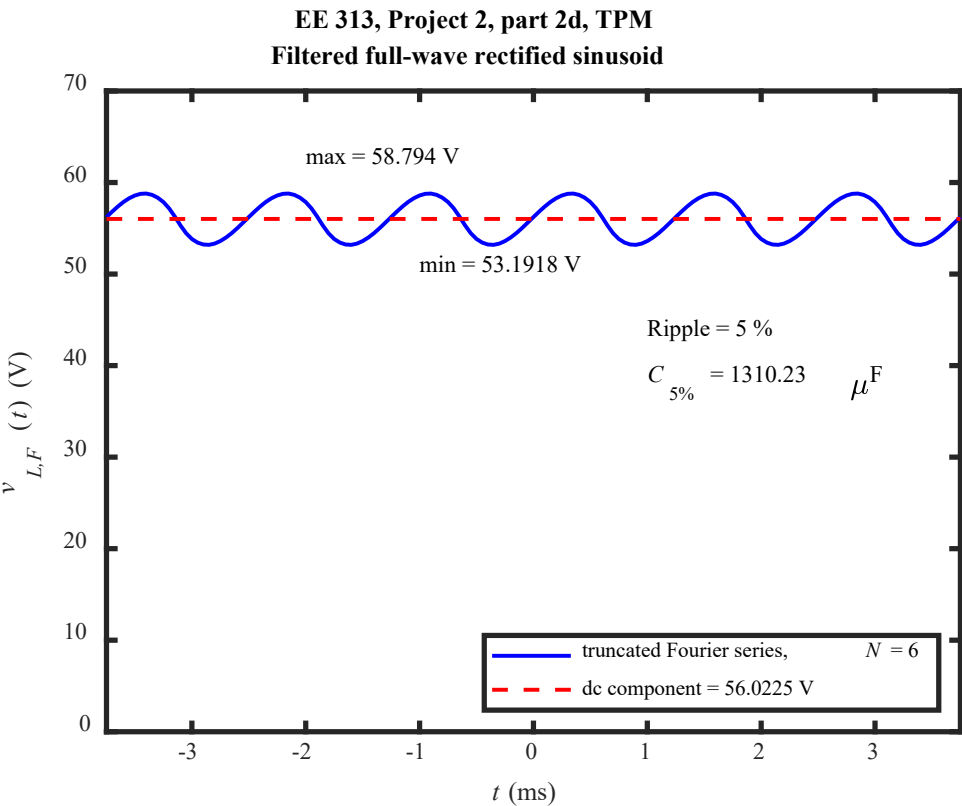

<snip>

- b) Using $C_{5\%}$, estimate the total power $P_{L,xx}$ in the filtered load voltage by adding the power in the dc plus first ten harmonics. For the three largest line spectra, fill-in the table below. What fraction of the total power is contained in these three?

Table 3 Power in three largest line spectra for 5% filtered full-wave rectification

harmonic #	f (Hz)	amplitude (V)	P (W)	% of $P_{L,xx}$
0	0	56.02254	784.631246	99.871407
1	800	2.827328	0.999223	0.127186
2	1600	0.283342	0.010035	0.001277

➤ $P_{L,FW,5\%} \cong 785.6415244 \text{ W}$ of which the first three account for 99.99987%.

<snip>