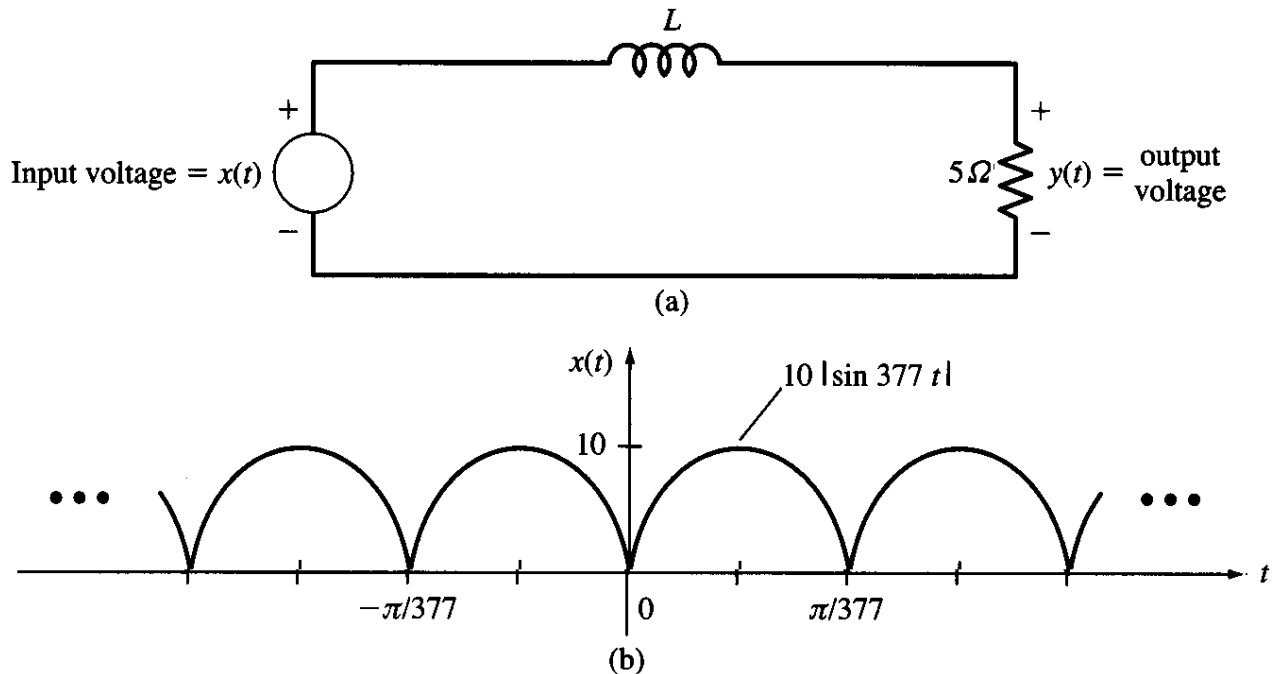
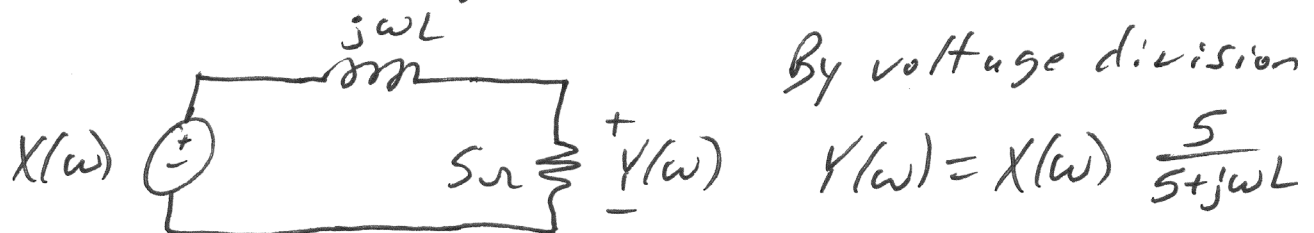


- 5.8** The voltage $x(t)$ shown in Figure P5.8b is applied to the RL circuit shown in Figure P5.8a.
- (a) Find the value of L so that the peak of the largest ac component (harmonic) in the output response $y(t)$ is $1/30$ of the dc component of the output.
- (b) Plot an approximation for $y(t)$, using the truncated complex exponential Fourier series from $k = -3$ to $k = 3$.



a) Put circuit in phasor form



$$H(\omega) = \frac{Y(\omega)}{X(\omega)} = \frac{5}{5 + j\omega L}$$

Next, calculate complex exponential F.S.

Per (3.20) + (3.7) $a_0 = c_0 = \frac{1}{T} \int_0^T x(t) dt$

where $T = \frac{\pi}{377} \text{ s}$ & $\omega_0 = \frac{2\pi}{T} = 754 \text{ rad/s}$

$x(t)$ is even $\Rightarrow b_k = 0$ & $c_k = \frac{1}{2} a_k = c_{-k}$ (3.20)

$$\begin{aligned}
 \text{a) cont. } C_0 &= \frac{377}{\pi} \int_0^{\pi/377} 10 \sin(377t) dt \\
 &= \frac{377}{\pi} 10 \left. \frac{-\cos(377t)}{377} \right|_0^{\pi/377} \\
 C_0 &= \frac{10}{\pi} [-\cos(\pi) + \cos(0)] = \frac{20}{\pi}
 \end{aligned}$$

$$\begin{aligned}
 (3.21) \quad C_k &= \frac{1}{T} \int_0^T x(t) e^{-jk\omega_0 t} dt \\
 &= \frac{377}{\pi} \int_0^{\pi/377} 10 \sin(377t) e^{-jk754t} dt \\
 &= \frac{377(10)}{\pi} \left. \frac{e^{-jk754t} [-jk754 \sin(377t) - 377 \cos(377t)]}{(-jk754)^2 + 377^2} \right|_0^{\pi/377} \\
 &= \frac{377(10)}{\pi} \left[\frac{e^{-jk2\pi} (-jk754 \sin(\pi) - 377 \cos(\pi))}{-k^2 754^2 + 377^2} - \frac{e^0 (-jk754 \sin(0) - 377 \cos(0))}{-k^2 754^2 + 377^2} \right] \\
 &= \frac{377(10)}{\pi} \left[\frac{1(0 + 377) - 1(0 - 377)}{377^2 - 2^2 377^2 k^2} \right] \\
 \underline{C_k} &= \frac{20}{\pi(1-4k^2)} \quad k = 0, \pm 1, \pm 2, \dots
 \end{aligned}$$

$k=1$ (1st harmonic) is largest. Since $a_k = 2C_k$,

We want $2|C_1| = \frac{1}{30} C_0$

$$C_0^y = C_0 H(0) = \frac{20}{\pi} \frac{5}{5+j0} = \frac{20}{\pi}$$

$$\text{Now, } |C_1^Y| = |C_1| |H(\omega_0)| = \left| \frac{20}{\pi(1-4(1)^2)} \right| \left| \frac{5}{5+j754L} \right|$$

$$= 2.122066 \left| \frac{5}{5+j754L} \right|$$

$$\text{So, } 2|C_1^Y| = 4.24413 \left| \frac{5}{5+j754L} \right| = \frac{1}{30} C_0^Y = \frac{20}{30\pi}$$

$$\hookrightarrow \frac{1}{|5+j754L|} = 0.01 \Rightarrow 5^2 + 754^2 L^2 = 100^2$$

$$\Rightarrow \underline{\underline{L = 0.13246 \text{ H}}}$$

b) Per notes -

$$y(t) = \sum_{k=-\infty}^{\infty} C_k^Y e^{j k \omega_0 t} = \sum_{k=-\infty}^{\infty} C_k H(k \omega_0) e^{j k \omega_0 t} \quad -\infty < t < \infty$$

$$y(t) \approx \sum_{k=-3}^3 \frac{20}{\pi(1-4k^2)} \frac{5}{5+jk754(0.13246)} e^{j k 754 t} \quad -\infty < t < \infty$$

↑ Implement using Matlab

```
% Chapter 5 problem 5.8b (chap5_5_08b.m)
% EE 313 Signals and Systems, your name, mm/dd/yyyy
% For x(t) = 10|sin(377t)|, plot the approximate output y(t)
% to input x(t) for an RL circuit with frequency response
% H(w) = 5/(5+jw) using complex exp. FS for k = -3 to 3.
clear; clc; close all;
N = 3; w0 = 754; % Define number of harmonics & fundamental freq (rad/s)
t = -0.02 : 0.0002 : 0.02; % define time vector
x = 10*abs(sin(377*t));
yN = zeros(1,length(t)); % initialize y(t) vector
for k1 = 1:1:2*N+1,
    ktmp = k1-(N+1); wk(k1) = ktmp*w0;
    H(k1) = 5./(5 + j*wk(k1)*0.13246); % RL circuit response at harmonics
    cxk(k1) = 20/pi/(1 - 4*ktmp^2); % Calculate x(t) line spectra
    cyk(k1) = H(k1)*cxk(k1); % Calculate y(t) line spectra
    yN = yN + cyk(k1).*exp(j*ktmp*w0*t); % complex exp. FS
end
yN = real(yN); % get rid of any rounding error imaginary components
plot(t,x,'b'), axis([-0.02 0.02 0 10]),
xlabel('\itt (sec)', 'fontsize', 16, 'fontname', 'times'),
ylabel('\itx(\itt)', 'fontsize', 16, 'fontname', 'times'),
title('Input \itx(\itt) = 10 |sin(377\itt)|', ...
```

```

    'fontsize',16,'fontname','times'),
figure, plot(t,yN,'b'), axis([-0.02 0.02 0 10]),
xlabel('\itt (sec)','fontsize',16,'fontname','times'),
ylabel('\ity(\itt)','fontsize',16,'fontname','times'),
title('Complex exponential FS of \ity(\itt) for \itN = 3',...
    'fontsize',16,'fontname','times'),
set(findobj('type','line'),'linewidth',2,'markersize',20)
set(findobj('type','axes'),'linewidth',2,'fontsize',12,'fontname','times')
set(findobj('type','text'),'fontsize',12,'fontname','times')

```

