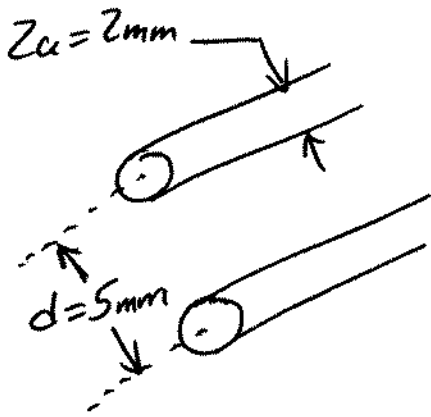


- 1) A two-wire transmission line consists of two perfectly-conducting wires of diameter 2 mm with a center-to-center spacing of 5 mm. If the insulation had an effective dielectric permittivity of $2.2\epsilon_0$, find L , C , Z_0 , and the phase velocity. At a frequency of 890 MHz, what are the phase constant and wavelength?



From Table 11.1,

$$L = \frac{\mu}{\pi} \cosh^{-1}\left(\frac{d}{2a}\right)$$

$$C = \frac{\pi \epsilon}{\cosh^{-1}(d/2a)}$$

$$L = \frac{\mu_0}{\pi} \cosh^{-1}\left(\frac{5\text{mm}}{2\text{mm}}\right) = \frac{4\pi \times 10^{-7}}{\pi} \cosh^{-1}(2.5)$$

$$L = 6.267 \times 10^{-7} \text{ H/m} = 626.7 \text{ nH/m}$$

$$C = \frac{\pi(2.2)8.854 \times 10^{-12}}{\cosh^{-1}(2.5)}$$

$$C = 3.906 \times 10^{-11} \text{ F/m} = 39.057 \text{ pF/m}$$


$$(11.21c) \quad Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{6.267 \times 10^{-7}}{3.906 \times 10^{-11}}} = \underline{\underline{126.67 \Omega}}$$

$$(11.21b) \quad u = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{6.267 \times 10^{-7} (3.906 \times 10^{-11})}} = \underline{\underline{2.021 \times 10^8 \text{ m/s}}}$$

$$(11.21b) \quad \beta = \frac{\omega}{u} = \frac{2\pi(890 \times 10^6)}{2.021 \times 10^8} = \underline{\underline{27.67 \text{ rad/m}}}$$

$$(11.13) \text{ or } (11.14) \quad \lambda = \frac{u}{f} = \frac{2\pi}{\beta} = \frac{2\pi}{27.67} = \underline{\underline{0.2271 \text{ m}}}$$

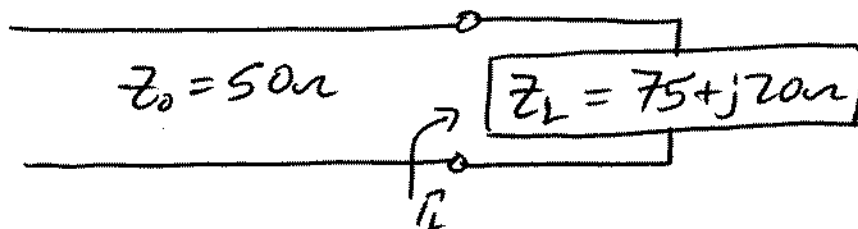A 50Ω coaxial cable feeds a $75 + j20\Omega$ dipole antenna. Find Γ and S .



Assume coaxial cable is lossless (SWR or VSWR doesn't make much sense for lossy trans. lines)

$$(11.36) \Gamma_L = \frac{z_L - z_0}{z_L + z_0} = \frac{(75 + j20) - 50}{(75 + j20) + 50} = \Gamma$$

$$\underline{\underline{\Gamma_L = 0.2529 \angle 29.57^\circ}}$$

$$\underline{\underline{|\Gamma| = |\Gamma_L| = 0.2529}}$$

$$(11.38) S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 0.2529}{1 - 0.2529}$$

$$\underline{\underline{S = 1.677}}$$