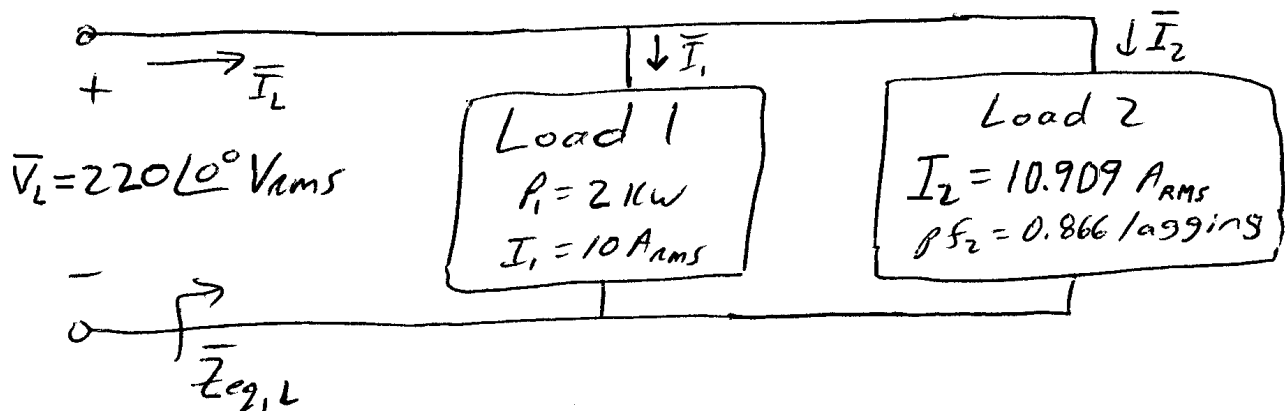



Example- A 220 V_{RMS} power line supplies two loads connected in parallel. Load 1 is an AC motor drawing a current of 10 A_{RMS} (measured using a multimeter) and power of 2 kW (measured using a wattmeter). Load 2 is a combination of lights and AC motors drawing 10.909 A_{RMS} with a lagging power factor of 0.866. Analyze each load as well as the overall equivalent load on the circuit. [Hint: Motors are resistive-inductive loads.]

⇒ Assume power line is @ 0° (reference)



Load 1

motor ⇒ lagging pf

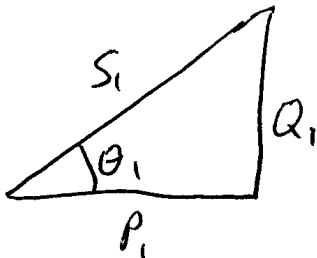

$$S_1 = V_{1,\text{rms}} I_{1,\text{rms}} = 220(10) = \underline{2200 \text{ VA}}$$

$$P_1 = 2000 \text{ W (given)}$$

$$\text{PF}_1 = \cos \theta_1 = \frac{P_1}{S_1} = \frac{2000}{2200} = \underline{0.9091 \text{ lagging}}$$

$$\theta_1 = \cos^{-1} 0.9091 = \underline{24.62^\circ} = \theta_{V_1} - \theta_{I_1}$$


$$\hookrightarrow \theta_{I_1} = \underline{-24.62^\circ}$$

$$\underline{\bar{I}_1 = 10 \angle -24.62^\circ \text{ A}_{\text{rms}}}$$

$$Q_1 = S_1 \sin \theta_1 = 2200 \sin 24.62^\circ = \underline{916.516 \text{ VAR}}$$

$$\bar{Z}_1 = \frac{\bar{V}_1}{\bar{I}_1} = \frac{220 \angle 0^\circ}{10 \angle -24.62^\circ} = \underline{22 \angle 24.62^\circ \Omega = 20 + j9.16516 \Omega}$$

$$\underline{\bar{S}_1 = P_1 + jQ_1 = 2000 + j916.516 \text{ VA} = 2200 \angle 24.62^\circ \text{ VA}}$$

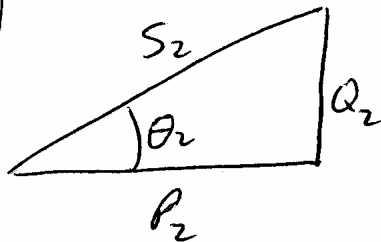Load 2

$$S_2 = 220(10.909) = 2400 \text{ VA}$$

$$PF_2 = 0.866 \text{ lagging} = \cos \theta_2$$

$$\hookrightarrow \theta_2 = \underbrace{+30^\circ}_{\text{lagging}} = \phi_{V_2} - \theta_{I_2}$$

$$\underline{\theta_{I_2} = -30^\circ}$$

$$I_2 = \underline{10.909 \text{ A}_{\text{rms}}}$$

$$\underline{\bar{I}_2 = 10.909 \angle -30^\circ \text{ A}_{\text{rms}}}$$

$$\begin{aligned} \bar{S}_2 &= \bar{V}_2 \bar{I}_{2\text{rms}}^* = (220 \angle 0^\circ)(10.909 \angle +30^\circ) \\ &= \underset{\substack{\uparrow \\ P_2 (\text{W})}}{2078.4} + j \underset{\substack{\uparrow \\ Q_2 (\text{VAR})}}{1200} \text{ VA} \end{aligned}$$

$$\begin{aligned} \bar{Z}_2 &= \frac{\bar{V}_2}{\bar{I}_2} = \frac{220 \angle 0^\circ}{10.909 \angle -30^\circ} = 20.167 \angle 30^\circ \Omega \\ &= \underline{17.465 + j10.083 \Omega} \end{aligned}$$

$$\begin{aligned} \bar{S}_{\text{power line}} &= \bar{S}_1 + \bar{S}_2 = 2200 \angle 24.62^\circ + 2400 \angle 30^\circ \\ &= 4594.94 \angle 27.427^\circ \text{ VA} = \underset{\substack{\uparrow \\ P_{\text{power line}}}}{4078.46} + j \underset{\substack{\uparrow \\ Q_{\text{power line}}}}{2116.516} \text{ VA} \end{aligned}$$

$$PF_L = \cos 27.427^\circ = \underline{0.8876 \text{ lagging}}$$

$$\bar{I}_L = \bar{I}_1 + \bar{I}_2 = 10 \angle -24.62^\circ + 10.909 \angle -30^\circ = \underline{20.886 \angle -27.427^\circ \text{ A}_{\text{RMS}}}$$

$$\bar{Z}_L = \bar{Z}_1 \parallel \bar{Z}_2 = \frac{\bar{V}_L}{\bar{I}_L} = \underline{10.53 \angle 27.427^\circ \Omega = 9.35 + j4.85 \Omega}$$