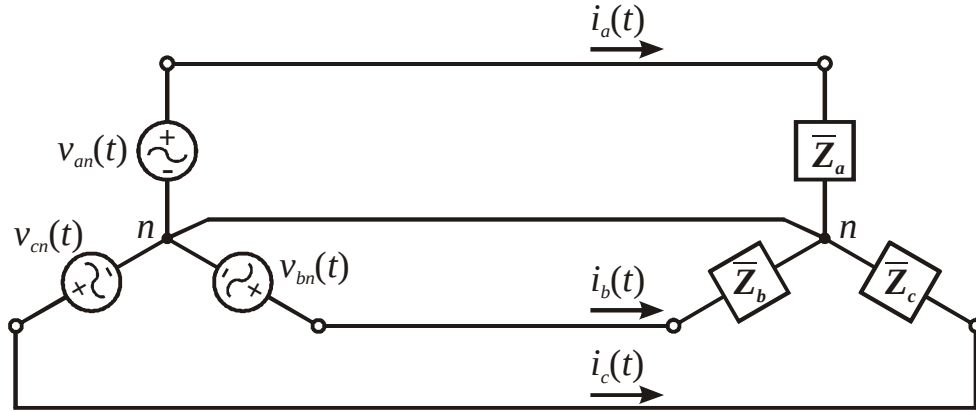


Three-phase unbalanced Wye-load power exampleDefine some constants for the source & load.

$$V := 120 \text{ V}_{\text{rms}} \quad Z_a := 20 \text{ } \Omega \quad \theta_a := 20 \cdot \frac{\pi}{180}$$

$$Z_b := 15 \text{ } \Omega \quad \theta_b := 15 \cdot \frac{\pi}{180} \quad Z_c := 25 \text{ } \Omega \quad \theta_c := -25 \cdot \frac{\pi}{180}$$

$$I_a := \frac{V}{Z_a} \quad I_b := \frac{V}{Z_b} \quad I_c := \frac{V}{Z_c}$$

$$I_a = 6 \text{ A}_{\text{rms}} \quad I_b = 8 \text{ A}_{\text{rms}} \quad I_c = 4.8 \text{ A}_{\text{rms}}$$

$$n := 0 .. 200 \quad \text{wt}_n := n \cdot \frac{2 \cdot \pi}{180}$$

Define phase voltages and currents.




$$\text{van}_n := \sqrt{2} \cdot V \cdot \cos(\text{wt}_n) \quad \text{ia}_n := \sqrt{2} \cdot I_a \cdot \cos(\text{wt}_n - \theta_a)$$

$$\text{vbn}_n := \sqrt{2} \cdot V \cdot \cos\left(\text{wt}_n - 120 \frac{\pi}{180}\right) \quad \text{ib}_n := \sqrt{2} \cdot I_b \cdot \cos\left(\text{wt}_n - 120 \frac{\pi}{180} - \theta_b\right)$$

$$\text{vcn}_n := \sqrt{2} \cdot V \cdot \cos\left(\text{wt}_n - 240 \frac{\pi}{180}\right) \quad \text{ic}_n := \sqrt{2} \cdot I_c \cdot \cos\left(\text{wt}_n - 240 \frac{\pi}{180} - \theta_c\right)$$

Calculate instantaneous power to each phase.
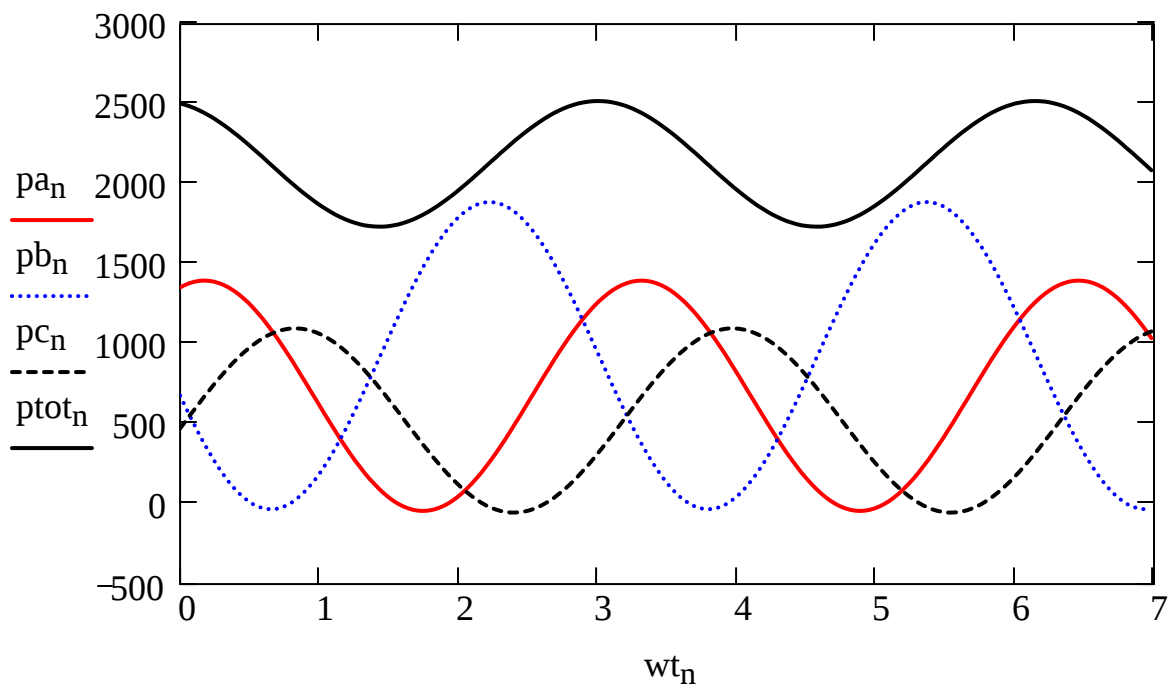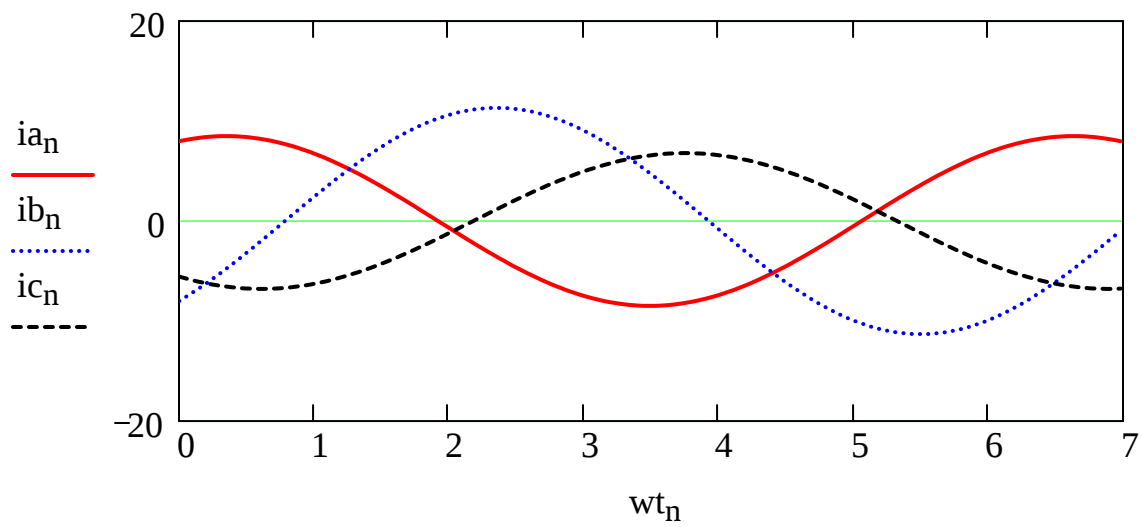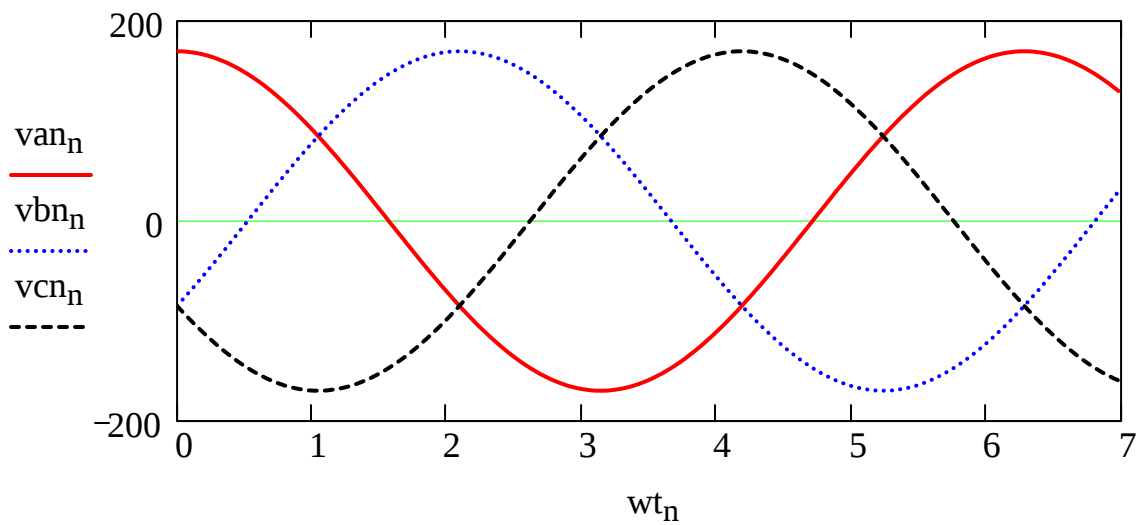
$$\text{pa}_n := \text{van}_n \text{ia}_n \quad \text{pb}_n := \text{vbn}_n \text{ib}_n \quad \text{pc}_n := \text{vcn}_n \text{ic}_n \quad \text{ptot}_n := \text{pa}_n + \text{pb}_n + \text{pc}_n$$



Calculate apparent power S to each phase.

$$S_a := V \cdot I_a \qquad S_a = 720 \qquad \text{VA}$$

$$S_b := V \cdot I_b \qquad S_b = 960 \qquad \text{VA}$$

$$S_c := V \cdot I_c \qquad S_c = 576 \qquad \text{VA}$$

$$S_{\text{tot}} := S_a + S_b + S_c \qquad S_{\text{tot}} = 2256 \qquad \text{VA}$$

Calculate time-ave real power P to each phase.

$$P_a := V \cdot I_a \cdot \cos(\theta_a) \qquad P_a = 676.579 \qquad \text{W}$$

$$P_b := V \cdot I_b \cdot \cos(\theta_b) \qquad P_b = 927.289 \qquad \text{W}$$

$$P_c := V \cdot I_c \cdot \cos(\theta_c) \qquad P_c = 522.033 \qquad \text{W}$$

$$P_{\text{tot}} := P_a + P_b + P_c \qquad P_{\text{tot}} = 2125.9 \qquad \text{W}$$

Calculate reactive power Q to each phase.

$$Q_a := V \cdot I_a \cdot \sin(\theta_a) \qquad Q_a = 246.255 \qquad \text{VAR}$$

$$Q_b := V \cdot I_b \cdot \sin(\theta_b) \qquad Q_b = 248.466 \qquad \text{VAR}$$

$$Q_c := V \cdot I_c \cdot \sin(\theta_c) \qquad Q_c = -243.428 \qquad \text{VAR}$$

$$Q_{\text{tot}} := Q_a + Q_b + Q_c \qquad Q_{\text{tot}} = 251.293 \qquad \text{VAR}$$

Calculate power factor (pf) for each phase.

$$\text{pf}_a := \cos(\theta_a) \qquad \text{pf}_a = 0.9397 \qquad \text{lagging since } Q_a > 0 \text{ \& } \theta_a > 0$$

$$\text{pf}_b := \cos(\theta_b) \qquad \text{pf}_b = 0.9659 \qquad \text{lagging since } Q_b > 0 \text{ \& } \theta_b > 0$$

$$\text{pf}_c := \cos(\theta_c) \qquad \text{pf}_c = 0.9063 \qquad \text{leading since } Q_c < 0 \text{ \& } \theta_c < 0$$

$$\text{pf}_{\text{tot}} := \frac{P_{\text{tot}}}{S_{\text{tot}}} \qquad \text{pf}_{\text{tot}} = 0.9423 \qquad \text{lagging since } Q_{\text{tot}} < 0$$

Not typically done as pf most important on per phase basis.