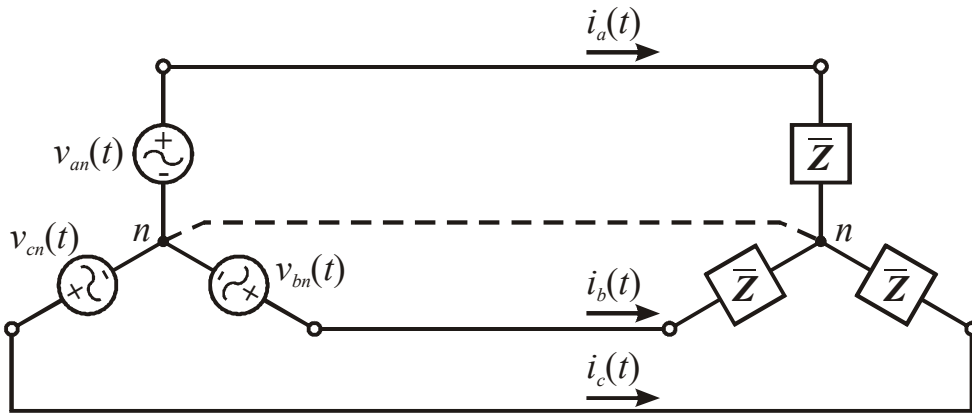


Balanced Three-phase Wye-source and Wye-load power example

Define some constants for the balanced sources & loads ($Z = 20/30^\circ \Omega$).

$$\begin{aligned} \underline{\underline{V}} &:= 120 \text{ V}_{\text{rms}} & Z &:= 20 \text{ } \Omega & \theta &:= 30 \cdot \frac{\pi}{180} & I &:= \frac{V}{Z} \\ I &= 6 \text{ A}_{\text{rms}} & n &:= 0 \dots 229 & \text{wt}_n &:= n \cdot \frac{2 \cdot \pi}{180} & \underline{\underline{m}} &:= 0 \dots 7 \end{aligned}$$


Define phase voltages and currents.

$$\begin{aligned} \text{van}_n &:= \sqrt{2} \cdot V \cdot \cos(\text{wt}_n) & \text{ia}_n &:= \sqrt{2} \cdot I \cdot \cos(\text{wt}_n - \theta) \\ \text{vbn}_n &:= \sqrt{2} \cdot V \cdot \cos\left(\text{wt}_n - 120 \frac{\pi}{180}\right) & \text{ib}_n &:= \sqrt{2} \cdot I \cdot \cos\left(\text{wt}_n - 120 \frac{\pi}{180} - \theta\right) \\ \text{vcn}_n &:= \sqrt{2} \cdot V \cdot \cos\left(\text{wt}_n - 240 \frac{\pi}{180}\right) & \text{ic}_n &:= \sqrt{2} \cdot I \cdot \cos\left(\text{wt}_n - 240 \frac{\pi}{180} - \theta\right) \end{aligned}$$

Calculate instantaneous power for each phase as well as total power (2 ways).

$$\begin{aligned} \text{pa}_n &:= \text{van}_n \text{ia}_n & \text{pb}_n &:= \text{vbn}_n \text{ib}_n & \text{pc}_n &:= \text{vcn}_n \text{ic}_n \\ \text{ptot}_n &:= \text{pa}_n + \text{pb}_n + \text{pc}_n & \text{or} & & \text{ptot1}_m &:= 3 \cdot V \cdot I \cdot \cos(\theta) \end{aligned}$$
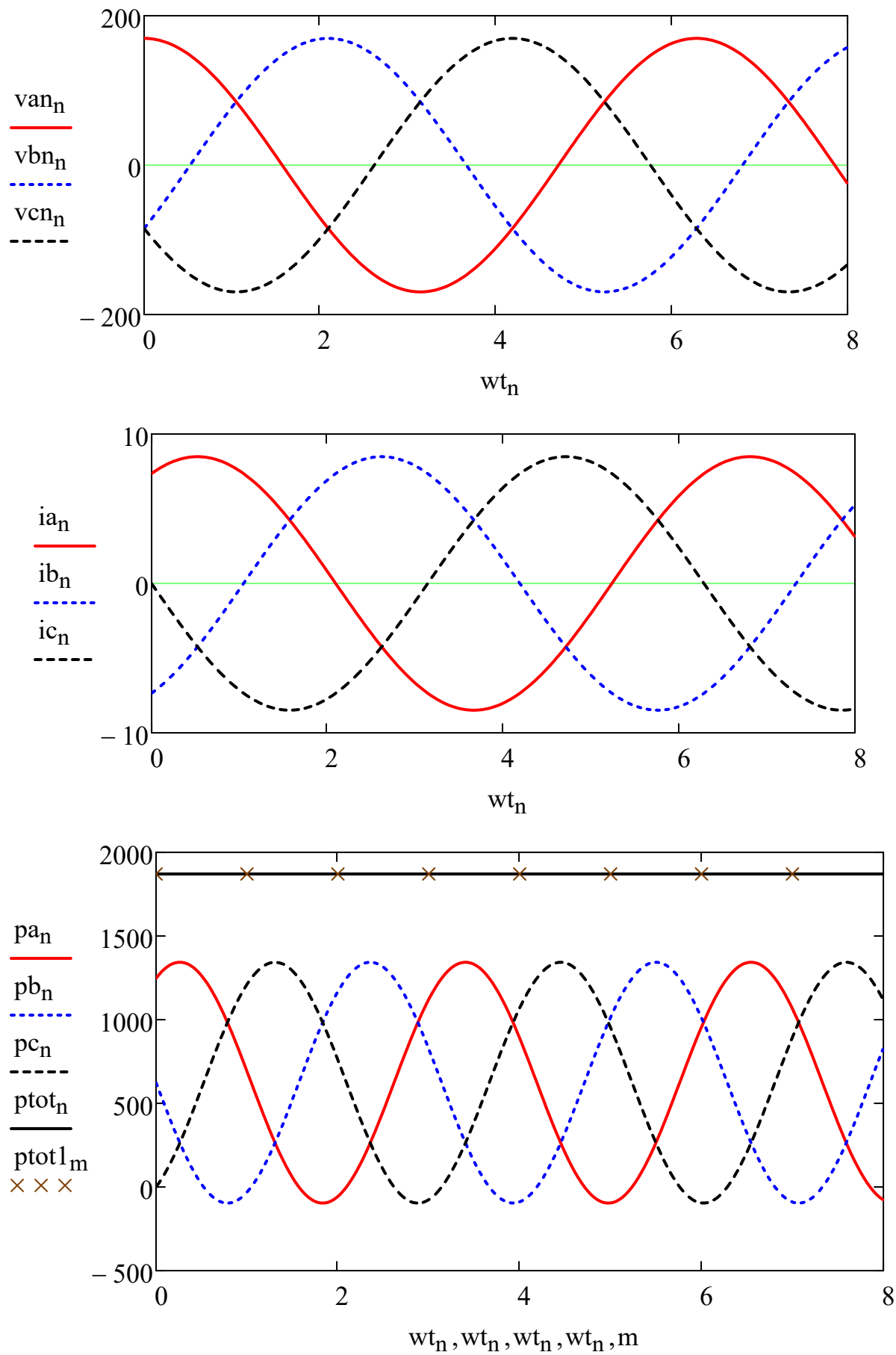
$$\boxed{\text{ptot22} = 1870.615} \text{ W} \quad \text{or} \quad \boxed{\text{ptot11} = 1870.615} \text{ W}$$



Calculate apparent power S to each phase.

$$S_a := V \cdot I \qquad S_a = 720 \qquad \text{VA}$$

$$S_b := V \cdot I \qquad S_b = 720 \qquad \text{VA}$$

$$S_c := V \cdot I \qquad S_c = 720 \qquad \text{VA}$$

$$S_{\text{tot}} := 3 \cdot V \cdot I \qquad S_{\text{tot}} = 2160 \qquad \text{VA}$$

Calculate time-average real power P to each phase.

$$P_a := V \cdot I \cdot \cos(\theta) \qquad P_a = 623.538 \qquad \text{W}$$

$$P_b := V \cdot I \cdot \cos(\theta) \qquad P_b = 623.538 \qquad \text{W}$$

$$P_c := V \cdot I \cdot \cos(\theta) \qquad P_c = 623.538 \qquad \text{W}$$

$$P_{\text{tot}} := 3 \cdot V \cdot I \cdot \cos(\theta) \qquad P_{\text{tot}} = 1870.61 \qquad \text{W}$$

Calculate reactive power Q to each phase.

$$Q_a := V \cdot I \cdot \sin(\theta) \qquad Q_a = 360 \qquad \text{var}$$

$$Q_b := V \cdot I \cdot \sin(\theta) \qquad Q_b = 360 \qquad \text{var}$$

$$Q_c := V \cdot I \cdot \sin(\theta) \qquad Q_c = 360 \qquad \text{var}$$

$$Q_{\text{tot}} := 3 V \cdot I \cdot \sin(\theta) \qquad Q_{\text{tot}} = 1080 \qquad \text{var}$$

Calculate power factor (PF) for each phase.

$$PF_a := \frac{P_a}{S_a} \qquad \boxed{PF_a = 0.866} \qquad \text{lagging since } Q_a > 0 \text{ \& } \theta > 0$$

$$PF_b := \cos(\theta) \qquad PF_b = 0.866 \qquad \text{lagging since } Q_b > 0 \text{ \& } \theta > 0$$

$$PF_c := \cos(\theta) \qquad PF_c = 0.866 \qquad \text{lagging since } Q_c > 0 \text{ \& } \theta > 0$$

$$PF := \frac{P_{\text{tot}}}{S_{\text{tot}}} \qquad PF = 0.866 \qquad \text{lagging since } Q > 0 \text{ \& } \theta > 0$$