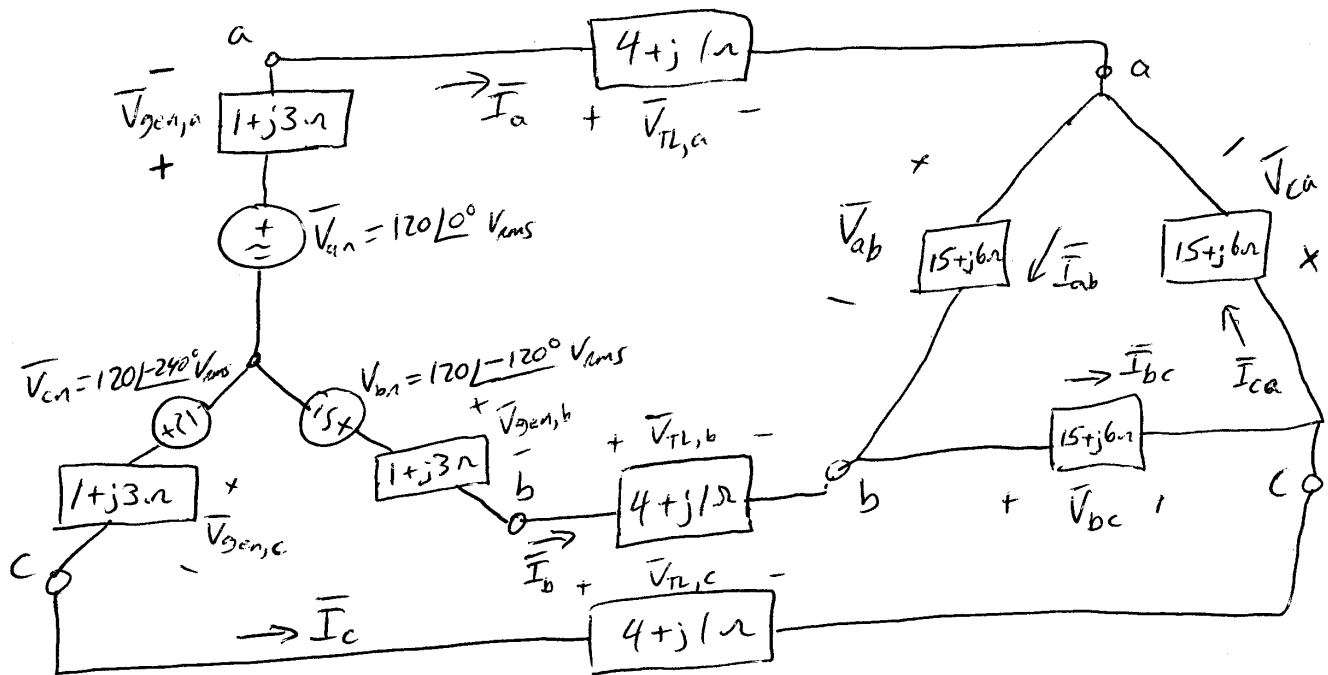


Three-Phase Circuit Power Example

ex. A balanced Y-config. 3- ϕ power source has a phase voltage of 120V_{rms} and impedance of $1+j3\Omega$. It is connected to a balanced Δ -config. load, $\bar{Z}_{\Delta} = 15+j6\Omega$, by transmission lines with line impedances of $4+j1\Omega$. Calculate all currents, voltages, and power quantities of interest.




Step 1 - convert Δ -load to Y-load


$$\bar{Z}_Y = \frac{\bar{Z}_{\Delta}}{3} = \frac{15+j6}{3} = 5+j2\Omega$$

Step 2 - Redraw circuit (Note that all impedances are now in series!).

ex. cont.

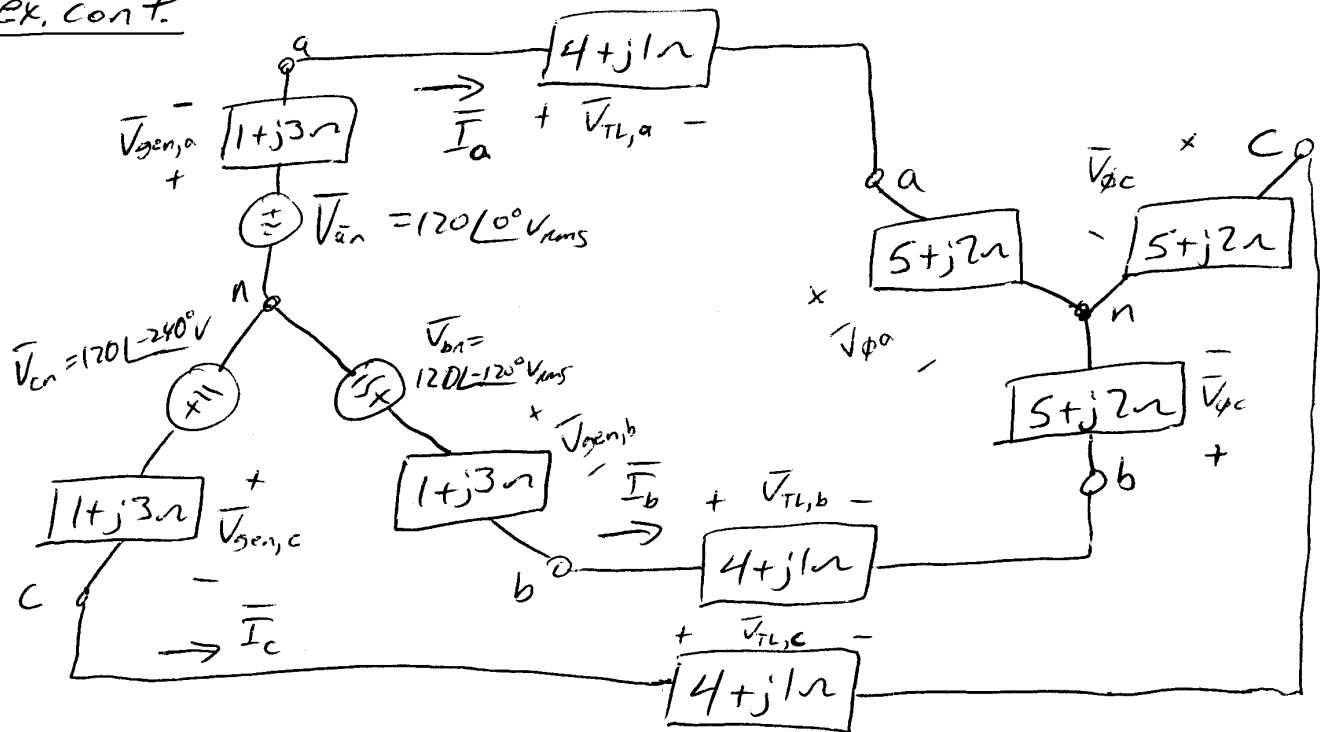

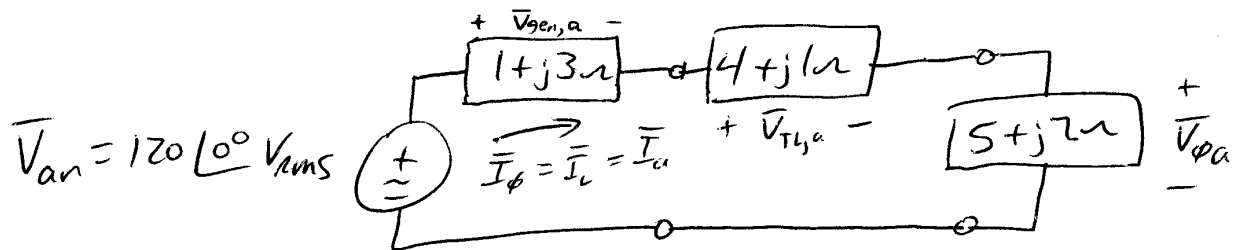Step 3 - Draw per-phase equivalent circuit (I'll choose phase a).



$$\bar{I}_a = \frac{120\angle 0^\circ}{(1+j3) + (4+j1) + (5+j2)} = \frac{120\angle 0^\circ}{11.6619\angle 30.9638^\circ}$$

$$\bar{I}_a = 10.29\angle -30.9638^\circ \text{ A}_{rms}$$

$$I_\phi = 10.289915 \text{ A}_{rms}$$

$$\bar{I}_b = 10.29\angle -150.9638^\circ \text{ A}_{rms} \quad (-120^\circ \text{ phase shift})$$

$$\bar{I}_c = 10.29\angle -270.9638^\circ \text{ A}_{rms} \quad (-240^\circ \text{ phase shift})$$

ex. cont.

$$P_{\phi} = P_a = P_b = P_c = V_{\phi} I_{\phi} \cos \theta = (120)(10.29) \cos 30.9638^{\circ}$$

$$\underline{P_{\phi} = 1058.8 \text{ W}}$$

$$\underline{P = 3 P_{\phi} = 3176.5 \text{ W}} \quad \leftarrow \text{Overall power from ideal 3}\phi \text{ voltage sources}$$

$$Q_{\phi} = Q_a = Q_b = Q_c = V_{\phi} I_{\phi} \sin \theta = (120)(10.29) \sin 30.9638^{\circ}$$

$$\underline{Q_{\phi} = 635.3 \text{ VAR}}$$

$$\underline{Q = 3 Q_{\phi} = 1905.9 \text{ VAR}} \quad \leftarrow \text{Overall reactive power from ideal 3}\phi \text{ voltage sources}$$

$$\underline{\bar{S}_{\phi} = \bar{S}_a + \bar{S}_b + \bar{S}_c = P_{\phi} + j Q_{\phi} = 1058.8 + j 635.3 \text{ VA}}$$

$$\underline{\bar{S} = P + j Q = 3176.5 + j 1905.9 \text{ VA}}$$

$$S_{\phi} = |\bar{S}_{\phi}| = \underline{1234.8 \text{ VA}} = V_{\phi} I_{\phi} = 120(10.29)$$

$$S = |\bar{S}| = \underline{3704.4 \text{ VA}}$$

$$pf = \frac{P}{S} = \cos(30.9638^{\circ}) = \underline{0.8575 \text{ lagging}}$$

$Q > 0$

ex. cont. Find how the various quantities divide up.

Generator Impedances -

$$\bar{V}_{gen,a} = \bar{I}_a (1+j3) = (10.29 \angle -30.964^\circ)(1+j3) = \underline{32.54 \angle 40.60^\circ V_{rms}}$$

$$\bar{V}_{gen,b} = \bar{I}_b (1+j3) = 32.54 \angle 40.6^\circ - 120^\circ = \underline{32.54 \angle -79.4^\circ V_{rms}}$$

$$\bar{V}_{gen,c} = \bar{I}_c (1+j3) = 32.54 \angle 40.6^\circ - 240^\circ = \underline{32.54 \angle -199.4^\circ V_{rms}}$$

$$\bar{S}_{gen,a} = \bar{V}_{gen,a} \bar{I}_a^* = (32.54 \angle 40.6^\circ)(10.29 \angle +30.96^\circ)$$

$$\bar{S}_{gen,a} = 105.885 + j 317.65 \text{ VA} = \bar{S}_{gen,b} = \bar{S}_{gen,c}$$

$$\begin{aligned} \text{all } 3\phi \quad \left\{ \begin{array}{ll} P_{gen} = 3(105.885) = 317.7 \text{ W} & \frac{P_{gen}}{P} = 10\% \\ Q_{gen} = 3(317.65) = 953 \text{ VAR} & \frac{Q_{gen}}{Q} = 50\% \end{array} \right. \end{aligned}$$

Transmission Line Impedances -

$$\bar{V}_{TL,a} = \bar{I}_a (4+j1) = (10.29 \angle -30.964^\circ)(4+j1) = \underline{42.426 \angle -16.93^\circ V_{rms}}$$

$$\bar{V}_{TL,b} = \bar{I}_b (4+j1) = 42.426 \angle -16.93^\circ - 120^\circ = \underline{42.426 \angle -136.93^\circ V_{rms}}$$

$$\bar{V}_{TL,c} = \bar{I}_c (4+j1) = 42.426 \angle -16.93^\circ - 240^\circ = \underline{42.426 \angle -256.93^\circ V_{rms}}$$

$$\bar{S}_{TL,a} = \bar{V}_{TL,a} \bar{I}_a^* = (42.426 \angle -16.93^\circ)(10.29 \angle +30.964^\circ)$$

$$\bar{S}_{TL,a} = \bar{S}_{TL,b} = \bar{S}_{TL,c} = 423.53 + j 105.88 \text{ VA}$$

$$\begin{aligned} \text{all } 3\phi \quad - \quad \left\{ \begin{array}{ll} P_{TL} = 3(423.5) = 1270.6 \text{ W} & \frac{P_{TL}}{P} = 40\% \\ Q_{TL} = 3(105.88) = 317.7 \text{ VAR} & \frac{Q_{TL}}{Q} = 16.67\% \end{array} \right. \end{aligned}$$

ex. cont.

Load Impedances -

From the per-phase equivalent model

$$\bar{V}_{\phi a} = \bar{I}_a (5 + j2) = \underline{55.4129 \angle -9.16^\circ V_{rms}}$$

$$\bar{V}_{\phi b} = \bar{I}_b (5 + j2) = \underline{55.4129 \angle -9.16^\circ - 120^\circ = 55.4129 \angle -129.16^\circ V_{rms}}$$

$$\bar{V}_{\phi c} = \bar{I}_c (5 + j2) = \underline{55.4129 \angle -9.16^\circ - 240^\circ = 55.4129 \angle -249.16^\circ V_{rms}}$$

Find line-to-line voltage $V_{LL} = \sqrt{3} V_{\phi} = \sqrt{3} (55.4) = \underline{95.98 V_{rms}}$

which is not very good compared to $\sqrt{3} \cdot 120 = \underline{207.95 V_{rms}}$
that left the ideal 3 ϕ Y-sources.

Powers to load (using per-phase equivalent circuit) -

$$\bar{S}_{LO,a} = \bar{V}_{\phi a} \bar{I}_a^* = (55.4129 \angle -9.16^\circ) (10.29 \angle +30.964^\circ) = I_a^2 \bar{Z}_{\phi a}$$

$$\underline{\bar{S}_{LO,a} = 529.4 + j 211.8 \text{ VA} = \bar{S}_{LO,b} = \bar{S}_{LO,c}}$$

$$\begin{array}{l} \text{Overall} \\ \text{3}\phi \\ \text{Load} \end{array} \left\{ \begin{array}{l} P_{LO} = 3(529.4) = \underline{1588.2 \text{ W}} \\ Q_{LO} = 3(211.8) = \underline{635.3 \text{ VAR}} \end{array} \right. \quad \begin{array}{l} P_{LO/P} = \underline{50\%} \\ Q_{LO/Q} = \underline{33.3\%} \end{array}$$

$\Rightarrow$ Looks like I better spend some \$\$
on better transmission line and
generator!!

ex. cont.

Lastly, we need to find the phasor voltages and currents for the original balanced Δ -load.

By KVL (on circuit on second page of example) -

$$\bar{V}_{ab} = \bar{V}_{\phi a} - \bar{V}_{\phi b} = (55.4129 \angle -9.16^\circ) - (55.4129 \angle -129.16^\circ)$$

$$\bar{V}_{ab} = 95.98 \angle 20.84^\circ \text{ V}_{rms}$$

$$\bar{V}_{bc} = \bar{V}_{\phi b} - \bar{V}_{\phi c} = (55.4129 \angle -129.16^\circ) - (55.4129 \angle -249.16^\circ)$$

$$\bar{V}_{bc} = 95.98 \angle -99.16^\circ \text{ V}_{rms}$$

$$\bar{V}_{ca} = \bar{V}_{\phi c} - \bar{V}_{\phi a} = (55.4 \angle -249.2^\circ) - (55.4 \angle -9.16^\circ) = 95.98 \angle 140.84^\circ \text{ V}_{rms}$$

$$\bar{V}_{ca} = 95.98 \angle -219.16^\circ \text{ V}_{rms}$$

As a check, do KVL around upper LH loop of original circuit -

$$-\bar{V}_{an} + \bar{V}_{gen,a} + \bar{V}_{TL,a} + \bar{V}_{ab} - \bar{V}_{TL,b} - \bar{V}_{gen,b} + \bar{V}_{bn} = 0$$

$$\bar{V}_{ab} = \bar{V}_{an} - \bar{V}_{gen,a} - \bar{V}_{TL,a} + \bar{V}_{TL,b} + \bar{V}_{gen,b} - \bar{V}_{bn}$$

$$= (120 \angle 0^\circ) - (32.54 \angle 40.6^\circ) - (42.426 \angle -16.93^\circ) + (42.426 \angle -136.93^\circ) + (32.54 \angle -79.4^\circ) - (120 \angle -120^\circ)$$

$$\bar{V}_{ab} = 95.98 \angle 20.84^\circ \text{ V}_{rms} \Leftarrow \text{Same answer}$$

ex. cont.

By Ohm's Law $\bar{I}_{ab} = \frac{\bar{V}_{ab}}{15+j6} = \frac{95.98 \angle 20.84^\circ}{15+j6} = \underline{5.941 \angle -0.96^\circ \text{ A}_{rms}}$

$$\bar{I}_{bc} = \frac{\bar{V}_{bc}}{15+j6} = \underline{5.941 \angle -120.96^\circ \text{ A}_{rms}}$$

$$\bar{I}_{ca} = \frac{\bar{V}_{ca}}{15+j6} = \underline{5.941 \angle -240.96^\circ \text{ A}_{rms}}$$

As a check, compute the complex power to each phase of the Δ -loads & compare w/ per-phase equivalent values

$$\begin{aligned} \bar{S}_{L,ab} &= \bar{V}_{ab} \bar{I}_{ab}^* = (95.98 \angle 20.84^\circ)(5.941 \angle +0.96^\circ) \\ &= \underline{529.4 + j211.8 \text{ VA}} \Leftarrow \text{Same answer!} \end{aligned}$$