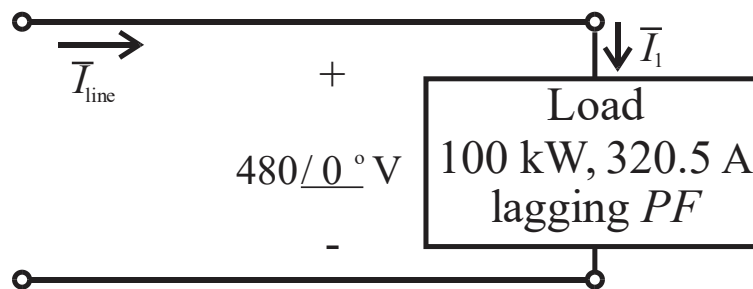


Example- A U.S. industrial plant ($f = 60$ Hz) is supplied by a 480 V power line. Without PF correction, the plant uses 100 kW (measured using wattmeter) and draws a current of 320.5 A (measured using ammeter). Given the equipment in the plant, the power factor is known to be lagging. For the best electrical rates, a power factor of $pf \geq 0.95$ is required by the utility company. Find the range of capacitances, connected in parallel, at the plant service entrance that will work. Also, determine the capacitance that will yield a $PF = 1$. To demonstrate why we do PF correction, calculate the input line current to the plant for the various cases.

- Arbitrarily make the input voltage the phase reference (i.e., 0°).

No PF correction



- The apparent power for the load (industrial plant) is

$$S_1 = V I_1 = 480 (320.5) \Rightarrow \underline{S_1 = 153,840 \text{ VA} = 153.84 \text{ kVA.}}$$

- The power factor for the load is

$$PF_1 = \frac{P_1}{S_1} = \frac{100 \text{ kW}}{153.84 \text{ kVA}} \Rightarrow \underline{PF_1 = 0.65 \text{ lagging.}}$$

- This leads to a power angle for the load of

$$PF_1 = \frac{100 \text{ kW}}{153.84 \text{ kVA}} = \cos(\theta_1) \Rightarrow \theta_1 = \cos^{-1}(0.65) \Rightarrow \underline{\theta_1 = 49.4564^\circ.}$$

- The load power angle can then be used to determine the current phase angle

$$\theta_1 = \theta_V - \theta_I = 0^\circ - \theta_I = 49.4564^\circ \Rightarrow \underline{\theta_I = -49.4564^\circ.}$$


- The line/load current with no PF correction is then

$$\underline{\bar{I}_{\text{line}} = \bar{I}_1 = I_1 \angle \theta_I \Rightarrow \bar{I}_{\text{line}} = \bar{I}_1 = 320.5 \angle -49.4564^\circ \text{ A}_{\text{rms}}.}$$


- To complete the load power triangle, compute the load reactive power

$$Q_1 = P_1 \tan(\theta_1) = 100 \tan(49.4564^\circ) \Rightarrow \underline{Q_1 = 116.9047 \text{ kvar.}}$$

Load power triangle

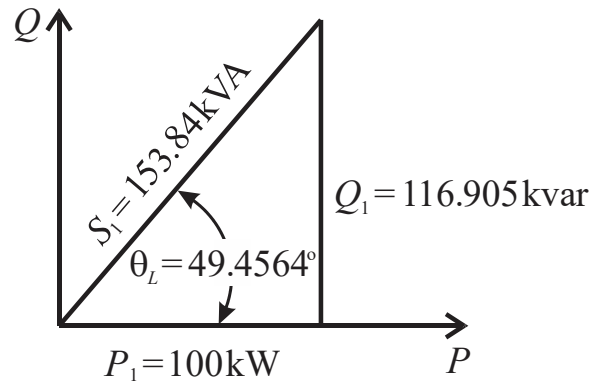

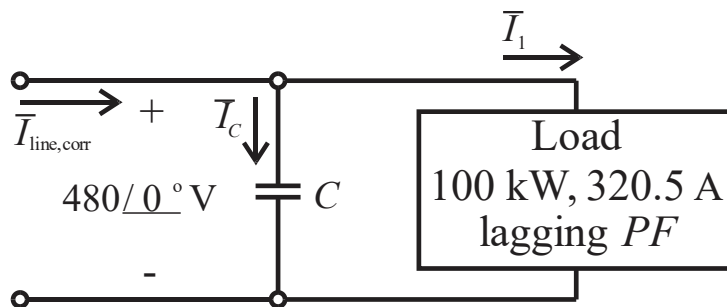Power Factor correction (i.e., add a capacitor).



$$\text{where } C = \frac{P_1 [\tan \theta_1 - \tan \theta_2]}{\omega V^2}.$$

- The goal of a $PF \geq 0.95$ leads to a desired power angle range of

$$\theta_2 = \pm \left| \cos^{-1}(0.95) \right| \Rightarrow \underline{\theta_2 = \pm 18.1949^\circ}.$$


- The **minimum** needed parallel capacitance, for a power factor of 0.95 **lagging** (i.e., $\theta_2 = +18.1949^\circ$, undercorrection), is

$$C_{\min} = \frac{100 \cdot 10^3 [\tan(49.4564^\circ) - \tan(18.1949^\circ)]}{2\pi (60) 480^2} \Rightarrow \underline{C_{\min} = 0.9676 \text{ mF.}}$$

- For a power factor of 0.95 **lagging** (i.e., $\theta_2 = 18.1949^\circ$), the apparent and reactive powers are

$$S_2 = \frac{P_2}{\cos(\theta_2)} = \frac{100 \cdot 10^3}{\cos(18.1949^\circ)} = 105.2632 \text{ kVA and}$$

$$Q_2 = P_2 \tan(\theta_2) = 100 \cdot 10^3 \tan(18.1949^\circ) = 32.8685.2632 \text{ kvar.}$$

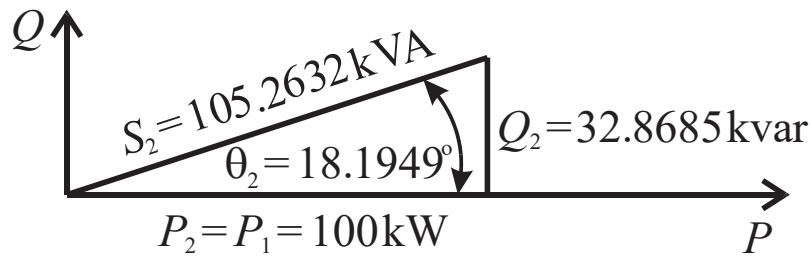Power triangle w/ PF = 0.95 lagging

- The associated phasor rms current for a power factor of 0.95 **lagging** is -

$$\bar{I}_{\text{line, corr}} = \frac{S_2}{V} \angle -\theta_2 = \frac{105.263 \cdot 10^3}{480} \angle -18.195^\circ \Rightarrow \bar{I}_{\text{line, corr}} = 219.3 \angle -18.195^\circ \text{ A}_{\text{rms}}$$


- The **maximum** required parallel capacitance, for a power factor of 0.95 **leading** ($\theta_2 = -18.1949^\circ$, overcorrection), is -

$$C_{\text{max}} = \frac{100 \cdot 10^3 [\tan(49.4564^\circ) - \tan(-18.1949^\circ)]}{2\pi(60)480^2} \Rightarrow \underline{C_{\text{max}} = 1.7243 \text{ mF.}}$$

- For a power factor of 0.95 **leading** (i.e., $\theta_2 = -18.1949^\circ$), the apparent and reactive powers are

$$S_2 = \frac{P_2}{\cos(\theta_2)} = \frac{100 \cdot 10^3}{\cos(-18.1949^\circ)} = 105.2632 \text{ kVA and}$$

$$Q_2 = P_2 \tan(\theta_2) = 100 \cdot 10^3 \tan(-18.1949^\circ) = -32.8685.2632 \text{ kvar.}$$

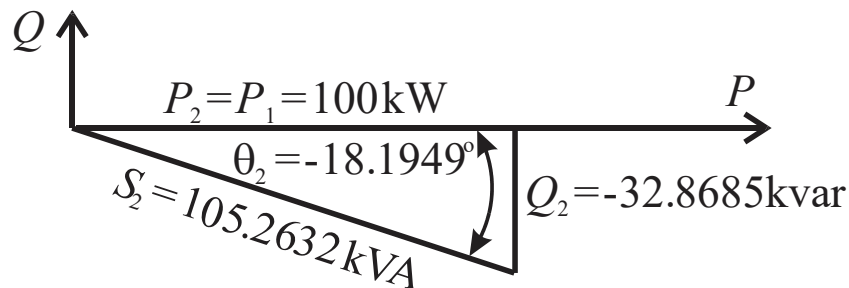Power triangle w/ PF = 0.95 leading

- The associated phasor rms current for a power factor of 0.95 **leading** is

$$\bar{I}_{\text{line, corr}} = \frac{S_2}{V_{\text{rms}}} \angle -\theta_2 = \frac{105.263 \cdot 10^3}{480} \angle 18.195^\circ \Rightarrow \bar{I}_{\text{line, corr}} = 219.3 \angle 18.195^\circ \text{ A}_{\text{rms}}.$$

- The overall capacitance range to meet the $PF \geq 0.95$ goal is

$$C_{\min} = 0.9676 \text{ mF} \leq C \leq C_{\max} = 1.7243 \text{ mF}.$$

- For perfect correction, i.e., $PF = 1$ and $\theta_2 = 0^\circ$, the required capacitance is

$$C_{PF=1} = \frac{100 \cdot 10^3 [\tan(49.4564^\circ) - \tan(0^\circ)]}{2\pi(60)480^2} \Rightarrow \underline{\underline{C_{PF=1} = 1.346 \text{ mF}}}.$$

- The associated phasor rms current for a $PF = 1$ (now $S_2 = P_2 = P_1$) is

$$\bar{I}_{\text{line, corr}} = \frac{S_2}{V_{\text{rms}}} \angle -\theta_2 = \frac{100 \cdot 10^3}{480} \angle 0^\circ \Rightarrow \underline{\underline{\bar{I}_{\text{line, corr}} = 208.3 \angle 0^\circ \text{ A}_{\text{rms}}}}.$$

- The rms line currents associated with the power factors after correction, i.e., 219.3 A w/ $PF = 0.95$ lagging, 208.3 A w/ $PF = 1$, & 219.3 A w/ $PF = 0.95$ leading, are **far smaller** than the uncorrected rms line current of 320.5 A.
- This would translate to **significant** reductions in the transmission line losses ($I_{\text{line}}^2 R_{TL}$). For example, with a $PF = 0.95$, the losses would be

$$219.3^2 / 320.5^2 = 0.4619 = \underline{\underline{46.19\%}}$$

of the uncorrected line losses!