


Chapter 6 Induction Motors

1

→ No externally supplied dc field current to rotor, only rely on induced rotor currents

→ virtually never used as generators by utilities, some applications in alt. energy (windmills, ...)

6.1 Induction Motor Construction

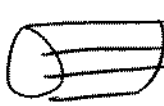Two types — cage rotor  shorting ring(s)
 — wound rotor ~ full set of 3 ϕ windings (like stator)

→ * usually Y-connected thru brushes/slip rings

* more control / more complicated / more maintenance

* cost \$ \$

→ cage rotor induction motors far more popular

6.2 Basic Induction Motor Concepts

2

→ Basics covered in Chap. 6

Key concept $n_{\text{induction motor}} < n_{\text{sync}} = \frac{120 f_e}{p}$

→ else τ goes to zero + it slows down

Concept of Rotor Slip

→ care about relative speed/velocities of rotor wrt magnetic field (stator)

$$n_{\text{slip}} = n_{\text{sync}} - n_m \equiv \text{Slip Speed}$$

$$n_{\text{sync}} = \frac{120 f_e}{p}$$

$n_m = \text{mech. speed of shaft}$

$$\text{Slip} \equiv S = \frac{n_{\text{slip}}}{n_{\text{sync}}} \times 100\% = \frac{n_{\text{sync}} - n_m}{n_{\text{sync}}} \times 100\%$$

$$0 \leq S \leq 1$$

synchronous ↑

stationary
(motor not turning)

$$n_m = (1 - S) n_{\text{sync}}$$

$$\omega_m = (1 - S) \omega_{\text{sync}}$$

6.2 cont.

3

Electrical Frequency on the Rotor

→ electrical freq. of e_{ind} + rotor NOT necessarily the same as f_e due to relative motion of rotor wrt B_{stator}

→ If $\omega_{rotor} = 0$, $f_{rotor} = f_e$ ← like a stationary transformer

→ If $\omega_{rotor} = \omega_{sync}$, $f_{rotor} = 0$ why? B_{net} doesn't vary w/ time

⇓ linear relationship

$$\underline{f_{rotor} = f_r = s f_e = \left(\frac{n_{sync} - n_m}{n_{sync}} \right) f_e}$$

$$\underline{f_{rotor} = \frac{P}{120} (n_{sync} - n_m)}$$

ex. A 210Vrms, $\frac{1}{3}$ hp, 4-pole, 60Hz, Y-connected induction motor runs at 1790 RPM under load. Find n_{sync} , slip speed, slip, + f_r

$$n_{sync} = \frac{120(60)}{4} = \underline{1800 \text{ RPM}}$$

$$n_{slip} = n_{sync} - n_m = 1800 - 1790 = \underline{10 \text{ RPM}}$$

$$s = \frac{n_{slip}}{n_{sync}} \times 100\% = \frac{10}{1800} \times 100\% = \underline{0.556\%}$$


$$f_r = s f_e = (0.00556)(60) = \underline{0.333 \text{ Hz}} \leftarrow \text{slow!}$$

6.3 The Equivalent Circuit of an Induction Motor

4

→ very similar to transformer circuit model as they operate in a similar fashion

→ However rotor operates @ f_r

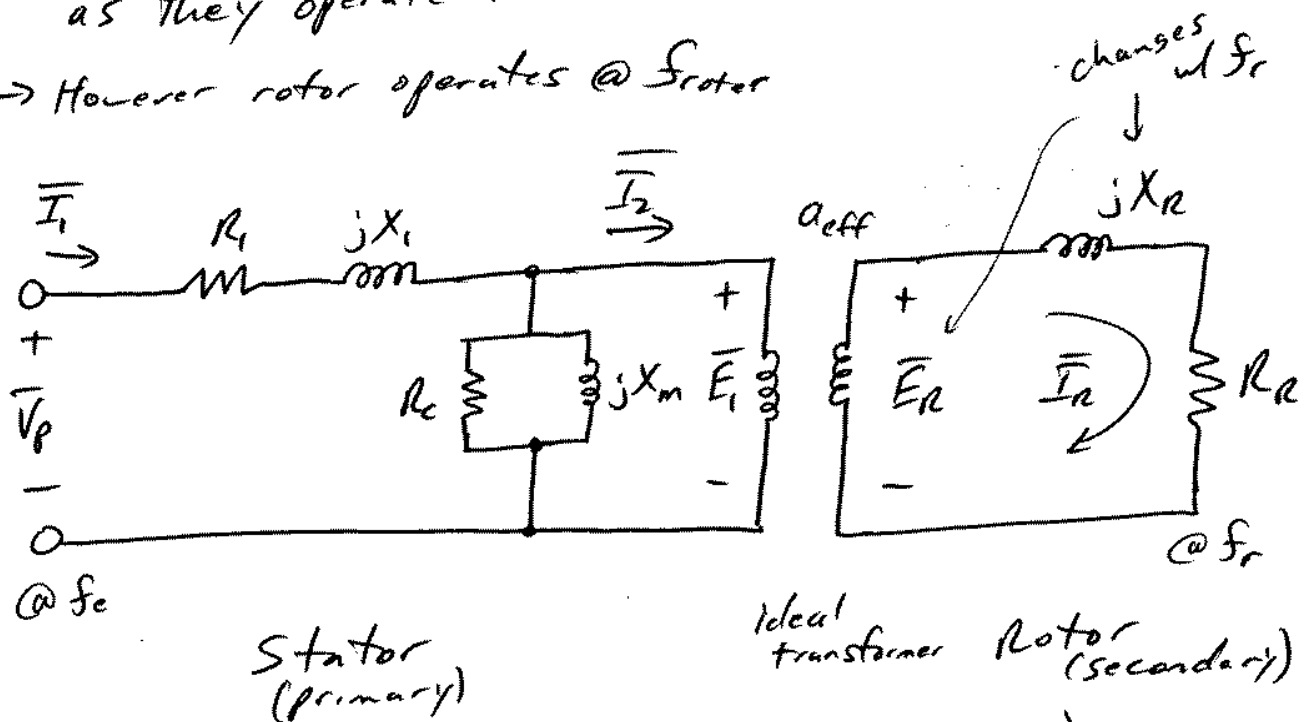

$R_1 \equiv$ stator resistance (wire resistance)

$X_1 \equiv$ stator leakage reactance (due to flux leakage)

$R_c \equiv$ equivalent core resistance (losses to eddy currents + hysteresis)

$X_m \equiv$ magnetizing reactance (will be smaller than for a transformer due to the air gap pushing equiv. reluctance up)

$a_{eff} \equiv$ effective turns ratio

$$= \frac{E_1}{E_2} = \frac{N_p}{N_r} \left. \begin{array}{l} \text{wound} \\ \text{rotor} \\ \text{only} \end{array} \right\} \uparrow \text{per-phase}$$

6.3 cont.Rotor Circuit Model

$$e_{ind} = (\vec{v}_{rel} \times \vec{B}) \cdot \vec{l} \Rightarrow v_{rel} \uparrow \quad e_{ind} \uparrow$$

If rotor motionless (locked rotor) test $v_{rel} = \text{max value}$ & $f_r = f_e$
 $\hookrightarrow E_R = E_{R0}$

If rotor @ ω_{sync} $v_{rel} = 0$ & $f_r = 0$

$\Downarrow$ linear relation

$$\underline{E_R = s E_{R0}} \quad \text{w/} \quad \underline{f_r = s f_e}$$

$\hookrightarrow$ rotor voltage & frequency functions of slip!

$$jX_R = j\omega_r L_R = j2\pi f_r L_R$$

$\uparrow$ rotor inductance
 $\uparrow$ rotor reactance


$\Downarrow$

Blocked/locked rotor test reactance

$$\underline{X_R = s X_{R0}}$$

6.3 cont.

6

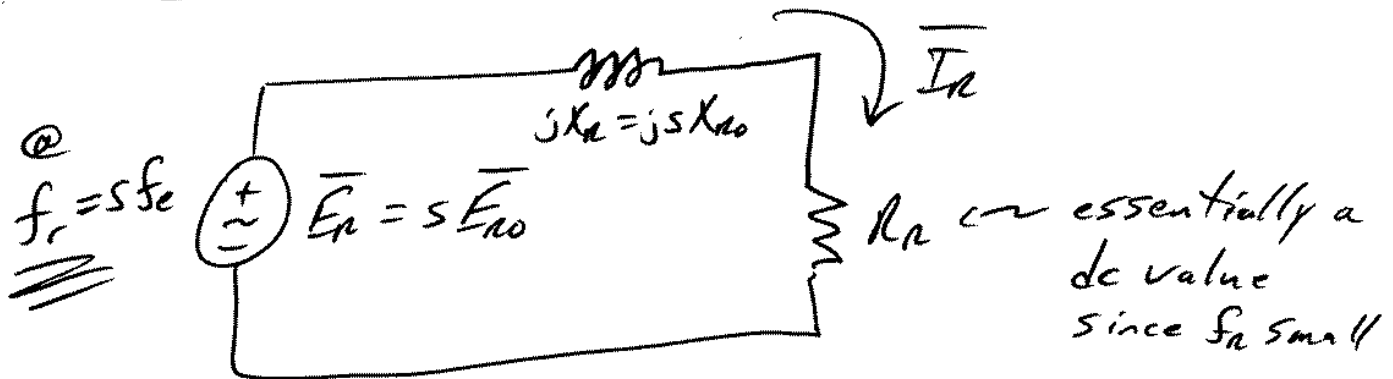
Equiv. Rotor Circuit

$$\bar{I}_r = \frac{\bar{E}_r}{R_r + jX_r} = \frac{\bar{E}_r}{R_r + jsX_{r0}}$$

$$\bar{I}_r = \frac{\bar{E}_{r0}}{\frac{R_r}{s} + jX_{r0}}$$


Define equivalent rotor impedance $\bar{Z}_{r,eq} = \frac{\bar{E}_{r0}}{\bar{I}_r}$
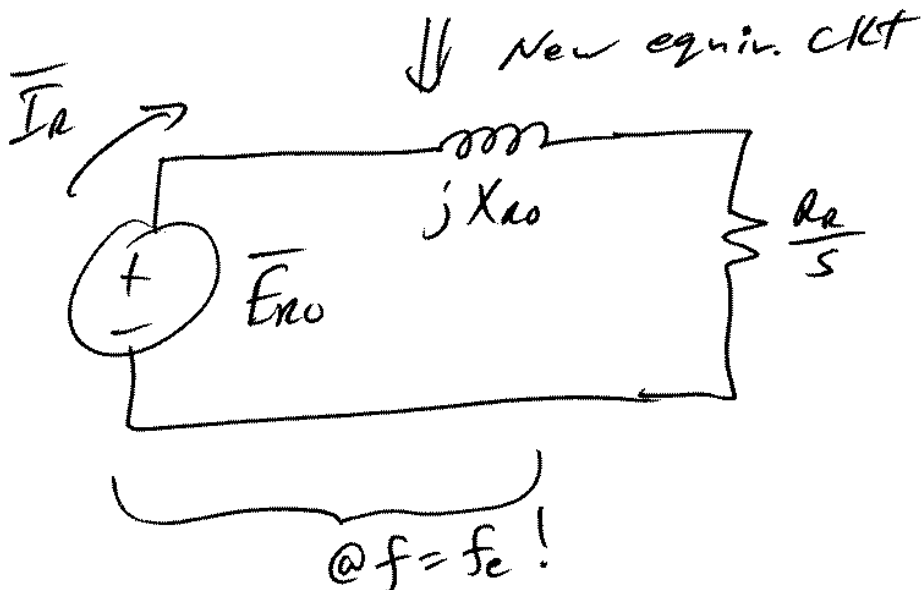
$$\bar{Z}_{r,eq} = \frac{R_r}{s} + jX_{r0} \quad (\Omega)$$



6.3 cont.

7

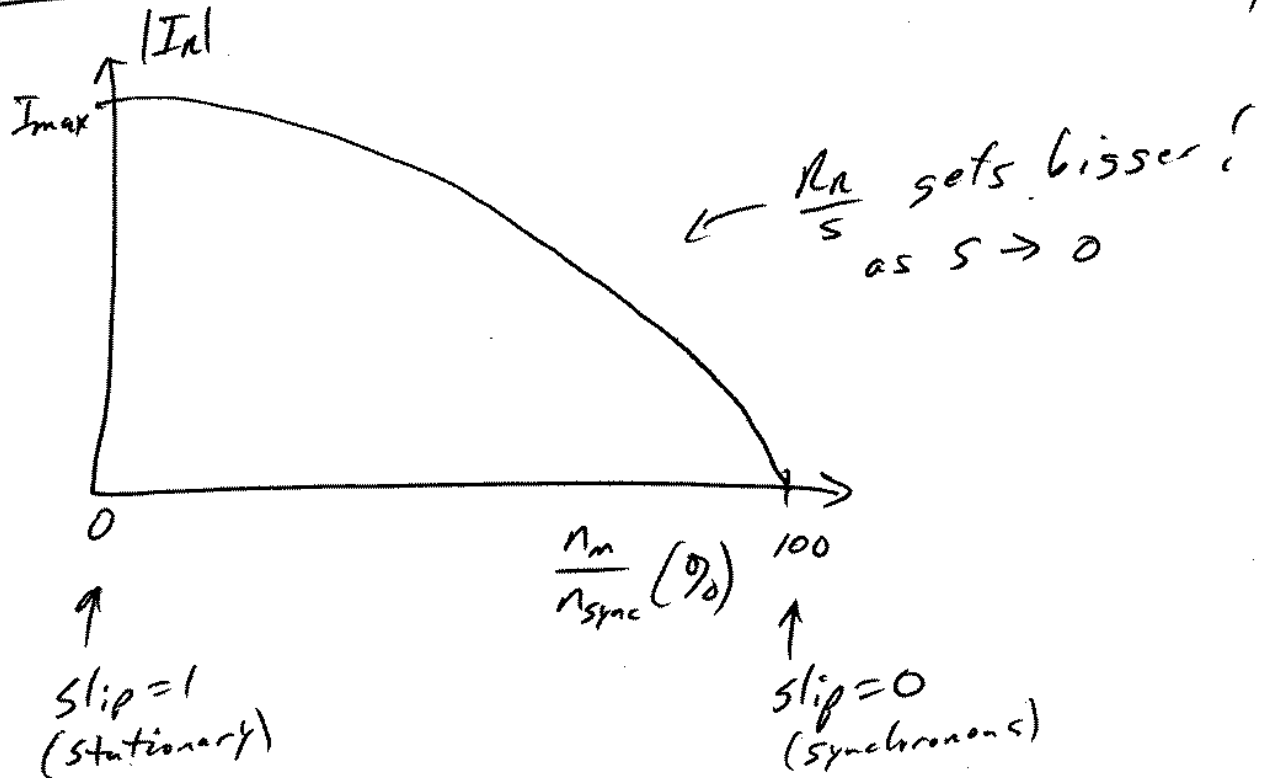Final Equiv. Circuit for Induction Motor

Refer rotor circuit over to primary (stator) side

$$\begin{aligned} \bar{E}_1 &= \bar{E}_n' = a_{eff} \bar{E}_{n0} \\ \bar{I}_2 &= \frac{\bar{I}_n}{a_{eff}} \end{aligned} \quad \left. \vphantom{\begin{aligned} \bar{E}_1 &= \bar{E}_n' = a_{eff} \bar{E}_{n0} \\ \bar{I}_2 &= \frac{\bar{I}_n}{a_{eff}} \end{aligned}} \right\} \text{from chap 2}$$

$$\begin{aligned} \bar{Z}_2 &= a_{eff}^2 \left(\frac{R_n}{s} + j X_{n0} \right) = \frac{a_{eff}^2 R_n}{s} + j a_{eff}^2 X_{n0} \\ &= \frac{R_2}{s} + j X_2 \end{aligned}$$

$R_2 + X_2$ referred resistance & reactance of rotor!


6.3 cont.

8

Very possible that we won't know

$R_L, X_{L0}, + a_{eff}$ but instead will know $R_2 + X_2$

for caged rotor machines.

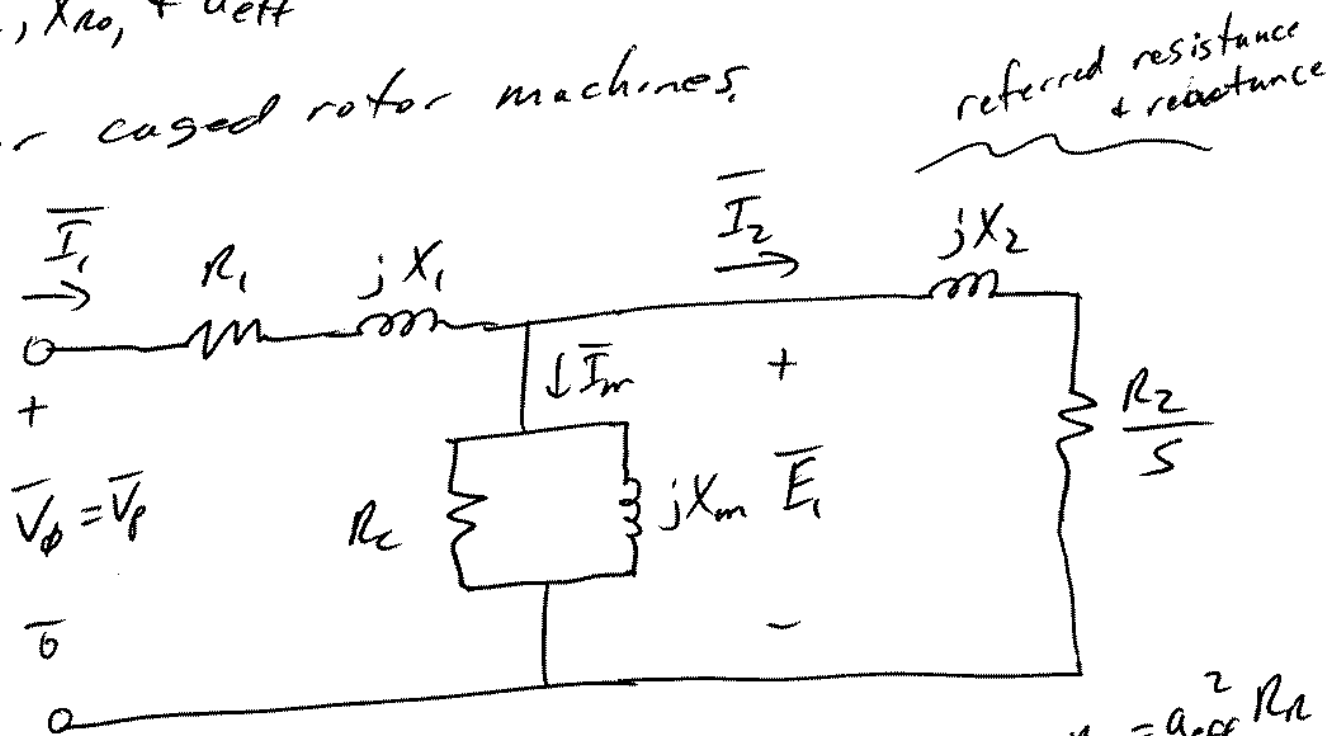

→ everything but s
is @ f_c

where $R_2 = a_{eff}^2 R_L$
 $X_2 = a_{eff}^2 X_{L0}$

Note: R_c often omitted or lumped in w/ R_2

why? $X_m \ll R_c$ due to $R_{air-gap}$ being large

So $jX_m \parallel R_c \approx \underline{jX_m}$

6.4 Power + Torque in Induction Motors

electrical

$$P_{in} = \sqrt{3} V_L I_L \cos \theta$$

air gap
 P_{AG}

$$P_{conv} = T_{ind} \omega_m$$

mechanical

$$P_{out} = T_L \omega_m$$

$$P_{scl} = 3 I_a^2 R_a$$

P_{core}
↑
actually split between
rotor & stator

$$P_{rcl}$$

$$P_{friction \text{ winding}}$$

$$P_{stray}$$

$$P_{AG} = P_{in} - P_{scl} - P_{core} \quad \leftarrow \text{power that gets over to rotor (across the air gap)}$$

$$P_{conv} = P_{in} - P_{scl} - P_{core} - P_{rcl} = T_{ind} \omega_m = T_{dev} \omega_m$$

↑
developed
torque

$$P_{out} = P_{in} - P_{all \text{ losses}} = T_{load} \omega_m$$

$$n_m \uparrow \quad \underbrace{P_{friction} \uparrow \quad P_{winding} \uparrow \quad P_{stray} \uparrow}_{\text{rotational}} \quad \text{but } P_{core} \downarrow \text{ f_{rel. smaller}}$$

In terms of the equivalent circuit:

$$P_{scl} = 3 I_1^2 R_1$$

$$P_{core} = 3 \frac{E_1^2}{R_c} = 3 E_1^2 G_c$$

$$P_{AG} = P_{in} - P_{scl} - P_{core} = 3 I_2^2 \frac{R_2}{s}$$

$$P_{rcl} = 3 I_2^2 R_2 = 3 I_a^2 R_a$$

$$\text{since } I_2 = \frac{I_a}{a_{eff}}$$

$$\& R_2 = a_{eff}^2 R_a$$

Also,

$$P_{rcl} = s P_{AG}$$

$s \rightarrow 0 \quad P_{rcl} \rightarrow 0$ makes sense

6.4 cont,

Converted power or developed mechanical power

$$P_{\text{conv}} = P_{\text{AG}} - P_{\text{RCL}} = 3I_2^2 \frac{R_2}{s} - 3I_2^2 R_2$$

$$\underline{P_{\text{conv}} = 3I_2^2 R_2 \left(\frac{1-s}{s} \right)}$$

$$= (1-s) P_{\text{AG}} \quad \leftarrow s=1 \text{ (stationary)} \\ \Rightarrow P_{\text{conv}} = 0!$$

$$T_{\text{ind}} = \frac{P_{\text{conv}}}{\omega_m} = \frac{P_{\text{AG}}}{\omega_{\text{sync}}}$$


Since the air gap power can be expressed as

$P_{\text{AG}} = P_{\text{conv}} + P_{\text{RCL}}$, it would be nice to split the $\frac{R_2}{s}$ equiv. ckt resistance into two parts - 1 for P_{conv} + 1 for P_{RCL}

$$\text{Define } R_{\text{conv}} = \frac{R_2}{s} - R_2 = R_2 \left(\frac{1-s}{s} \right)$$

$$P_{\text{conv}} = 3I_2^2 R_{\text{conv}} = 3I_2^2 R_2 \left(\frac{1-s}{s} \right)$$

$$+ P_{\text{RCL}} = 3I_2^2 R_2$$

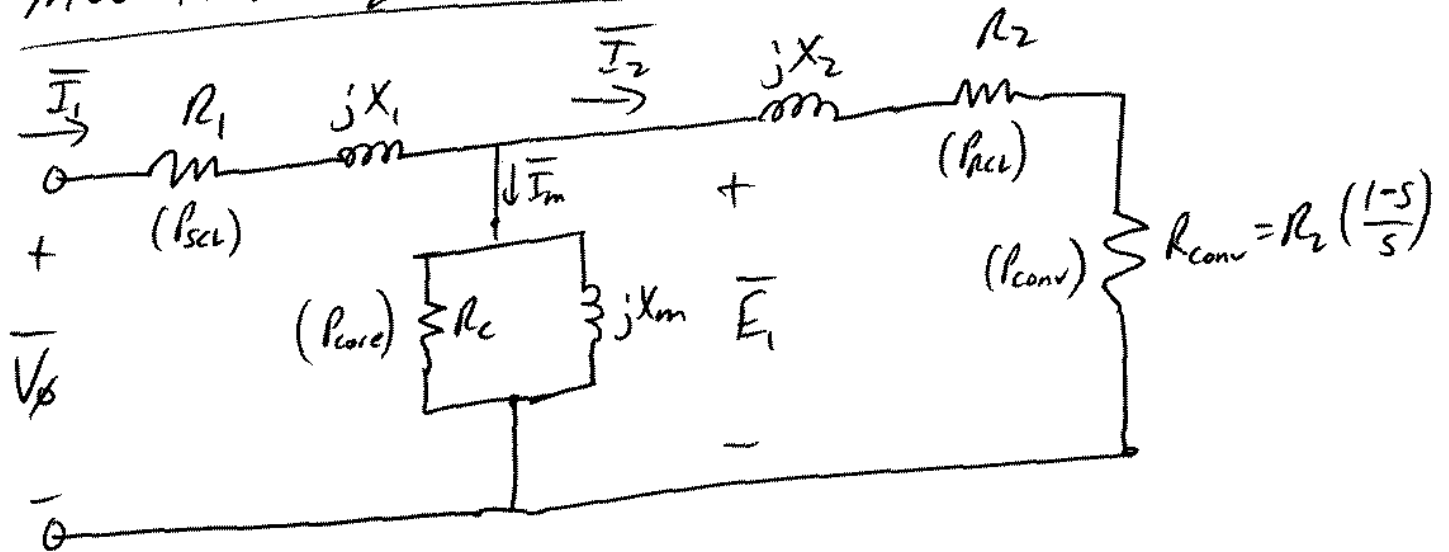6.4 cont.Modified Equiv. CKT. Model

6.4 cont.

ex. A 3- ϕ , Y-connected, 220V_{rms}, 10hp, 60Hz, 6-pole induction motor has

$$R_1 = 0.3 \Omega, X_1 = 0.5 \Omega$$

$$R_2 = 0.15 \Omega, X_2 = 0.21 \Omega$$


$$\text{and } X_m = 13.3 \Omega \text{ w/ } R_c \text{ omitted}$$

The total friction, windage, & core losses are 405W (roughly constant). For a slip of 2%, analyze the motor.

$$n_{\text{sync}} = \frac{120 f_e}{p} = \frac{120(60)}{6} = 1200 \text{ RPM}$$

$$\omega_{\text{sync}} = n_{\text{sync}} \frac{\pi}{30} = 125.663706 \text{ rad/s}$$

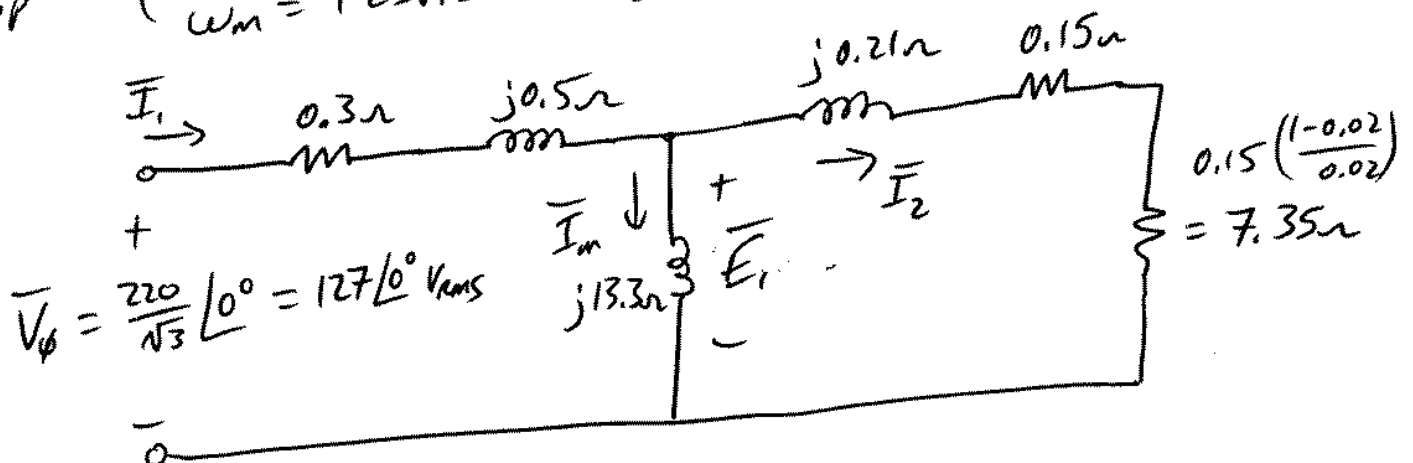shaft speed $\begin{cases} n_m = (1-s)n_{\text{sync}} = (1-0.02)1200 = 1176 \text{ RPM} \\ \omega_m = 123.1504 \text{ rad/s} \end{cases}$



6.4 cont.

13

ex. cont.

To find $\bar{I}_1$ (stator current), determine input impedance

$$\begin{aligned}\bar{Z}_{TOT} &= (0.3 + j0.5) + (j13.3) // (7.35 + 0.15 + j0.21) \\ &= (0.3 + j0.5) + (5.5563 + j3.229) \\ &= 5.8563 + j3.7913 \Omega = \underline{6.976379 / 32.91845^\circ}\end{aligned}$$

$$\bar{I}_1 = \frac{\bar{V}_\phi}{\bar{Z}_{TOT}} = \frac{220/\sqrt{3}}{6.976/32.92^\circ} = \underline{18.2067 / -32.9184^\circ \text{ A rms}}$$

$$pf = \cos \theta = \cos(32.91844675^\circ) = \underline{0.8394 \text{ lagging}}$$

$$P_{in} = \sqrt{3} V_L I_L \cos \theta = \sqrt{3} (220)(18.2067) \cos 32.918^\circ$$

$$\underline{P_{in} = 5823.8 \text{ W}}$$

$$P_{scL} = 3 |\bar{I}_1|^2 R_1 = 3 (18.2067)^2 0.3 = \underline{298.336 \text{ W}}$$

$$P_{AG} = P_{in} - P_{scL} = 5823.8 - 298.336 = \underline{5525.5 \text{ W}}$$

$$P_{conv} = (1 - s) P_{AG} = (1 - 0.02) 5525.5 = \underline{5415 \text{ W}}$$

$$P_{out} = P_{conv} - P_{rot} = 5415 - 405 = \underline{5010 \text{ W}}$$

$$= (5010) \left(\frac{1 \text{ hp}}{746 \text{ W}} \right) = \underline{6.716 \text{ hp}}$$

6.4 cont.

14

ex. cont.

$$\bar{I}_2 = \bar{I}_1 \frac{j13.3}{j13.3 + (7.5 + j0.21)} = 15.671 \angle -3.882^\circ \text{ A}_{rms}$$

$$\bar{I}_m = \bar{I}_1 - \bar{I}_2 = \frac{\bar{E}_1}{j13.3} = 8.84 \angle -92.78^\circ \text{ A}_{rms}$$

$$\bar{E}_1 = \bar{V}_\phi \frac{j13.3 / (7.5 + j0.21)}{\bar{Z}_{TOT}} = 117.6 \angle -2.78^\circ \text{ V}_{rms}$$

$$P_{RC1} = 3 |\bar{I}_2|^2 R_2 = 3 (15.67)^2 (0.15)$$

$$\underline{\underline{P_{RC1} = 110.5 \text{ W}}}$$

$$P_{RC1} = s P_{AG} = (0.02)(5525.5) = 110.5 \text{ W}$$

6.4 cont.

15

ex. cont.

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{5010}{5823.8} \times 100\% = \underline{\underline{86\%}}$$

$$\tau_{ind} = \frac{P_{ac}}{W_{sync}} = \frac{5525.5}{125.6637} = \underline{\underline{43.97 \text{ Nm}}}$$

$$\tau_{load} = \frac{P_{out}}{W_m} = \frac{5010}{123.1504} = \underline{\underline{40.682 \text{ Nm}}}$$

OR in English units

$$\tau_{ind} = (43.97) \left(0.7372 \frac{\text{lb-ft}}{\text{Nm}} \right) = \underline{\underline{32.4 \text{ lb-ft}}}$$


$$\tau_{load} = 40.682 (0.7372) = \underline{\underline{30 \text{ lb-ft}}}$$

6.5 Induction Motor Torque-Speed

16

Characteristics

→ very important topic for all motors

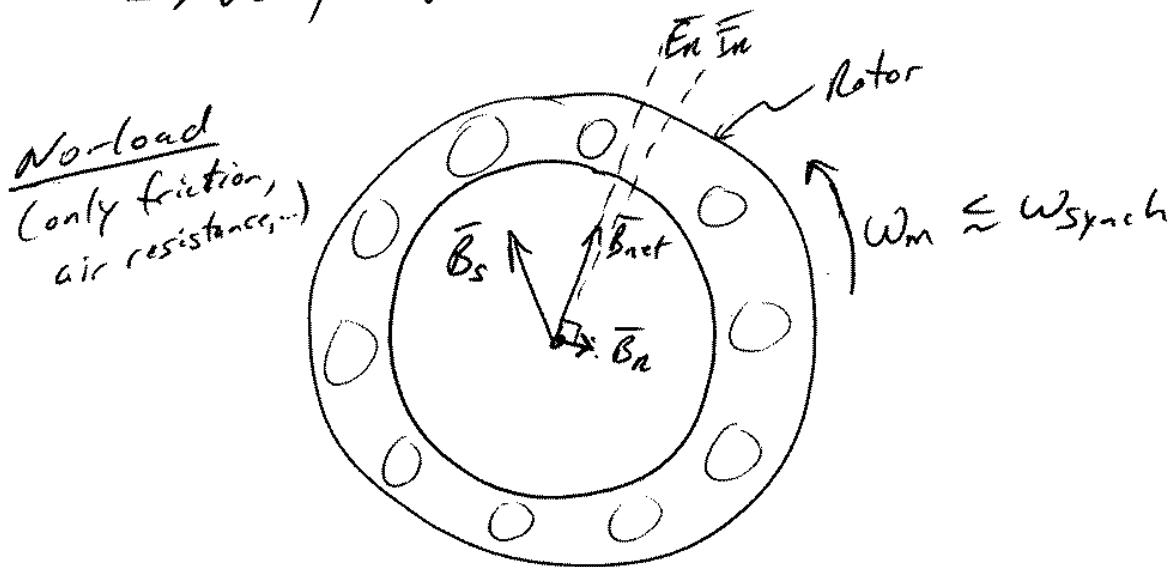

* $\vec{B}_{net}$ due to $\vec{I}_m$ & $|\vec{I}_m| \propto |\vec{E}_r|$

* s very small since $\omega_m \approx \omega_{sync}$

↳ f_r very small & v_{rel} very small

↳ $\vec{E}_r$ very small & $\vec{I}_r$ very small

↳ sX_{ro} very small


⇓
 $\vec{E}_r + \vec{I}_r$ approximately in phase!

* $\vec{B}_r \approx 90^\circ$ behind $\vec{B}_{net}$ & small $\phi \approx 90^\circ$

$$\vec{T}_{ind} = k \vec{B}_r \times \vec{B}_{net} \rightarrow T_{ind} = k B_r B_{net} \sin \phi$$

6.5 cont.

17

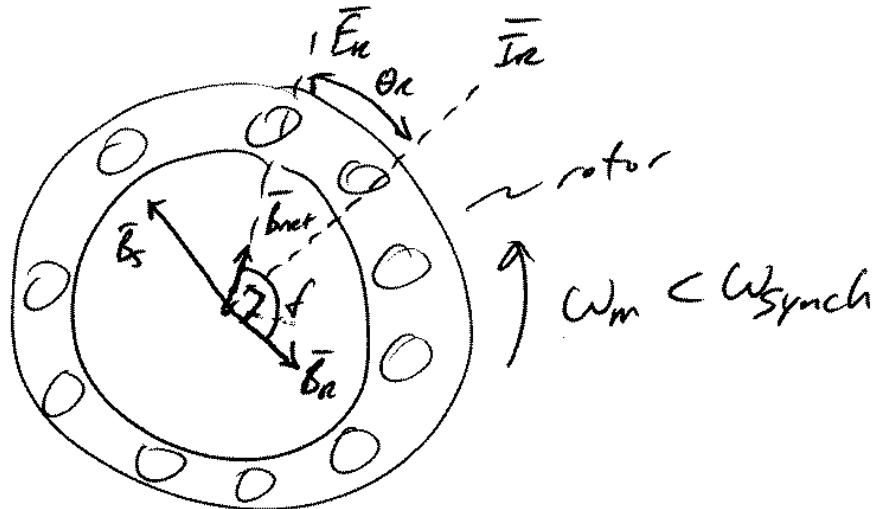Big Load

* s larger $\rightarrow f_r$ bigger + v_{rel} bigger

$\hookrightarrow \bar{E}_r$ bigger + $\bar{I}_r$ bigger

Now sX_{ro} is bigger $\Rightarrow \bar{I}_r$ less $\bar{E}_r$

* $\bar{B}_r$ now more than 90° behind $\bar{B}_{net}$ ($\delta > 90^\circ$)
and larger

$|\bar{B}_r| \uparrow \Rightarrow$ more torque (bigger effect)
but $\sin \delta \downarrow \Rightarrow$ less torque


At some point, the decrease in $\sin \delta$ is equal to increase due to $|\bar{B}_r|$ and the increase in T_{ind} stops $\Rightarrow$ any further increase in load will cause motor to stop!

6.5 cont.

18


Summary
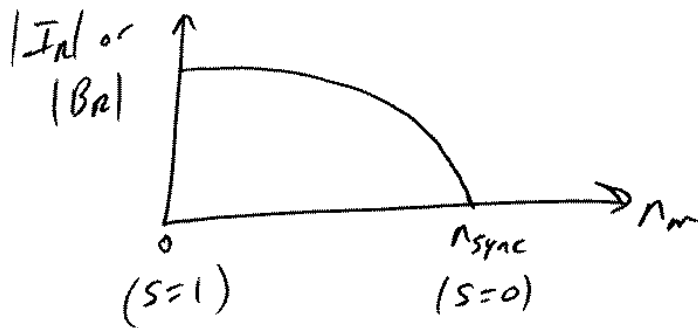
$$1) \bar{B}_R \propto \bar{I}_R \quad \text{and} \quad \bar{I}_R \uparrow \text{ w/ } s \uparrow$$



$$2) |\bar{B}_{net}| \approx \text{constant} \quad \text{assuming losses across } R_1 + jX_1 \text{ are small}$$

$$\propto |\bar{I}_m| \propto |\bar{E}_1|$$

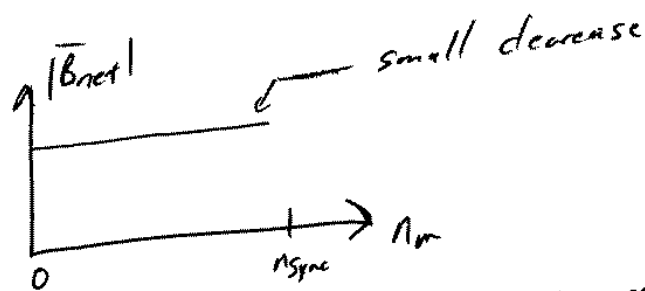

$$3) \sin \delta \rightarrow \delta = \theta_R + 90^\circ$$

power factor angle of rotor


$$\sin(\theta_R + 90^\circ) = \cos \theta_R = \text{pf}_R$$

$$\text{where } \theta_R = \tan^{-1}\left(\frac{X_R}{R_R}\right) = \tan^{-1}\left(\frac{sX_{R0}}{R_R}\right)$$



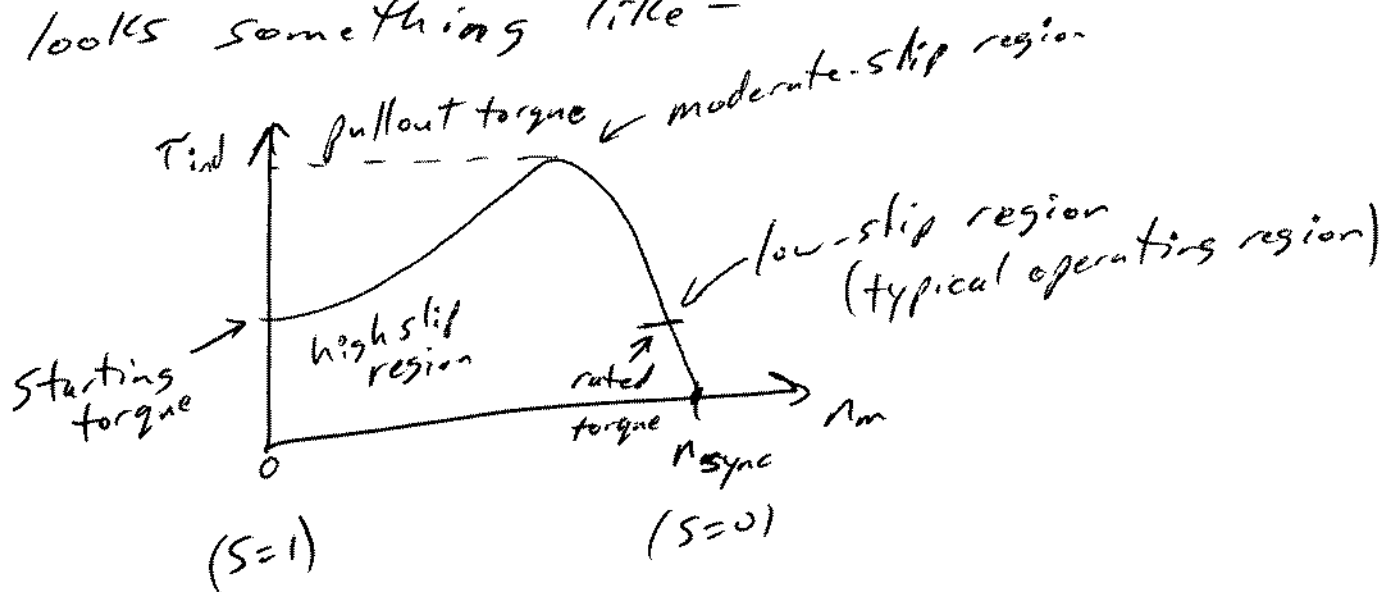6.5 cont.

The overall Torque vs n_m curve then looks something like -



→ pullout torque usually 2 to 2.5 times rated load torque

→ starting torque ~ 1.5 times rated load torque
to 2


$$T_{ind} = \frac{P_{conv}}{\omega_m} = \frac{P_{AG}}{\omega_{sync}}$$

↳ Can we put this in terms of equivalent ckt parameters?


yes!

6.5 cont.

20

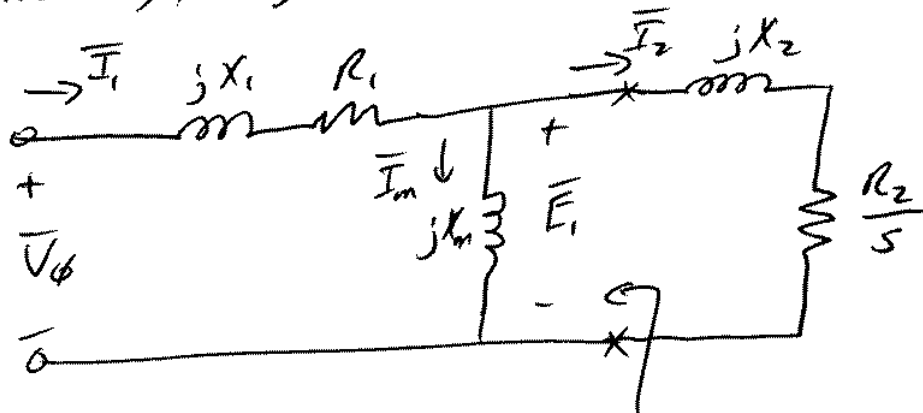Ignoring / neglecting R_{core} 

Find Thevenin equivalent circuit

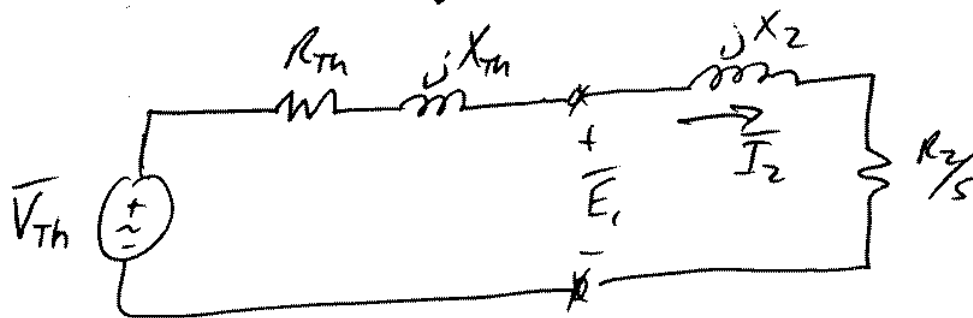

$$\bar{V}_{Th} = \bar{V}_\phi \left(\frac{jX_m}{R_1 + jX_1 + jX_m} \right)$$

magnitude $V_{Th} = \frac{V_\phi X_m}{\sqrt{R_1^2 + (X_1 + X_m)^2}} \approx \frac{V_\phi X_m}{X_1 + X_m} \quad (R_1 \ll X_1 + X_m)$

$$\bar{Z}_{Th} = R_{Th} + jX_{Th} = \frac{jX_m (R_1 + jX_1)}{R_1 + j(X_1 + X_m)}$$

approx. $\hookrightarrow R_{Th} \approx R_1 \left(\frac{X_m}{X_1 + X_m} \right)^2$

$$X_{Th} \approx X_1$$

6.5 cont.

21

$$\bar{I}_2 = \frac{\bar{V}_{Th}}{R_{Th} + \frac{R_2}{s} + j(X_2 + X_{Th})}$$

$$I_2 = \frac{V_{Th}}{\sqrt{(R_{Th} + \frac{R_2}{s})^2 + (X_2 + X_{Th})^2}}$$

$$P_{AG} = 3 I_2^2 \frac{R_2}{s}$$

$$T_{ind} = \frac{P_{AG}}{\omega_{sync}}$$

$$T_{ind} = \frac{3 V_{Th}^2 \left(\frac{R_2}{s}\right)}{\omega_{sync} \left[\left(R_{Th} + \frac{R_2}{s}\right)^2 + (X_2 + X_{Th})^2 \right]}$$

Notes:

- * Can stop induction motor by reversing $\vec{B}_{stator}$ (i.e. switch phases)
- * T_{ind} vs $n_m \sim$ linear near n_{sync} (low-slip)
 - $\rightarrow \frac{R_2}{s} \gg X_R$
- * can't exceed pull-out torque (motor stops)
- * starting torque > full-load torque (else it won't start!)
- * $T_{ind} \propto (V_{Th})^2$
- * $n_m > n_{sync} \Rightarrow$ generator!

6.5 cont.

22

Be nice to know $T_{ind,max}$ (ALFA pullout torque)


$$T_{ind,max} = \frac{(P_{AG})_{max}}{\omega_{sync}}$$

where

$$P_{AG} = 3 I_2^2 \frac{R_2}{s}$$

Need to find where P_{AG} is maximized

→ Back in Circuits, we found for the ckt

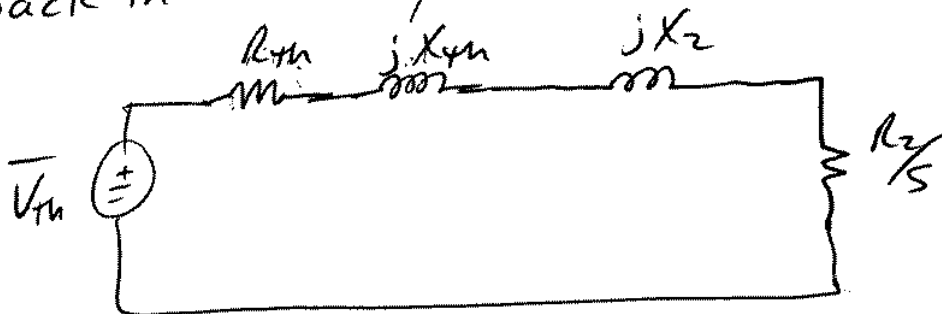

Max. power is transferred when

$$\frac{R_2}{s_{max}} = \sqrt{R_{th}^2 + (X_{th} + X_2)^2}$$

$$s_{max} = \frac{R_2}{\sqrt{R_{th}^2 + (X_{th} + X_2)^2}}$$

* directly proportional to $R_2 = a_{eff}^2 R_L$!

6.5 cont.

Putting s_{max} into our T_{ind} eqn yields-

$$(T_{ind})_{max} = T_{max} = \frac{3 V_{Th}^2}{2 \omega_{sync} [R_{Th} + \sqrt{R_{Th}^2 + (X_{Th} + X_2)^2}]}$$

Note! T_{max} doesn't depend on $R_2 = a_{eff}^2 R_R$
 but s_{max} does depend on $R_2 = a_{eff}^2 R_R$



By controlling R_R , we can put T_{max}
 at whatever n_m we want!
 (speed)

Application - move T_{max} to near $n_m = 0$
 when starting motor by increasing
 R_R ($s_{max} \approx 1$ corresponds to $n_m = 0$);
 remove once motor gets moving
 ⇓
 more starting torque!

6.5 cont.

24

ex. Revisit earlier example

3 ϕ , Y-connected, 220 V_{rms}, 10 hp, 60 Hz, 6-polemotor w/ $R_1 = 0.3 \Omega$ $X_1 = 0.5 \Omega$ $R_2 = 0.15 \Omega$ $X_2 = 0.21 \Omega$ and $X_m = 13.3 \Omega$

where

$$n_{sync} = 1200 \text{ RPM} \quad \& \quad \omega_{sync} = 125.6637 \text{ rad/s}$$

Find S_{max} , T_{max} , $T_{start-up}$

$$\bar{V}_{Th} = \bar{V}_\phi \frac{jX_m}{R_1 + j(X_1 + X_m)} = \left(\frac{220}{\sqrt{3}} \angle 0^\circ \right) \frac{j13.3}{0.3 + j(0.5 + 13.3)}$$

$$= 122.386 \angle 1.2454^\circ \text{ V}_{rms} \quad \left(\frac{220}{\sqrt{3}} = 127 \text{ V}_{rms} \right)$$

$$\bar{Z}_{Th} = \frac{jX_m(R_1 + jX_1)}{R_1 + j(X_1 + X_m)} = \frac{(j13.3)(0.3 + j0.5)}{0.3 + j(13.3 + 0.5)}$$

$$= 0.278523 + j0.48794 \Omega$$

$$S_{max} = \frac{R_2}{\sqrt{R_{Th}^2 + (X_{Th} + X_2)^2}} = \frac{0.15}{\sqrt{0.2785^2 + (0.488 + 0.21)^2}}$$

$$= 0.1996 \approx 20\% \text{ slip}$$

6.5 cont.

ex. cont.

$$T_{max} = \frac{3V_{th}^2}{2\omega_{sync} \left[R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_2)^2} \right]}$$

$$= \frac{3(127.386)^2}{2(125.6637) \left[0.2785 + \sqrt{0.2785^2 + (0.488 + 0.21)^2} \right]}$$

$$\underline{T_{max} = 173.6 \text{ N}\cdot\text{m} \approx 128 \text{ ft}\cdot\text{lbs}}$$

$$\textcircled{a} \quad \omega_{max} = (1 - s_{max}) \omega_{sync} = \underline{100.58 \text{ rad/s}}$$

$$n_{max} = (1 - s_{max}) n_{sync} = \underline{960.5 \text{ RPM}}$$

$$T_{start} (s=1) = \frac{3V_{th}^2 (R_2/s)}{\omega_{sync} \left[(R_{th} + R_2/s)^2 + (X_{th} + X_2)^2 \right]}$$

$$= \frac{3(127.386)^2 (0.15)}{125.6637 \left[(0.2785 + 0.15)^2 + (0.488 + 0.21)^2 \right]}$$

$$= \underline{79.97 \text{ N}\cdot\text{m} = 59 \text{ ft}\cdot\text{lbs}}$$

6.6 Variations in Induction Motor Torque-Speed Characteristics

Trade-offs

- * Bigger $R_a \rightarrow$ better start-up torque but worse steady-state efficiency (if R_a can't be varied as w/ wound rotor motors)
- * It is possible, w/in limits, to cause R_a to vary w/ f_r based on rotor bar cross section (read section 7.6)
- * Leads to various "design classes" for cage rotor induction motors as designated by Nat'l Electrical Manufacturers Assoc. (NEMA)

6.7 Trends in Induction Motor Design

- * Better materials e.g. mag. steels, insulation, ...
- * Better efficiency
- * Better construction (e.g. smaller air gaps)

6.8 Starting Induction Motors

27

→ Got to be careful w/ initial current surge;
can cause voltage dips

→ Can estimate start-up current from NEMA code letter
Table shown in Fig 6-34

$$S_{\text{start}} = (\text{rated hp})(\text{code letter factor})$$

$$I_{L, \text{start}} = \frac{S_{\text{start}}}{\sqrt{3} V_T}$$

e.x. Use earlier 10hp motor example w/ 220Vrms
and assume code letter B

$$S_{\text{start}} = (10 \text{ hp}) \left(3.55 \frac{\text{KVA}}{\text{hp}} \right) = 35.5 \text{ KVA}$$

← upper bound to be safe

$$I_{L, \text{start}} = \frac{35.5 \times 10^3}{\sqrt{3} (220)} = \underline{\underline{93.16 \text{ Arms}}}$$

(earlier example had $I_L = 18.2 \text{ Arms}$ @ 2% slip)

6.8 cont.

How can we deal w/ this large current?

→ In-line inductors to damp down current surge (or resistors)

→ Start w/ lower V_T before applying full V_T (reduces torque) using switches and/or an auto transformer

→ Also include various protection features

- * Short ckt protection w/ fuses

- * Overload protection (some sort of thermal breaker)

- * Under voltage protection (relay opens)

6.9 Speed Control of Induction Motors

29

* Various solid-state drives can accomplish this by:

1) Vary f_c/p thence synchronous speed

2) vary slip s by changing R_r and/or V_T

* read on own

6.10 Solid-State Induction Motor Drives

→ can provide 0 to 120 Hz and

0 to V_{rated} both!

→ read on own

6.11 Determining Circuit Model Parameters


30

Want to find/measure $R_1, R_2, X_1, X_2, \text{ \& } X_m$.


No-Load Test

- * Find rotational losses (e.g., friction, windage)
- * Slip very small

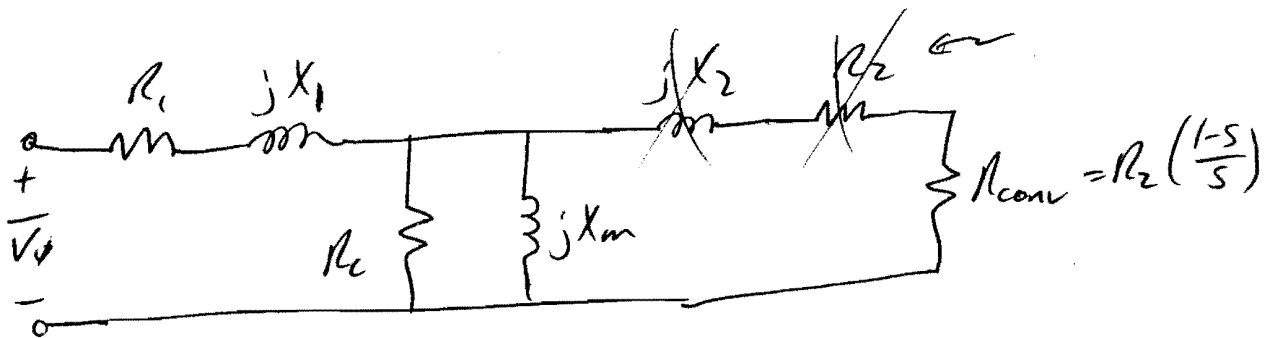$\hookrightarrow R_{\text{conv}} = R_2 \left(\frac{1-s}{s} \right) \gg R_2 \text{ and } X_2$
@ No-load, this accounts for mech losses



↓ Combine R_c and R_{conv}

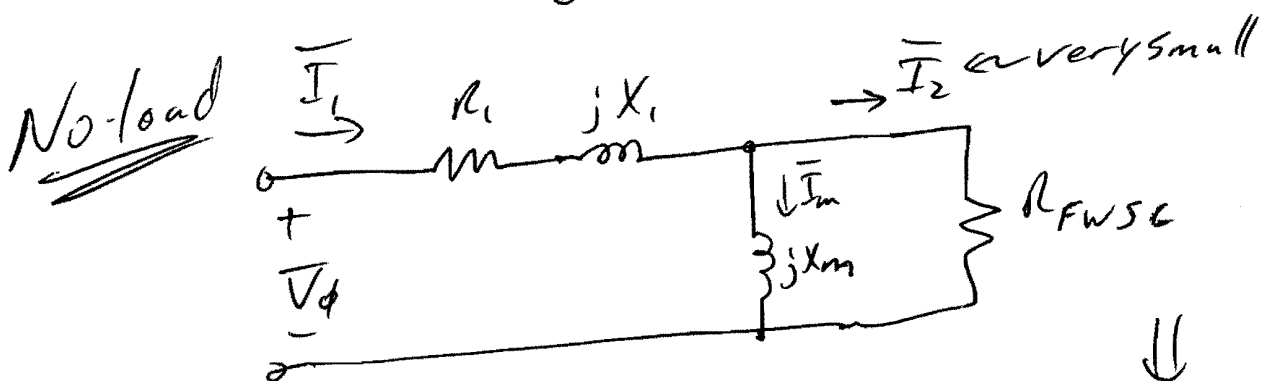

- * much bigger than X_m
 * lump together friction, windage, stray & core losses

6.11 cont.No-load cont.

$$P_{in, nl} = P_{sc} + \underbrace{P_{core} + P_{F+W} + P_{misc}}_{P_{rot}} \quad \leftarrow \text{AKA: } P_{stray}$$

$$= 3|\bar{I}_1|^2 R_1 + P_{rot}$$

Most of voltage drops across $jX_1 + jX_m$,

So

$$|Z_{eq}| = \frac{V_\phi}{I_{1, nl}} \approx \underline{X_1 + X_m} \quad \leftarrow \begin{array}{l} \text{assumes} \\ R_{F+W} \parallel jX_m \\ \approx jX_m \end{array}$$

So, what do we measure?

- 1) All 3 line currents - $I_{1, nl} = \frac{I_A + I_B + I_C}{3}$
- 2) All 3 line-to-line voltages - $V_{LL, nl} = \frac{V_{AB} + V_{BC} + V_{CA}}{3}$
(full rated voltage)
- 3) $P_{in, nl}$

$\uparrow$
 $V_{T, nl}$
Taking averages

Still need more info!

6.11 cont.

32

DC Test for Stator Resistance

$$\left. \begin{array}{l} Y\text{-conn: } R_T = 2R_1 \Rightarrow R_1 = R_T/2 \\ \Delta\text{-conn: } R_T = \frac{2}{3}R_1 \Rightarrow R_1 = \frac{3}{2}R_T \end{array} \right\} \underline{\underline{\text{Result}}}$$

How?

1) Use ohmmeter, measure R_{TAB} , R_{TBC} , R_{TCA}

$$R_T = \frac{R_{TAB} + R_{TBC} + R_{TCA}}{3}$$

2) More accurate to apply DC test voltage such that $I_{DC} = I_{L, \text{rated}}$ (heats up windings, simulating operating conditions)

↳ Measure I_{DC} w/ multimeter
Measure V_{DC} w/ multimeter

$$R_T = \frac{V_{DC}}{I_{DC}}$$

for best accuracy repeat test across AB, BC, & CA and average

$$R_T = \frac{\left(\frac{V_{DC}}{I_{DC}}\right)_{AB} + \left(\frac{V_{DC}}{I_{DC}}\right)_{BC} + \left(\frac{V_{DC}}{I_{DC}}\right)_{CA}}{3}$$

6.11 cont.

33

Locked-Rotor Test ($s=1$) (AKA: Blocked-Rotor Test)


→ analogous to transformer short ckt test

→ Since $s=1$, $R_2/s = R_2$ (smaller #) and

$$R_{conv} = 0$$

→ $\bar{I}_m$ very small in comparison to $\bar{I}_2$ since $R_2 + jX_2$ are smaller than $R_c \parallel jX_m$

Equiv. Ckt for Locked-Rotor Test

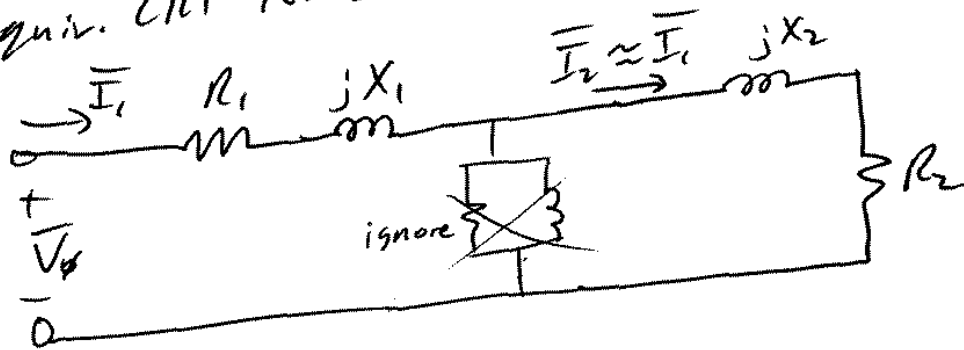

Issue: What do we do about frequency?

In normal op'n, $f_r \approx 1$ to 3 Hz at slips of 2 to 4%.w/ locked rotor $f_c = f_r$, so we can get abnormal results! Some testers will reduce f_c to 25% of normal [e.g. $0.25(60) = 15\text{ Hz}$].

Others just use 60 Hz + accept inaccuracy.

6.11 cont.

34

Locked-Rotor cont.

What do we measure?

1) Measure all 3 line currents - $I_{L,LR} = \frac{I_A + I_B + I_C}{3}$
 (~ $I_{L,rated}$, adjust V_T to get)

2) Measure all 3 line-line voltages - $V_{LL,LR} = \frac{V_{AB} + V_{BC} + V_{CA}}{3}$
 (adjust w/ variac)
 $\uparrow$
 $V_{T,LR}$

3) Measure $P_{in,LR}$

Using this data, we get:

$$pf_{LR} = \cos \theta_{LR} = \frac{P_{in}}{\sqrt{3} V_{T,LR} I_{L,LR}}$$

$$\hookrightarrow \theta_{LR} = \cos^{-1}(pf_{LR}) \leftarrow \text{also impedance phase } \phi$$

$$|\bar{Z}_{LR}| = \frac{V_{\phi}}{I_1} = \frac{V_{T,LR}}{\sqrt{3} I_{L,LR}}$$

$$\bar{Z}_{LR} = |\bar{Z}_{LR}| \angle \theta_{LR} = R_{LR} + j X'_{LR}$$

$$= |\bar{Z}_{LR}| \cos \theta_{LR} + j |\bar{Z}_{LR}| \sin \theta_{LR}$$

6.11 cont.

Now, we can start getting some equivalent values.

$$R_{LR} = |Z_{LR}| \cos \theta_{LR} = R_1 + R_2$$

R_1 is known from DC test

$$\underline{R_2 = R_{LR} - R_1}$$

$$X_{LR}' = X_1' + X_2' \quad \leftarrow \text{at } f_c = f_{\text{test}}$$

$$X_{LR} = \frac{f_{\text{rated}}}{f_{\text{test}}} X_{LR}' = X_1 + X_2 \quad \leftarrow \text{No way to separate easily}$$

Fig. 6-56

Rule-of-thumb division of $X_1 + X_2$

Rotor Design	X_1	X_2
Wound	$0.5 X_{LR}$	$0.5 X_{LR}$
Design A	$0.5 X_{LR}$	$0.5 X_{LR}$
B	$0.4 X_{LR}$	$0.6 X_{LR}$
C	$0.3 X_{LR}$	$0.7 X_{LR}$
D	$0.5 X_{LR}$	$0.5 X_{LR}$

6.11 cont.

ex. A 5 hp, 60 Hz, Y-connected, 210 V_{rms}, 4-pole, design class A motor is tested to determine its per-phase equivalent circuit. The following results are measured -

No-Load Test: 210.5 V_{rms} = $V_{T,ave}$, $I_{L,ave}$ = 4.45 A_{rms},
and 250 W = $P_{in,NL}$

Locked Rotor Test: $V_{T,ave,Lr}$ = 20.66 V_{rms}, $I_{L,ave,Lr}$ = 12.8 A_{rms},
 $P_{in,Lr}$ = 480 W @ $f_e = 15$ Hz

DC Test: V_{DC} = 19.8 V I_{DC} = 12.83 A

From DC Test: $R_T = \frac{V_{DC}}{I_{DC}} = \frac{19.8}{12.83} = 1.54326 \Omega = 2 R_i$
(6-61)

$$\underline{R_i = 0.77163 \Omega}$$

From No-Load Test: $V_\phi = \frac{210.5}{\sqrt{3}} = 121.532$ V_{rms} ← Y-connected

$$(6-60) \quad |Z_{eq}| = \frac{V_{\phi,NL}}{I_{L,NL}} = \frac{121.532}{4.45} = 27.3106 \Omega \cong X_i + X_m$$

$$(6-25) \quad P_{scl} = 3 I_1^2 R_i = 3 (4.45)^2 0.77163 = 45.84 \text{ W}$$

$$(6-58) \quad P_{rot} = P_{in,NL} - P_{scl,NL} = 250 - 45.84 = 204.16 \text{ W}$$

6.11 cont.ex. cont.

From Locked Rotor Test:

$$(6-63) |Z_{LR}| = \frac{V_{\phi}}{I_L} = \frac{28.66/\sqrt{3}}{12.8} = 1.2927 \Omega$$

$$(6-62) pf = \cos \theta_{LR} = \frac{P_{in,LR}}{\sqrt{3} V_{T,LR} I_{L,LR}} = \frac{480}{\sqrt{3} (28.66) 12.8} = 0.7554$$

$$\hookrightarrow \theta_{LR} = 40.937^\circ$$

$$\bar{Z}_{LR} = |Z_{LR}| \angle \theta_{LR} = 1.2927 \angle 40.937^\circ = 0.97656 + j0.84703 \Omega$$

$\swarrow R_{LR}$ $\swarrow X'_{LR}$

$$(6-65) R_{LR} = R_1 + R_2 = 0.97656 \Rightarrow R_2 = 0.97656 - 0.77163 \Omega$$

$$\underline{R_2 = 0.2049 \Omega}$$

$$(6-68) X_{LR} = \frac{f_{rated}}{f_{test}} X'_{LR} = \left(\frac{60}{15}\right)(0.84703) = 3.38812 \Omega$$

$$= X_1 + X_2$$


Per Fig. 6-56, $X_1 = 0.5 X_{LR}$ & $X_2 = 0.5 X_{LR}$ for class A

$$\underline{X_1 = X_2 = 1.694 \Omega}$$


$$X_m = 27.3106 - 1.69406 = \underline{25.61654 \Omega}$$

6.11 cont

ex. cont.

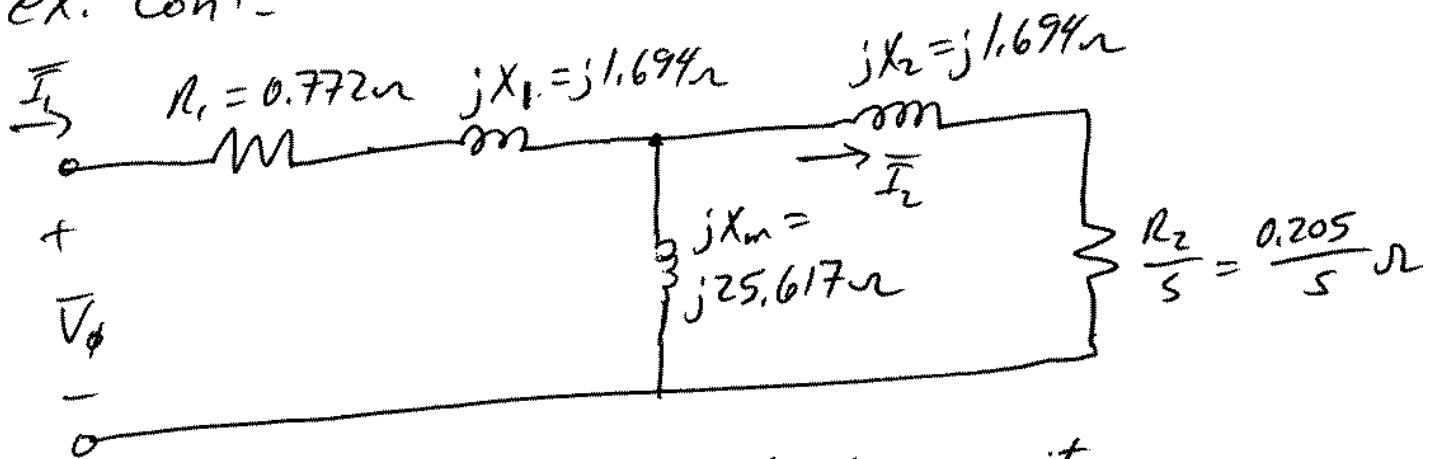

Per-phase Equivalent Circuit.

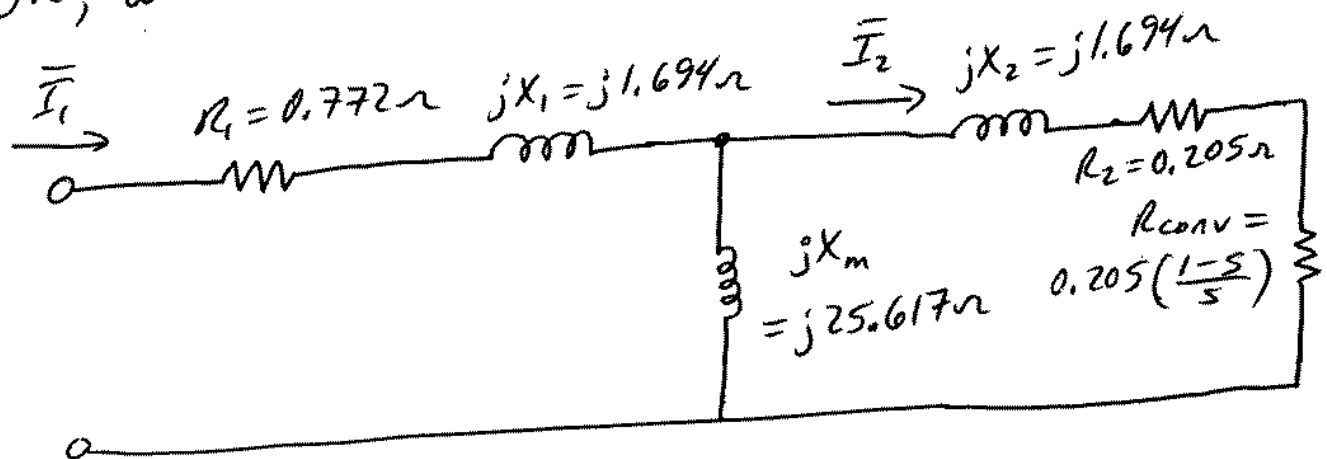OR, with R_2 & R_{conv} separated,

6.12 Induction Generator


- * If an induction machine is driven at a mechanical speed $n_m > n_{sync} \Rightarrow$ Generator
- * As shown in typical torque-speed characteristic, there is a maximum possible induced torque for an induction generator ($T_{pushover}$). If n_m exceed $n_{pushover}$, the generator will overspeed. why?

Below $n_{pushover}$, $\sum \tau = \tau_{\text{prime mover}} + \tau_{\text{induced}} = 0$

$$\hookrightarrow \tau = J\alpha \Rightarrow \alpha = 0 \text{ (No acceleration)}$$

Above $n_{pushover}$, $\sum \tau = \tau_{\text{prime mover}} + \tau_{\text{induced}} > 0$

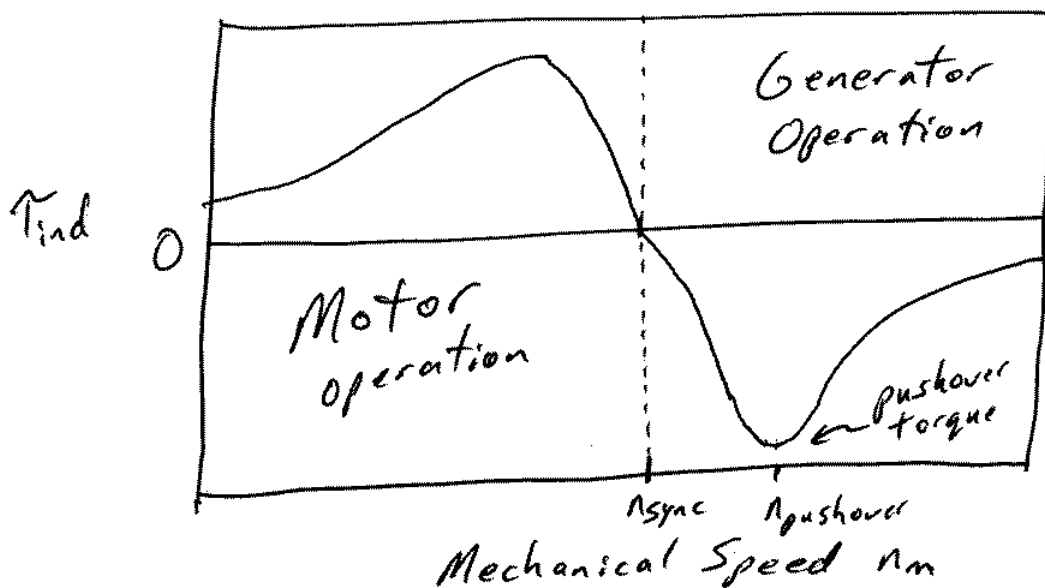$\Rightarrow \alpha > 0$ (generator accelerates until something gives)



6.12 cont.

Other problems w/ induction generators:

* Can NOT produce reactive power

* Can NOT control output voltage



Need external source

Advantage - very simple construction / light

- used (some) w/ windmills

(rectify AC output to DC, convert back to 60Hz AC)

- also used to recover / scavenge energy / power (competes w/ permanent magnet generators).

6.13 Induction Motor Ratings

Output Power (e.g. $\frac{1}{2}$ hp)

Voltage (e.g. 208 Vrms) $\leftarrow$ what will saturate mag. core

Current (e.g. 10 Arms) $\leftarrow$ what will overheat windings

power factor

Speed

Nominal efficiency

NEMA Design Class

Start Code

$\Rightarrow$ Not all of these quantities will be given/
available on all motors