

ex. Ideal Transformers Circuit

Say I have a portable generator w/ an output of 120Vrms that I want to use to power some load ($\bar{Z}_L = 6 + j2\Omega$) in a barn 200m away.

For twin-lead (each way) $R = \frac{\ell}{\sigma A} (2) \leftarrow \text{current goes out + back}$



$L = \frac{\mu \ell}{\pi} \cosh^{-1}\left(\frac{d}{2a}\right) \leftarrow \text{counts both wires}$

For 12AWG, $2a = 2.053 \text{ mm}$ $\sigma_{\text{cu}} = 5.8 \times 10^7 \text{ S/m}$
Copper wire $d \approx 6 \text{ mm}$

$$R = \frac{2(200)}{(5.8 \times 10^7) \pi \left(\frac{2.053 \times 10^{-2}}{2}\right)^2} = 2.08336 \Omega$$

$$L = \frac{(4\pi \times 10^{-7})(200)}{\pi} \cosh^{-1}\left(\frac{6 \text{ mm}}{2.053 \text{ mm}}\right) = 1.39 \times 10^{-4} \text{ H}$$

$$\bar{Z}_L = j\omega L = j 2\pi(60)(1.39 \times 10^{-4}) = j0.0523 \Omega$$

$$\bar{Z}_{\text{wire}} = 2.08336 + j0.0523 \Omega \leftarrow \text{or nearly negligible}$$


$\Downarrow$ Round to

$$\bar{Z}_{\text{wire}} = 2.1 + j0.05 \Omega$$

ex. cont.

How much of a difference in terms of power + efficiency will using step-up and step-down transformers make?

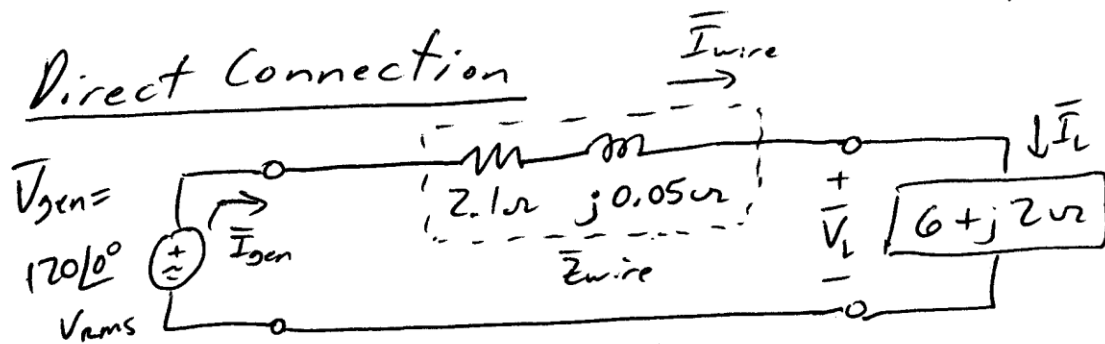Assume 1:4 (step-up) & 4:1 (step-down) transformers are available. $\nearrow$ voltage limits for wiring



$$\bar{I}_{gen} = \bar{I}_{wire} = \bar{I}_L = \frac{120\angle 0^\circ}{(2.1 + j0.05) + (6 + j2)}$$

$$\bar{I}_{gen} = 14.362 \angle -14.0256^\circ \text{ A}_{rms}$$

$$\begin{aligned} \bar{S}_{gen} &= \bar{V}_{gen} \bar{I}_{gen}^* = (120\angle 0^\circ)(14.362 \angle +14.03^\circ) \\ &= 1672 + j417.7 \text{ VA} \end{aligned}$$

$$P_{gen} = 1672 \text{ W} \quad Q_{gen} = 417.7 \text{ VA}$$

$$pf_{gen} = \cos 14.03^\circ = 0.97 \text{ lagging}$$

ex. cont.Direct cont.

$$\bar{V}_{\text{wire}} = \bar{I}_{\text{wire}} (\bar{Z}_{\text{wire}}) = (14.362 \angle -14.03^\circ)(2.1 + j0.05) \\ = 30.16875 \angle -12.662^\circ \text{ Vrms}$$

$$\bar{S}_{\text{wire}} = \bar{V}_{\text{wire}} \bar{I}_{\text{wire}}^* = (30.17 \angle -12.66^\circ)(14.362 \angle +14.03^\circ)$$

$$\bar{S}_{\text{wire}} = 433.16 + j10.313 \text{ VA}, \quad \underline{P_{\text{wire}} = 433.2 \text{ W}}, \quad \underline{Q_{\text{wire}} = 10.3 \text{ VAR}}$$

$$\bar{V}_L = \bar{I}_{\text{wire}} \bar{Z}_L = (14.362 \angle -14.03^\circ)(6 + j2)$$

$$= 90.833 \angle 4.409^\circ$$

Very bad (lights dim, $I \uparrow$ for constant power)

$$\bar{S}_L = \bar{V}_L \bar{I}_L^* = (90.833 \angle 4.409^\circ)(14.362 \angle +14.03^\circ)$$

$$= 1237.6 + j412.5 \text{ VA}$$

$$\underline{P_L = 1237.6 \text{ W}} \quad + \quad \underline{Q_L = 412.5 \text{ VAR}}$$


$$\% \text{ loss} = \frac{P_{\text{wire}}}{P_{\text{gen}}} \times 100\% = \frac{433.2}{1672} \times 100\% = \underline{26\%}$$

$$\% \text{ load} = \text{efficiency} = \frac{P_L}{P_{\text{gen}}} \times 100\% = \underline{74\%}$$

↑
not good


ex. cont.

Using Transformers

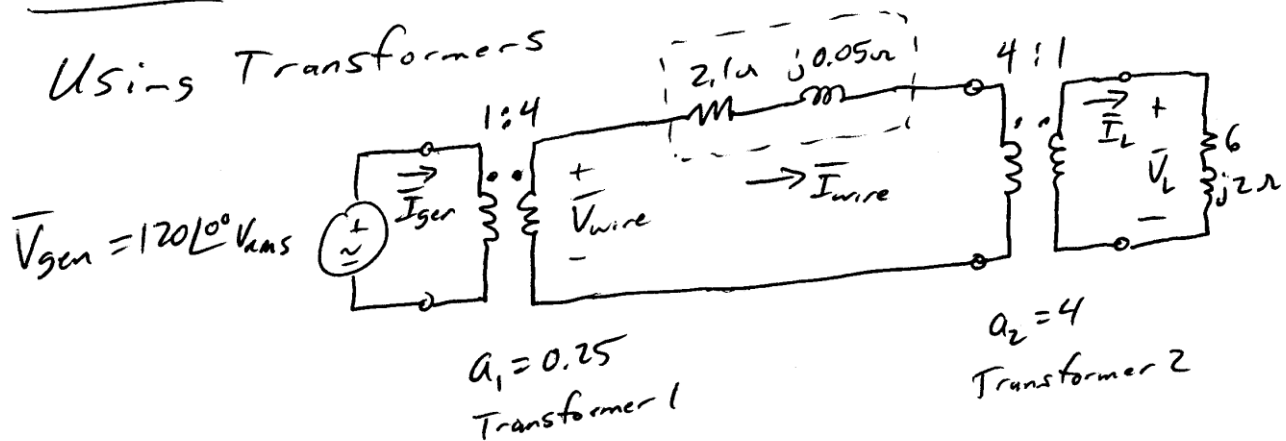


Use (2-15), to refer load impedance across Transformer 2
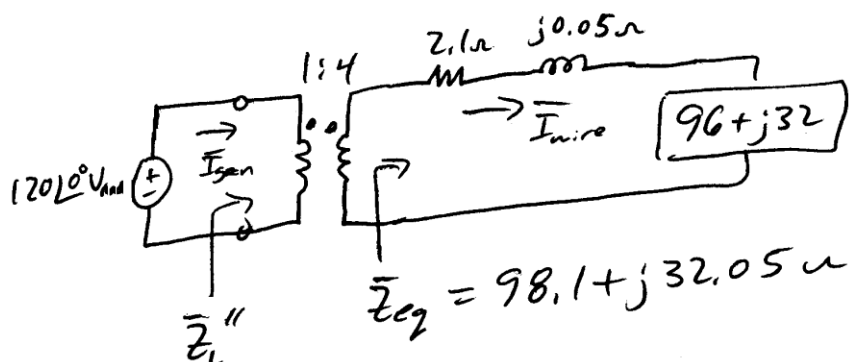
$$\bar{Z}_L' = a_2^2 \bar{Z}_L = 4^2 (6 + j2) = 96 + j32 \, \Omega$$



The "load seen" by the generator is then
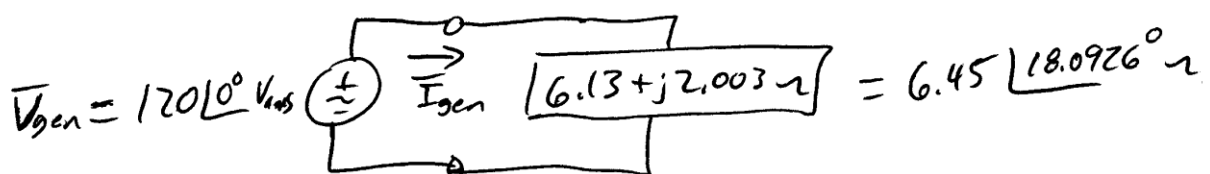
$$\begin{aligned}
 \bar{Z}_L'' &= a_1^2 \bar{Z}_{eq} = (0.25)^2 (98.1 + j32.05) \\
 &= 6.13125 + j2.003125 \, \Omega \leftarrow \text{close to } \bar{Z}_L!
 \end{aligned}$$



ex. cont.

Transformers cont.

$$\bar{I}_{gen,T} = \frac{120 \angle 0^\circ}{6.13 + j2.003} = 18.60415 \angle -18.0926^\circ \text{ Arms}$$

$$\begin{aligned} \bar{S}_{gen} &= \bar{V}_{gen} \bar{I}_{gen,T}^* = (120 \angle 0^\circ)(18.60415 \angle +18.0926^\circ) \\ &= \underline{2122.1 + j693.3 \text{ VA}} \quad \leftarrow \text{More power out!} \end{aligned}$$

$$P_{gen,T} = \underline{2122 \text{ W}} \quad \text{vs.} \quad P_{gen,0} = \underline{1672 \text{ W}}$$

$$Q_{gen,T} = 693.3 \text{ VAR} \quad \text{vs.} \quad Q_{gen,0} = 417.7 \text{ VAR}$$

$$\text{By (2-5)} \quad \frac{\bar{I}_p}{\bar{I}_s} = \frac{1}{a}, \quad \text{so} \quad \bar{I}_{wire,T} = a_1 \bar{I}_{gen,T}$$

$$\bar{I}_{wire,T} = (0.25)(18.60415 \angle -18.0926^\circ)$$

$$\bar{I}_{wire,T} = \underline{4.6510375 \angle -18.0926^\circ \text{ Arms}}$$

$$\bar{V}_{wire,T} = \bar{I}_{wire,T} (2.1 + j0.05)$$

$$= \underline{9.77 \angle -16.73^\circ \text{ V}_{rms}} \quad \leftarrow \underline{\text{Much lower!}}$$

$$\bar{S}_{wire,T} = \bar{V}_{wire,T} \bar{I}_{wire,T}^*$$

$$= (9.77 \angle -16.73^\circ)(4.651 \angle +18.093^\circ)$$

$$= 45.4 + j1.1 \text{ VA}$$

$$\text{Big Reduc.} \quad \left\{ \begin{array}{ll} P_{wire,T} = 45.4 \text{ W} & \text{vs.} \quad P_{wire,0} = 433.2 \text{ W} \\ Q_{wire,T} = 1.1 \text{ VAR} & \text{vs.} \quad Q_{wire,T} = 10.3 \text{ VAR} \end{array} \right.$$

Ex. Cont.Transformers cont.

Using (2-5) $\frac{\bar{I}_p}{\bar{I}_s} = 1/a$ again, $\bar{I}_L = a_2 \bar{I}_{wire,T}$

$$\bar{I}_{L,T} = (4)(4.651 \angle -18.0926^\circ) = \underline{18.60415 \angle -18.0926^\circ \text{ A}_{rms}}$$

$$= \bar{I}_{gen,T} !$$

$$\bar{V}_{L,T} = \bar{I}_{L,T} * (6 + j2) = (18.604 \angle -18.09^\circ)(6 + j2)$$

$$\underline{\bar{V}_{L,T} = 117.663 \angle 0.342^\circ \text{ V}_{rms}} \quad \leftarrow \text{only minor voltage drop}$$

$$\bar{S}_{L,T} = \bar{V}_{L,T} \bar{I}_{L,T}^* = (117.663 \angle 0.342^\circ)(18.604 \angle +18.09^\circ)$$

$$= 2076.7 + j 692.2 \text{ VA}$$

$$P_{L,T} = 2076.7 \text{ W} \quad \text{vs} \quad P_{L,0} = 1237.6 \text{ W}$$

$$Q_{L,T} = 692.2 \text{ VAR} \quad \text{vs.} \quad Q_{L,0} = 412.5 \text{ VAR}$$

$$\% \text{ loss} = \frac{P_{wire,T}}{P_{gen,T}} * 100\% = \frac{45.4}{2122.1} * 100\% = \underline{2.1\%}$$

$$\% \text{ load, efficiency} = \frac{P_{L,T}}{P_{gen,T}} * 100\% = \frac{2076.7}{2122.1} * 100\%$$

$$= \underline{\underline{97.9\%}}$$