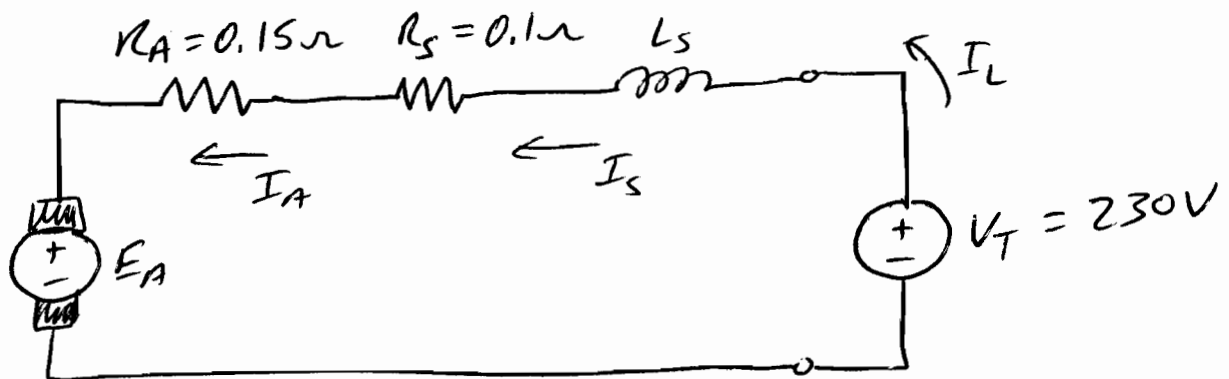


ex. A 230 V series DC motor has an armature resistance of 0.15Ω and a field winding resistance of 0.1Ω . When it operates at 750 RPM, the motor draws 80 A of current when supplied with the rated voltage. A lighter load is applied, causing the current to drop to 28 A. From a magnetization curve, it was found that the magnetic flux at 28 A is 40% of the flux at 80 A (non-linear). What is the new motor speed?



@ Steady-state, KVL gives

$$V_T = I_A R_S + I_A R_A + E_A$$

So, operating @ $n_m = 750 \text{ RPM}$ w/ 80 A current gives

$$E_{A,80} = 230 - 80(0.1 + 0.15) = 210 \text{ V}$$

By (7-41), $E_A = K' \phi n_m$. So, $E_{A,80} = K' \phi_{80} 750 = 210$
 $\hookrightarrow K' = \frac{0.28}{\phi_{80}}$

With a load drawing 20 A -

$$E_{A,20} = 230 - 20(0.1 + 0.15) = 223 \text{ V} = K' \phi_{20} n_m$$

$$\hookrightarrow 223 = \left(\frac{0.28}{\phi_{80}}\right)(0.4 \phi_{80}) n_m \Rightarrow n_{m,20} = 1991.07 \text{ RPM}$$

\Rightarrow lower load, faster speed \Leftarrow

ex. Next, the terminal voltage is changed from 230 V to 200 V while the current remains 80 A. What will be the new speed of the motor?

$$\text{By KVL, } E_{A,\text{new}} = 200\text{V} - 80(0.1 + 0.25) \\ = 180\text{V}$$

$$\text{Using } E_A = K' \Phi \omega_m, \text{ where } K' = \frac{0.28}{\Phi_{80}}$$

$$180 = \frac{0.28}{\Phi_{80}} \Phi_{80} \omega_{m,\text{new}}$$

$$\hookrightarrow \omega_{m,\text{new}} = \underline{\underline{642.86 \text{ RPM}}}$$

\Rightarrow lower V_T , lower speed!