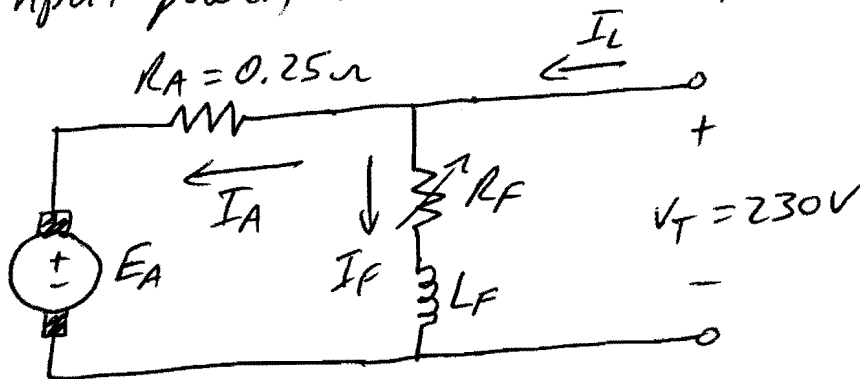


ex. A 230V shunt DC motor has an armature resistance of 0.25Ω and a field circuit resistance of 115Ω . At full load, the armature draws a current of 38A and the motor has a shaft speed of 1100 RPM. Assume core, mechanical, brush, and stray losses of 700W.

a) What is the induced + load torque, output power, input power, and efficiency at full load?



By KVL, $V_T = I_A R_A + E_A$

$$E_A = 230 - 38(0.25) = \underline{\underline{220.5\text{ V}}}$$

$$P_{\text{conv}} = E_A I_A = 220.5(38)$$

$$P_{\text{conv}} = \omega_m T_{\text{ind}} = \underline{\underline{8379\text{ W}}}$$

$$T_{\text{ind}} = \frac{8379}{1100(\pi/30)} = \underline{\underline{72.74\text{ N}\cdot\text{m}}}$$

ex. cont.

$$a) \text{ cont. } P_{out} = P_{conv} - \text{losses}$$

$$= 8379 - 700$$

$$\underline{P_{out} = 7679 \text{ W} = 10.3 \text{ hp}}$$

$$\tau_{LP} = \frac{P_{out}}{\omega_m} = \frac{7679}{1100(1/30)} = \underline{66.66 \text{ N}\cdot\text{m}}$$

$$I_F = \frac{V_T}{R_F} = \frac{230}{115} = 2 \text{ A}$$

$$I_L = I_A + I_F = 38 + 2 = \underline{40 \text{ A}} \quad (\text{KCL})$$

$$P_{IN} = V_T I_L = 230(40) = \underline{9200 \text{ W}}$$

$$P_{electrical} = P_{IN} - P_{conv} = 9200 - 8379 = \underline{821 \text{ W}}$$

or

$$= I_A^2 R_A + I_F^2 R_F = 38^2(0.25) + 2^2(115) \quad \nearrow$$

$$\text{Efficiency} = \eta = \frac{P_{out}}{P_{IN}} \times 100\% = \frac{7679}{9200} \times 100\%$$

$$\underline{\underline{\eta = 83.47\%}}$$

ex. conti.

b) Now, adjust the field resistance to 130Ω .
If the armature current & losses remain the same, what happens to the machine speed and other quantities?

$$E_{A_b} = 230 - 38(0.25) = \underline{220.5 \text{ V}} \quad \text{or No change}$$

$$I_{F_b} = \frac{230}{130} = \underline{1.76923 \text{ A}}$$

Back in Chapter 7, we found $E_A = K' \phi \Omega_m$

$$\text{So } E_{A_a} = 220.5 \text{ V} = K' \phi_a 1100$$

$$E_{A_b} = 220.5 \text{ V} = K' \phi_b \Omega_{m_b}$$

$$\text{Further, } \phi \propto I. \quad \text{So, } \frac{\phi_a}{\phi_b} = \frac{I_{F_a}}{I_{F_b}} = \frac{2}{1.76923}$$

Taking the ratio of E_A , we have

$$\frac{E_{A_b}}{E_{A_a}} = \frac{220.5}{220.5} = 1 = \frac{K' \phi_a 1100}{K' \phi_b \Omega_{m_b}}$$

$$\hookrightarrow \Omega_{m_b} = \frac{\phi_a}{\phi_b} (1100) = \frac{2}{1.76923} (1100) = \underline{\underline{1243.48 \text{ RPM}}}$$

↑
sped up!

ex. cont.

$$b) \text{ cont. } P_{conv_b} = E_A I_A = (220.5)(38) = \underline{8379 \text{ W}}$$

↑ No change

$$\tau_{ind_b} = \frac{P_{conv_b}}{\omega_{mb}} = \frac{8379}{1243.48(\text{rps})} = \underline{6.74 \text{ N.m}}$$

↑ less torque

$$P_{out_b} = P_{conv_b} - \text{losses} = 8379 - 700 = \underline{7679 \text{ W}}$$

↑
assume
constant

↑ No change

$$\tau_{out_b} = \tau_{L_b} = \frac{7679}{1243.48(\text{rps})} = \underline{\underline{6.18 \text{ N.m}}}$$

$$I_{L_b} = I_A + I_{F_b} = 38 + 1.76923 = \underline{39.76923 \text{ A}}$$

$$P_{IN_b} = V_T I_{L_b} = 230(39.76923) = \underline{9146.923 \text{ W}}$$

↑ lower

$$P_{electrical_b} = P_{IN_b} - P_{conv_b} = 9146.923 - 8379$$

$$= \underline{\underline{767.9 \text{ W}}}$$

$$\text{Efficiency} = \eta_b = \frac{P_{out_b}}{P_{IN_b}} \times 100 \%$$

$$= \frac{7679}{9146.923} \times 100 \%$$

$$\underline{\underline{\eta_b = 83.95 \%}}$$