- **Example-** The 1 MVA, 2.3 kVrms, 3-phase, Y-connected, 6-pole, 60 Hz, synchronous generator of the previous example is supplied the rated field current of 12 A and is turned by a steam turbine at 1200 RPM. If the core losses are 15 kW and the friction and windage losses are 20 kW, determine the following:
- a) What are the terminal voltage, phase voltage and induced voltage if the load draws the rated current at a power factor of 0.866 lagging? Assume we are looking at phase A with an assumed terminal voltage phase angle of zero (other phases will be at $\pm 120^{\circ}$).



From (A-31),

$$I_{\text{rated}} = \frac{S_{\text{rated}}}{\sqrt{3} V_{\text{rated}}} = \frac{10^6}{\sqrt{3} (2300)} = 251.022 \text{ A}_{\text{rms}}$$

The phase/armature current angle is $\theta = \cos^{-1}(pf) = \cos^{-1}(0.866) = 30^{\circ}$.

Then, the armature current is $\overline{I_A} = 251.022 \angle -30^\circ A_{\rm rms}$.

From the previous example, $V_T = 2470.8 \text{ V}_{\text{rms}}$ from the OCC at a field current of $I_f = 12 \text{ A}$. For a Y-connection, then

$$V_{\phi,\text{OC}} = \frac{2470.833}{\sqrt{3}} = 1426.5363 \text{ V}_{\text{rms}}.$$

a) cont.

By KVL,

$$\overline{E}_{A} = \overline{I}_{A} \left(R_{A} + j X_{S} \right) + V_{\phi} \angle 0$$

which yields

$$1426.5 \angle \delta = (251.022 \angle -30^{\circ})(0.3 + j1.57) + V_{\phi} \angle 0$$

 $1426.5 e^{j\delta} = 1426.5 \cos \delta + j1426.5 \sin \delta = 262.285 + j303.6379 + V_{\phi}$

Equate imaginary parts to solve for δ -

$$j1426.5\sin\delta = j303.6379$$

$$\sin \delta = \frac{303.6379}{1426.5} \implies \delta = \sin^{-1} \left(\frac{303.6379}{1426.5} \right) = 12.2897^{\circ}$$

Equate real parts to solve for phase voltage magnitude-

$$1426.5\cos\delta = 262.285 + V_{\phi}$$
$$V_{\phi} = 1426.5\cos(12.2897^{\circ}) - 262.285$$
$$V_{\phi} = 1131.525 \text{ V}_{\text{rms}}$$

Since, we assume the phase voltage is at zero degrees-

$$\overline{V_{\phi}} = 1131.525 \angle 0^{\circ} \mathrm{V_{rms}},$$

and the line-to-line terminal voltage for the Y-connected generator

$$V_T = (\sqrt{3}) 1131.525 = 1959.86 \text{ V}_{\text{rms}}.$$

synch_gen_load_example.doc

b) What are the voltage regulation VR, input power P_{in} , output power P_{out} , armature/stator copper losses P_{SCL} , and efficiency η ?

$$VR = \frac{V_{NL} - V_{FL}}{V_{FL}} * 100\% = \frac{2470.8 - 1959.86}{1959.86} * 100\%$$

$$\frac{VR = 26.1\%}{V_{FL}}$$

$$P_{SCL} = 3 |\overline{I}_{A}|^{2} R_{A} = 3(251.022)^{2} 0.3$$

$$P_{SCL} = 56,710.8 \text{ W} = 56.7 \text{ kW}$$

$$P_{out} = S_{out} \cos \theta = 10^{6} (0.866)$$

$$P_{out} = 866,000 \text{ W} = 866 \text{ kW}$$

$$P_{in} = P_{out} + P_{losses} = P_{out} + (P_{friction/windage} + P_{core} + P_{SCL})$$

$$P_{in} = 866 + 20 + 15 + 56.7 = 957.7 \text{ kW}$$

$$\eta = \frac{P_{out}}{P_{in}} * 100\% = \frac{866}{957.7} * 100\% = 90.4\%$$

c) What are the applied torque τ_{app} (from the prime mover), converted power P_{conv} , and the induced torque (acts against prime mover) τ_{ind} ?

Now
$$P_{\rm in} = \tau_{\rm app} \,\omega_{\rm m}$$
, where $\omega_{\rm m} = n_{\rm m} \left(\frac{\pi}{30}\right) = 1200 \left(\frac{\pi}{30}\right) = 125.6637 \text{ rad/s}$.

So,

$$\tau_{\rm app} = \frac{P_{\rm in}}{\omega_{\rm m}} = \frac{957,711}{125.6637} = 7621.2 \text{ N} \cdot \text{m}.$$

$$P_{\rm conv} = P_{\rm in} - P_{\rm friction/windage} - P_{\rm core}$$

$$P_{\rm conv} = 957.7 - 20 - 15 = 922.7 \text{ kW}$$

$$\tau_{\rm ind} = \frac{P_{\rm conv}}{\omega_{\rm m}} = \frac{922,711}{125.6637} = 7342.7 \text{ N} \cdot \text{m}$$