

ex. A 45KVA, 2300:208-V_{rms} transformer has the following per-unit equivalent circuit parameters - $R_{eq} = 0.02$, $X_{eq} = 0.04$, $X_m = 20$, and $R_c = 90$. Determine the Secondary equivalent circuit. Then, determine the voltage regulation and efficiency for loads of:

a) 40 KVA w/ 0.9 leading pf, b) 45 KVA w/ pf = 1, and c) 38 KVA w/ 0.65 lagging pf.

$$S_{base} = 45 \text{ KVA}, V_{base} = 208 \text{ V}_{rms}$$

$$\Downarrow$$

$$Z_{base} = \frac{V_{base}^2}{S_{base}} = \frac{208^2}{45 \times 10^3} = 0.9614 \bar{2}$$


$$R_{eq,s} = R_{eq,pu}(Z_{base}) = 0.02(0.9614 \bar{2}) = 0.019228 \bar{4} \Omega$$

$$X_{eq,s} = X_{eq,pu}(Z_{base}) = 0.04(0.9614 \bar{2}) = 0.0384569 \Omega$$

$$R_{c,s} = R_{c,pu}(Z_{base}) = 86.528 \Omega$$

$$X_{m,s} = X_{m,pu}(Z_{base}) = 19.228 \bar{4} \Omega$$

$$a = \frac{2300}{208} = 11.0577$$

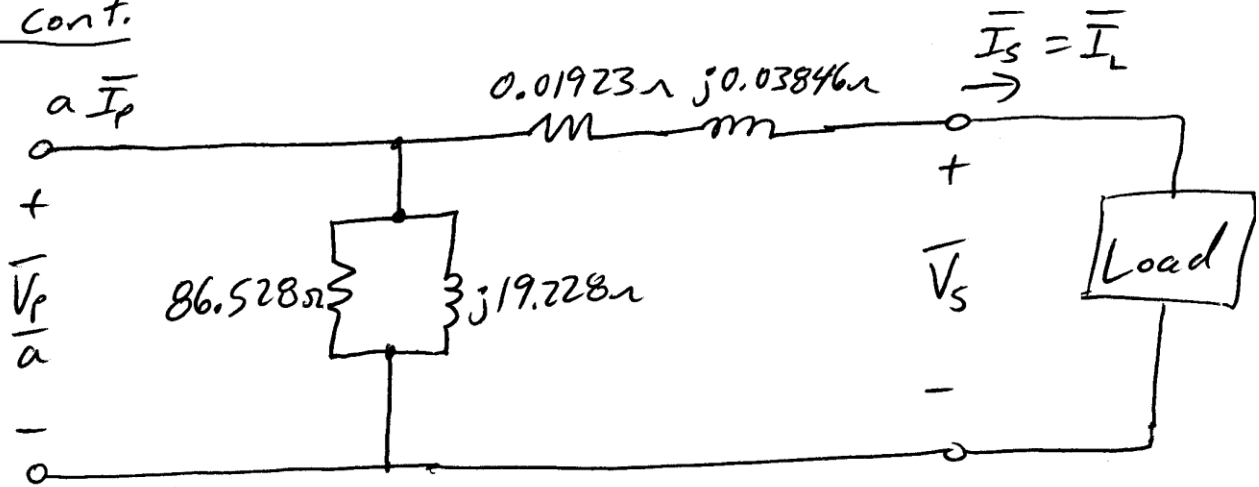Ex. cont.

a) Given $S_a = 40 \text{ kVA}$ & $\text{pf}_a = 0.9$ leading

Assume: $V_s = 208 \text{ V}_{\text{rms}}$ & $\underline{\bar{V}_s} = 208 \angle 0^\circ \text{ V}_{\text{rms}}$

$$I_s = I_L = \frac{S_L}{V_s} = \frac{40 \times 10^3}{208} = 192.3077 \text{ A}_{\text{rms}}$$

$$\theta_a = \cos^{-1}(0.9) = 25.841933^\circ \text{ leading}$$

$$\underline{\bar{I}_s} = 192.3077 \angle +25.842^\circ \text{ A}_{\text{rms}}$$

By KVL, $\underline{\bar{V}_p/a} = \underline{\bar{I}_s} (0.01923 + j0.03846) + \underline{\bar{V}_s}$

$$= (192.3 \angle 25.842^\circ) (0.01923 + j0.03846) + 208 \angle 0^\circ$$

$$= 208.2685 \angle 2.275^\circ \text{ V}_{\text{rms}}$$

$$VR_a = \frac{V_{p/a} - V_s}{V_s} \times 100\% = \frac{208.2685 - 208}{208} \times 100\%$$

$$\underline{VR_a = +0.129\%}$$

ex. cont.

a) cont.

$$P_{core} = \frac{(V_{p/a})^2}{R_{c,s}} = \frac{208.2685^2}{86.528} = \underline{\underline{501.29 \text{ W}}}$$

$$P_{cu} = (I_s)^2 R_{eq,s} = (192.3077)^2 0.01923$$

$$= \underline{\underline{711.11 \text{ W}}}$$

$$P_{out} = S_a(\text{pf}_a) = V_s I_s \cos \theta = (40 \times 10^3)(0.9)$$

$$= \underline{\underline{36,000 \text{ W}}}$$

$$\eta_a = \frac{P_{out}}{P_{cu} + P_{core} + P_{out}} \times 100\% = \frac{36000}{501.29 + 711.11 + 36000} \times 100\%$$

$$\underline{\underline{\eta_a = 96.74\%}}$$

b) Here, $S_b = 45 \text{ kVA}$ & $\text{pf}_b = 1 \Rightarrow \theta_b = 0^\circ$

$$\bar{V}_s = 208 \angle 0^\circ \text{ V}_{rms}, \quad I_s = \frac{45 \times 10^3}{208} = 216.346 \text{ A}_{rms}$$

$$\bar{I}_s = 216.346 \angle 0^\circ \text{ A}_{rms}$$

$$\bar{V}_p = (216.346 \angle 0^\circ)(0.01923 + j0.03846) + 208 \angle 0^\circ$$

$$= \underline{\underline{212.323 \angle 2.246^\circ \text{ V}_{rms}}}$$

ex. cont.

$$b) \text{ cont. } VR_b = \frac{212.323 - 208}{208} \times 100\% = \underline{\underline{+2.08\%}}$$

$$P_{\text{core}} = \frac{(212.323)^2}{86.528} = \underline{\underline{521 \text{ W}}}$$

$$P_{\text{cu}} = (216.346)^2 (0.01923) = \underline{\underline{900 \text{ W}}}$$

$$P_{\text{out}} = 45 \times 10^3 (1) = \underline{\underline{45,000 \text{ W}}}$$

$$\eta_b = \frac{45000}{521 + 900 + 45000} \times 100\% = \underline{\underline{96.94\%}}$$

$$c) \text{ Here, } S_c = 38 \text{ kVA} + pf_c = 0.65 \Rightarrow \theta_c = 49.4584^\circ$$

$$\bar{V}_s = 208 \angle 0^\circ \text{ V}_{\text{rms}}, \quad \bar{I}_s = \frac{38 \times 10^3}{208} = 182.6923 \text{ A}_{\text{rms}}$$

$$\bar{I}_c = 182.6923 \angle \overset{\text{lossing!}}{-49.4584^\circ} \text{ A}_{\text{rms}}$$

$$\begin{aligned} \frac{\bar{V}_p}{a} &= (182.6923 \angle -49.4584^\circ) (0.01923 + j0.03846) + 208 \angle 0^\circ \\ &= 215.63085 \angle 0.504^\circ \text{ V}_{\text{rms}} \end{aligned}$$

ex. cont.

c) cont.

$$VR_c = \frac{215.63 - 208}{208} \times 100\%$$

$$VR_c = 3.67\%$$

$$P_{core} = \frac{215.63^2}{86.528} = \underline{537.36 \text{ W}}$$

$$P_{cu} = (182.6923)^2 \cdot 0.01923 = \underline{641.78 \text{ W}}$$

$$P_{out} = S_c (pf_c) = 38 \times 10^3 (0.65) = \underline{24,700 \text{ W}}$$

$$\eta_c = \frac{24,700}{537.36 + 641.78 + 24,700} \times 100\%$$

$$\underline{\eta_c = 95.4\%}$$