

ex. Transformer Equivalent Circuit

ex. Given a transformer rated $220\text{ V}_{\text{rms}}$; $440\text{ V}_{\text{rms}}$ and 25 KVA at 60 Hz . An open circuit test on the $220\text{ V}_{\text{rms}}$ side yields: $V_{\text{oc}} = 220\text{ V}_{\text{rms}}$, $10\text{ A}_{\text{rms}} = I_{\text{oc}}$ and $P_{\text{oc}} = 700\text{ W}$. The short circuit test on the $220\text{ V}_{\text{rms}}$ side yields: $I_{\text{sc}} = 113.64\text{ A}_{\text{rms}}$, $V_{\text{sc}} = 19\text{ V}_{\text{rms}}$, and $P_{\text{sc}} = 1000\text{ W}$. Determine the equivalent transformer circuit on the primary side and secondary side,

$$\frac{\text{Open}}{\text{Ckt}} \quad Y_E = \frac{I_{\text{oc}}}{V_{\text{oc}}} = \frac{10}{220} = 0.045 \text{ S}$$

$$\theta_{ZE} = \cos^{-1}\left(\frac{P_{\text{oc}}}{V_{\text{oc}} I_{\text{oc}}}\right) = \cos^{-1}\left(\frac{700}{220(10)}\right)$$

$$= \cos^{-1}(0.318) = \underline{71.447^\circ}$$

$$\underline{pf = 0.3182 \text{ lagging}}$$

$$\downarrow$$

$$\bar{Y}_E = 0.045 \angle -71.447^\circ \text{ S} = 0.01446281 - j0.04309226 \text{ S}$$

$$R_c = \frac{1}{0.01446} = 69.143 \Omega \quad X_m = \frac{1}{0.0431} = 23.206 \Omega$$

$$\Rightarrow L_m = \frac{X_m}{2\pi(60)} = 61.56 \text{ mH}$$


ex. cont.

$$\frac{\text{Short}}{\text{ckt}} \quad Z_{SE} = \frac{V_{sc}}{I_{sc}} = \frac{19}{113.64} = 0.16719465 \, \Omega$$

$$\theta_{SE} = \cos^{-1} \left(\frac{P_{sc}}{V_{sc} I_{sc}} \right) = \cos^{-1} \left(\frac{1000}{19(113.64)} \right)$$

$$= \cos^{-1}(0.463143) = 62.4099^\circ$$


$$\bar{Z}_{SE} = 0.1672 \angle 62.41^\circ \, \Omega = \frac{0.077435 + j0.14818 \, \Omega}{\begin{matrix} \uparrow & \uparrow \\ R_{eq,P} & X_{eq,P} \end{matrix}}$$

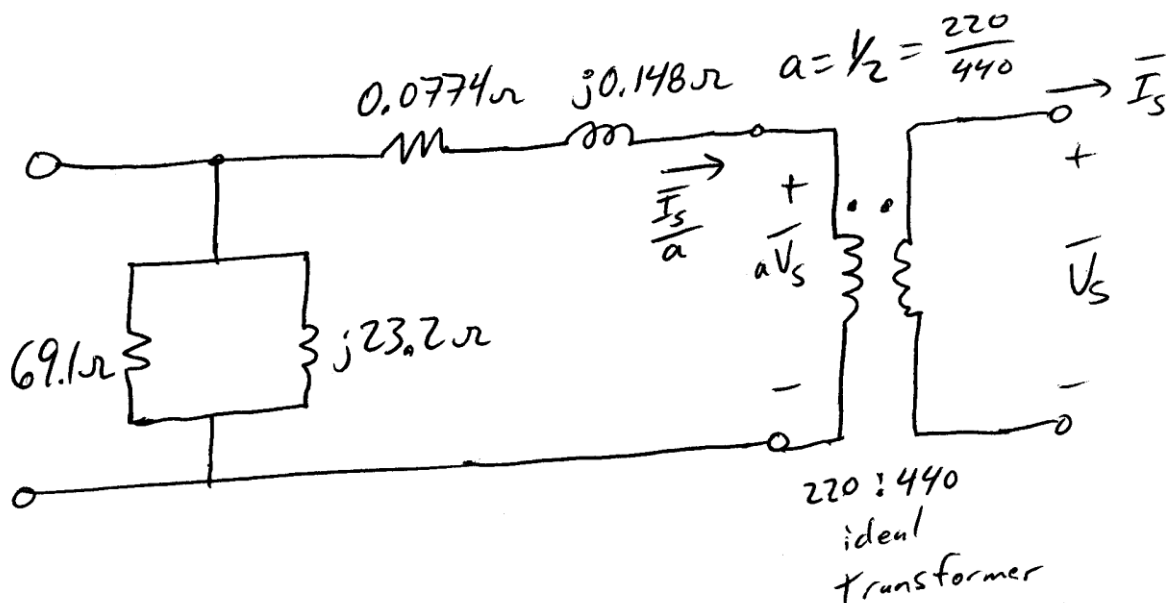Primary Approx. Equivalent Circuit

ex. cont.

To move/refer the impedances to the secondary side of the transformer, divide by a^2 .

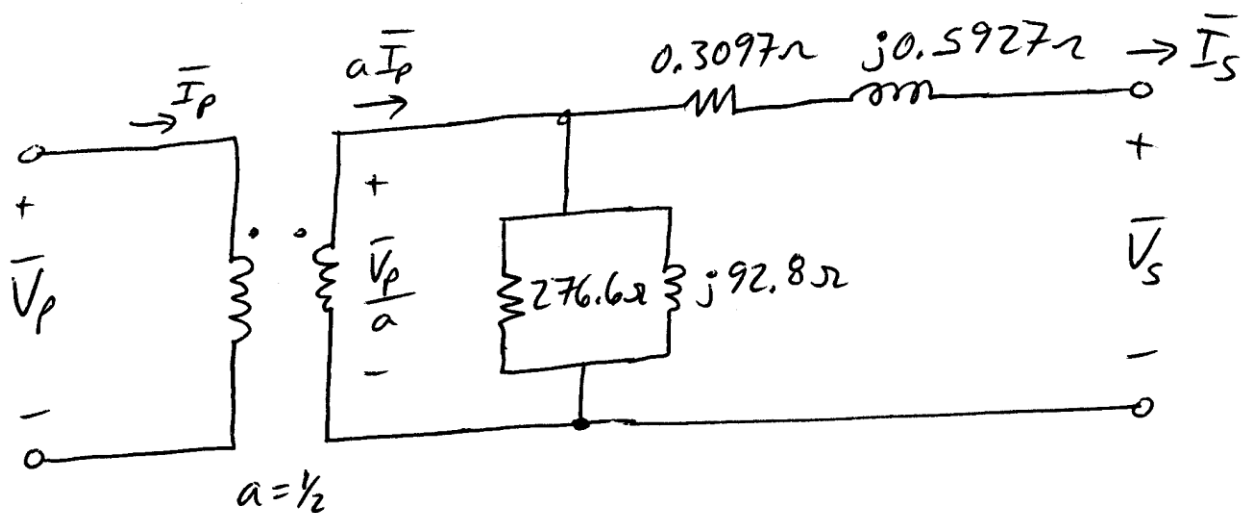In this case, $a^2 = (\frac{1}{2})^2 = \frac{1}{4}$. So, dividing by a^2 is the same as multiplying by 4.



If the dc wire resistances are measured to be

$$R_{w,p} = 0.05\Omega \text{ and } R_{w,s} = 0.1\Omega.$$

Estimate R_p , R_s , X_p , and X_s as well as L_p and L_s .

Previously -

$$R_{eq,p} = 0.077435\Omega$$

$$X_{eq,p} = 0.14818\Omega$$

$$\text{and } a = \frac{1}{2}$$

Assume that $\frac{R_p}{R_s} \approx \frac{R_{w,p}}{R_{w,s}} = \frac{0.05}{0.1} = \frac{1}{2} = K_w$

Then $R_{eq,p} = R_p + a^2 R_s = K_w R_s + a^2 R_s$

$$0.077435 = \frac{1}{2} R_s + \left(\frac{1}{2}\right)^2 R_s$$

$$\hookrightarrow \underline{\underline{R_s = 0.103247 \Omega}}$$

$$R_p = K_w R_s = \frac{1}{2} R_s = \underline{\underline{0.051623 \Omega}}$$

Similarly, assume $\frac{X_p}{X_s} = K_w$

Then $X_{eq,p} = X_p + a^2 X_s = K_w X_s + a^2 X_s$

$$0.14818 = \frac{1}{2} X_s + \left(\frac{1}{2}\right)^2 X_s$$

$$\hookrightarrow \underline{\underline{X_s = 0.19757 \Omega}} \quad \Rightarrow \quad \underline{\underline{L_s = \frac{X_s}{2\pi(60)} = 0.524 \text{ mH}}}$$

$$X_p = K_w X_s = \underline{\underline{0.098787 \Omega}} \quad \Rightarrow \quad \underline{\underline{L_p = 0.262 \text{ mH}}}$$