

EX. Take transformer equivalent circuit from previous example and express on a per-unit basis.

Ratings: 220:440 V_{rms}, 25 KVA @ 60 Hz

Choose $S_{base} = 25 \text{ KVA}$ $\rightarrow a = \frac{1}{2}$

$V_{base} = 440 \text{ V}_{rms}$ $\leftarrow$ secondary side

$$I_{base} = \frac{S_{base}}{V_{base}} = \frac{25 \times 10^3}{440} = 56.81 \text{ A}_{rms}$$

$$Z_{base} = \frac{V_{base}}{I_{base}} = \frac{440}{56.81} = 7.744 \Omega \quad \text{or}$$

$$= \frac{V_{base}^2}{S_{base}} = \frac{440^2}{25 \times 10^3} = 7.744 \Omega$$


Per-Unit (Secondary) Equiv. Circuit values:

$$R_{c,spu} = \frac{R_{c,s}}{Z_{base}} = \frac{276.6}{7.744} = 35.72 = 35.7$$

$$X_{m,spu} = \frac{X_{m,s}}{Z_{base}} = \frac{92.8}{7.744} = 11.98$$

$$R_{eq,spu} = \frac{R_{eq,s}}{Z_{base}} = \frac{0.3097}{7.744} = 0.0400$$

$$X_{eq,spu} = \frac{X_{eq,s}}{Z_{base}} = \frac{0.5927}{7.744} = 0.07654$$

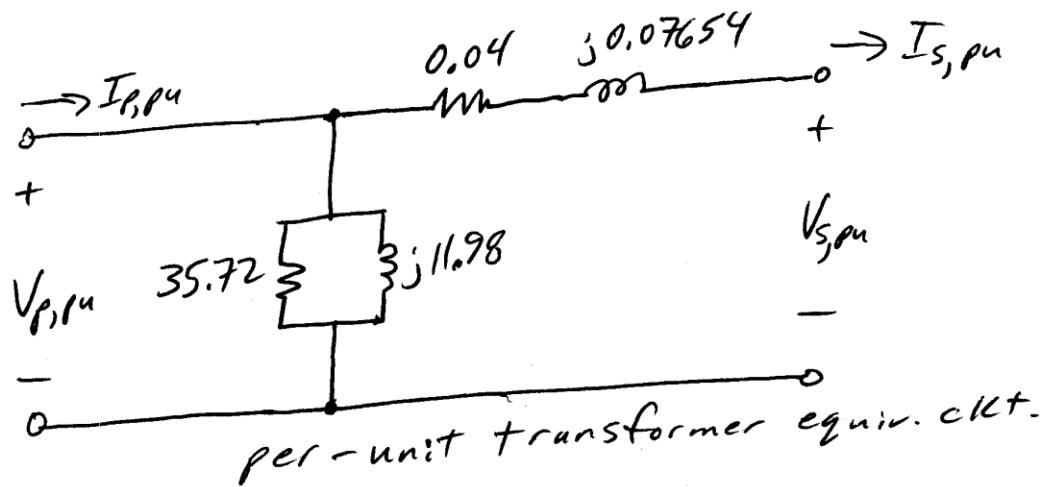ex. cont.

What if I wanted the primary side per-unit Equiv. circuit?

$$S_{base} = 25 \text{ KVA (no change)}$$

$$V_{base,p} = V_{base,s} a = 440 \left(\frac{1}{2}\right) = 220 \text{ V}_{rms}$$

$$I_{base,p} = \frac{S_{base}}{V_{base,p}} = \frac{25 \times 10^3}{220} = 113.63 \text{ A}_{rms}$$

$$Z_{base,p} = \frac{V_{base,p}}{I_{base,p}} = \frac{220}{113.63} = 1.936 \Omega$$

Express primary equiv. circuit values on per-unit basis.

$$\left\{ \begin{array}{l} R_{c,p,pu} = \frac{R_c}{Z_{base,p}} = \frac{69.1}{1.936} = 35.69 \approx 35.7 \\ X_{m,p,pu} = \frac{X_{m,p}}{Z_{base,p}} = \frac{23.2}{1.936} = 11.98 \\ R_{eq,p,pu} = \frac{0.0774}{1.936} = 0.4 \quad + \quad X_{eq,p,pu} = 0.07654 \end{array} \right\} \text{ look familiar?}$$

Same equiv. ckt!